

Lecture 1

I. Bazarov

web site: blackboard.cornell.edu
↳ TA info, office hours, etc.

Texts: E. Kirkland and R. Littauer, Lab Manual
I. Bazarov, Supplement

Labs: 401 MW 7:30PM - 10:30PM
402 TR 1:25PM - 4:25PM


HW: 1 each week, due next week (Friday)
no late HW accepted

Grade: 35% lab

More info: Blackboard, printouts, 1st lab (!)

Goals: -
-
-

Typical Electronic Device

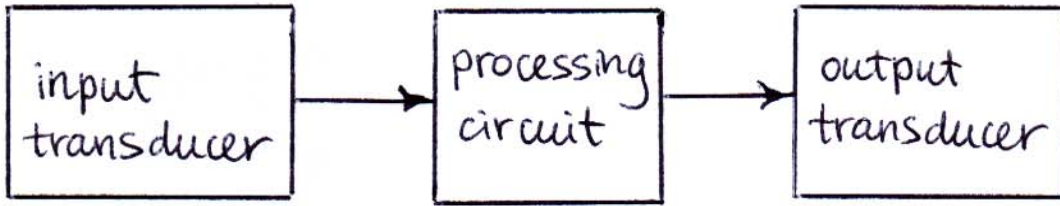

transducer :

input transducer :

output transducer :

Two types of circuits

info is represented by

typical functions :

Q: possible problems ?

input/output signals have

typical fcn :

Basic quantities of interest

$V = \text{voltage} =$

$I = \text{current} =$

DC :

AC :


Convention $I, V -$
 $i, v -$

$I, V -$ represent

Electric circuit -

Linear circuit devices

- ① Resistor obeys Ohm's law

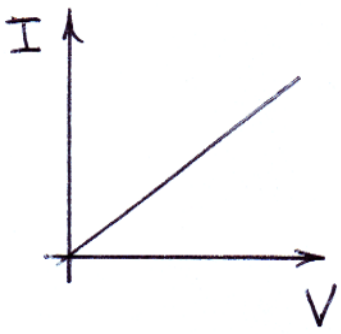

I-V curve


$R \neq f(I, V)$



Black	0	n/a - 20%
Brown	1	silver - 10%
R	2	gold - 5%
O	3	
Y	4	
G	5	
B	6	
V	7	
Gray	8	
White	9	


Conductance = inverse resistance

Series resistors

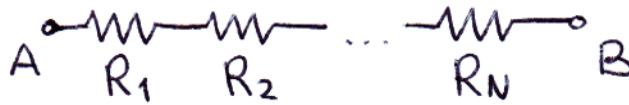


$R_T = \sum_k R_k$

Parallel

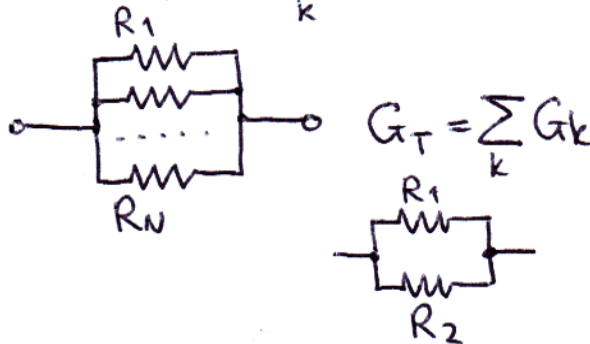


Y-Δ transformation

$\Delta \rightarrow Y$:

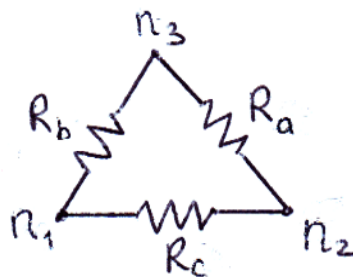


$Y \rightarrow \Delta$:

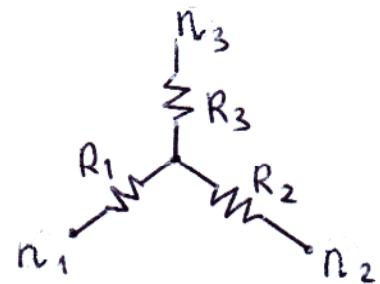


Lecture 2

Power

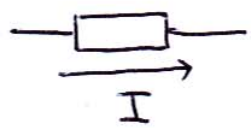

instantaneous power

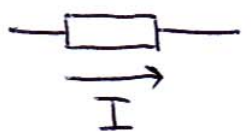


② Voltage source

or

or

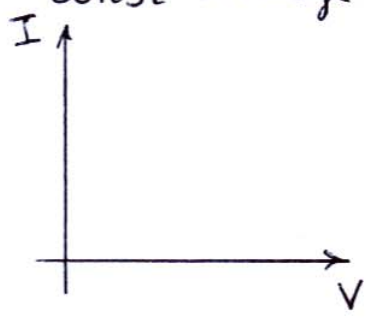ideal voltage source holds const voltage no matter what




Practical vott. source

voltage may not be const

③ Current source

or or


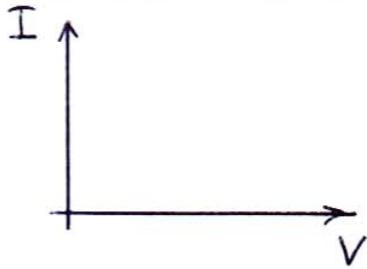
Ideal current source supplies const current no matter what




Practical current source

Circuit analysis

Kirchhoff's voltage law (KVL)

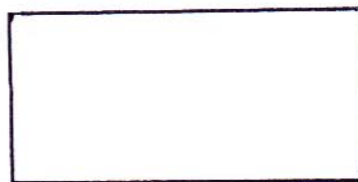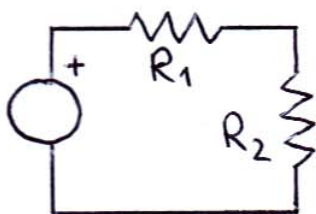


Kirchhoff's current law (KCL)

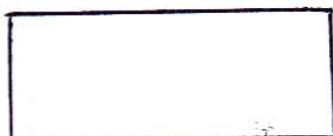


KVL & KCL are completely general

Voltage divider

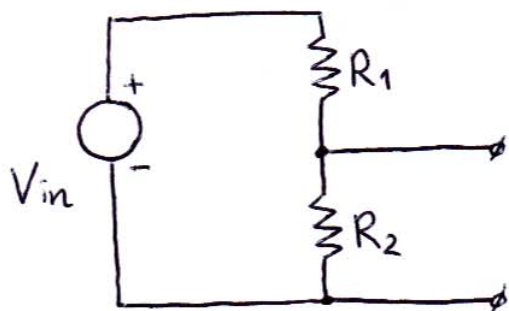

A word on notations

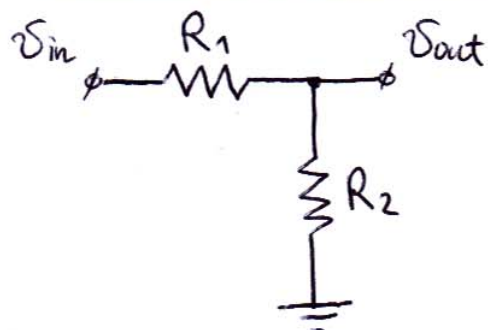

Circuit simplifying techniques

Superposition

Given a _____ circuit containing several i_s , v_s , the total i , v at a given point is algebraic sum from _____ source.


step 1.

step 2.

step 3.

Ex.

Find I?




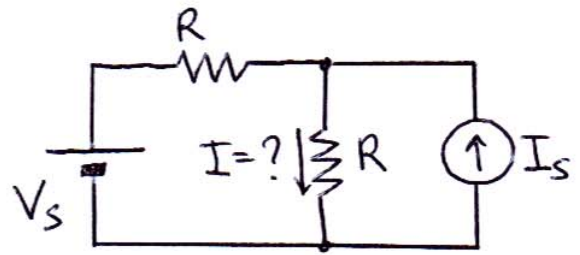


① open I_s

② short V_s

③ sum

Thevenin equivalent

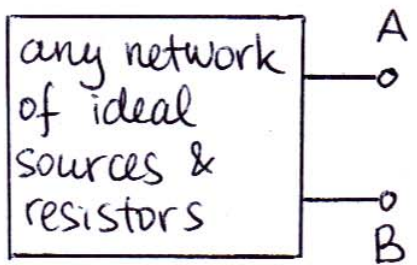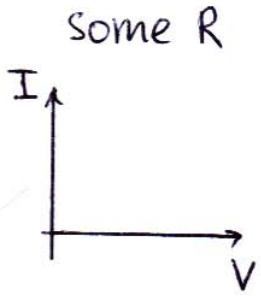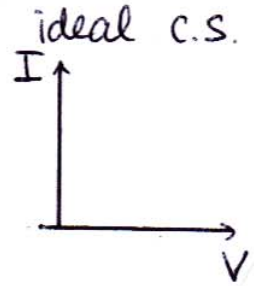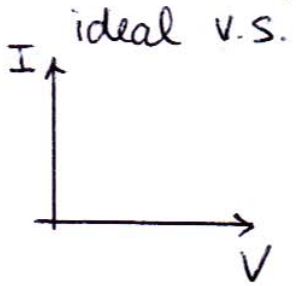


any combination of _____ circuit elements
 with two output terminals may be replaced with
 _____ and _____

$V_{TH} =$

$R_{TH} =$

Lecture 3

Thevenin th. - example

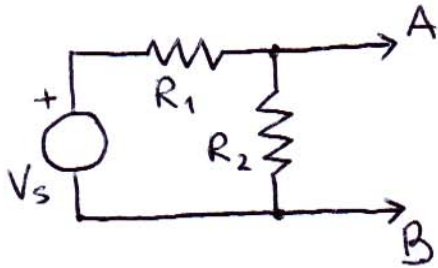

Useful trick: to find R_{Th} , short _____ and open _____. R_{Th} is resistance by looking inside the two terminals.

Norton equivalent

same as Thevenin but \Rightarrow

$$I_N = \quad , R_N =$$

Linear time-dep. elements

(2)

Linear if KVL & KCL contain terms \propto
but never

(4) Capacitor




2 parallel plates
separated by
insulator

$$Q =$$


$$[C] = \text{farads}$$

$$C_{\text{Total}} =$$
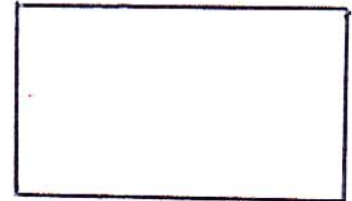
$$V = \frac{Q}{C}, \Rightarrow \frac{dV}{dt} =$$



(5) Inductors


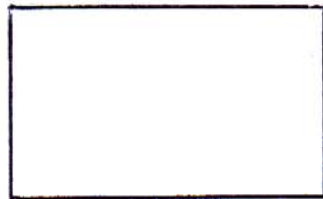


$$[L] = \frac{V \cdot s}{A} = \text{henries}$$

$$L_{TOTAL} =$$

Bulky \approx MHz, not routinely used

Low - Pass filter

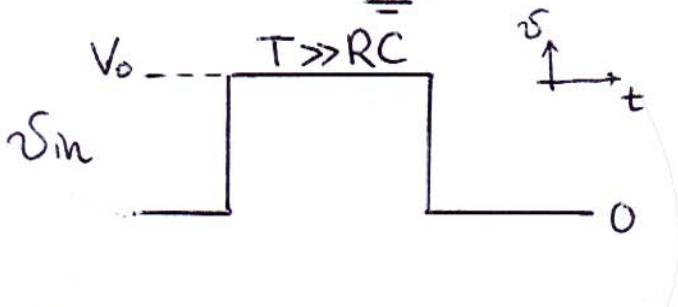
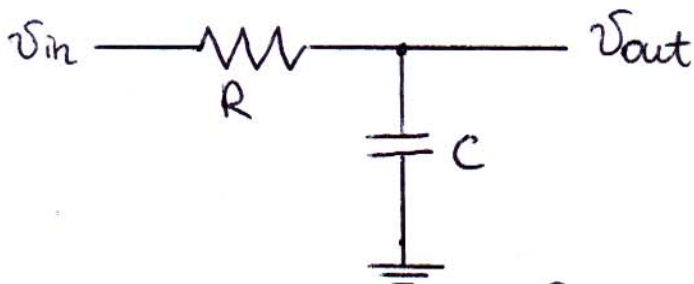


v_out


v_R

Piece of trivia:
v_c vs t after
step in voltage

High-pass filter

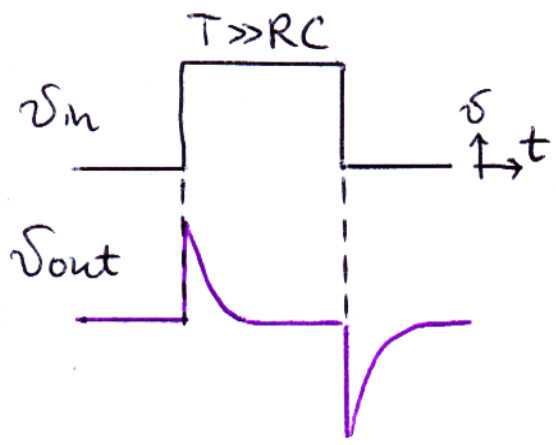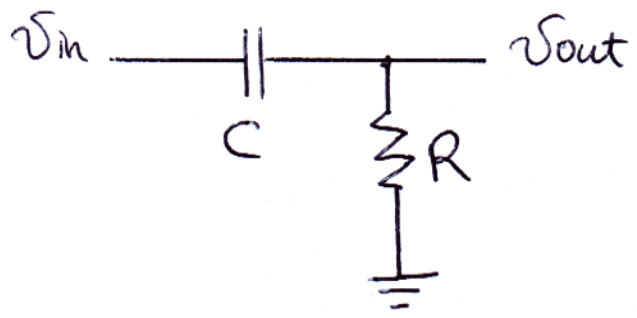

Exp I-10

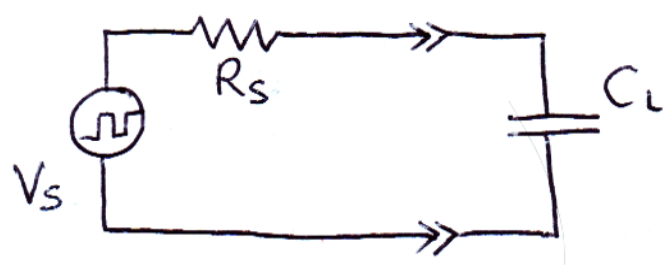

Function generator produces \square , \wedge , \sim
drives capacitive load C_L

input \square

\Rightarrow output

'Fake' large R_i by adding large R to f -generator.

Need to transmit shape. How?

Soln.