

Lecture 1

I. Bazarov , Newman 210 / Wilson 373

web site: blackboard.cornell.edu (self enroll)
↳ TA info, office hours, etc.

Texts: E. Kirkland and R. Littauer, Lab Manual
I. Bazarov, Supplement

Labs: 401 MW 7:30PM-10:30PM starts today!
402 TR 1:25PM-4:25PM

HW: 1 each week, due next week (Friday)
Soln. handed out → no late HW accepted


Grade: 40% lab
40% exam (prelim + final)
15% HW
5% participation (e.g. mailing list)

More info: Blackboard, printouts, 1st lab (!)

Goals:

- design & build simple circuits
- trouble shoot equipment
- analyze complicated circuit diagrams

Typical Electronic Device

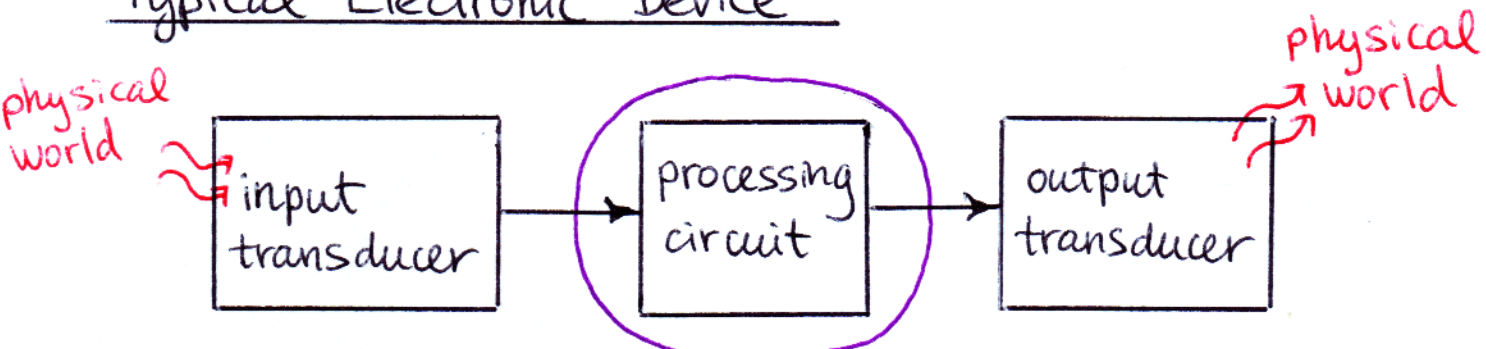

transducer: converts physical quantity into electric signal (and vice versa)

input transducer: e.g. thermistor (T → R)
(sensor) microphone (sound → electric signal)

output transducer: e.g. LED (electr. → light)
speaker (electr. → sound)
robotic arm (aka actuator)

Two types of circuits


Analog info is represented by continuously varying signal

typical functions: amplification
filters (bass, treble)
mixing

Q: possible problems?

- sensitive to noise
- p.s. drift

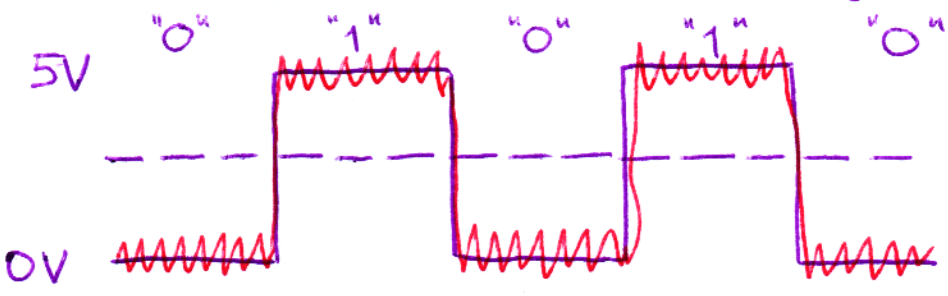Digital input/output signals have discrete values, e.g. 0 and 5V



typical fcn: memory storage
logic, etc.

Basic quantities of interest

$V = \text{voltage} = \text{electric potential difference}$
(measured w.r.t. some reference, e.g. "ground")

$[V] = \text{volts}$

$q\Delta V = \Delta PE$ (of charge q due to ΔV)

$I = \text{current} = \text{charge flow rate} = \text{charge / unit time}$

$[I] = \text{amps}$

direction: dir. of +ve charge flow

DC : I, V indep. of time

AC : ~~n~~ time varying


Convention I, V - pure dc
 i, v - ac or dc+ac

I, V - represent physical quantities (sound, temp, color, etc.)

Electric circuit - interconnection of elect. devices which creates and/or manipulates I, V to perform some fcn.

Linear circuit devices


① Resistor

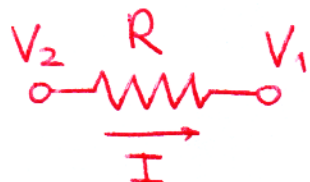

obeys Ohm's law


$$I = \frac{V_2 - V_1}{R} = \frac{V}{R}$$

$[R] = \text{ohm}, \Omega$

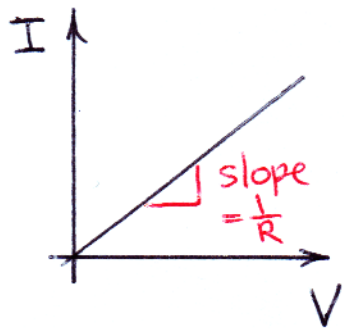

value	
Black	0
Brown	1
R	2
O	3
Y	4
G	5
B	6
V	7
Gray	8
White	9

accuracy	
n/a	-20%
silver	-10%
gold	-5%

example

 O B R S
 3 6 2 (10%)
 $= 36 \times 10^2 \pm 10\%$
 $= 3.6 \text{ k}\Omega$


Richard of York gave battle in vain

Typical power rating $\frac{1}{4}$ to $\frac{1}{2}$ W

Conductance = inverse resistance $= G = \frac{1}{R} = \frac{I}{V}$


[G] = siemens (mho)

Series resistors

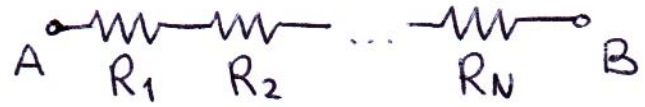


$R_T = \sum_k R_k$ add resistances

Parallel

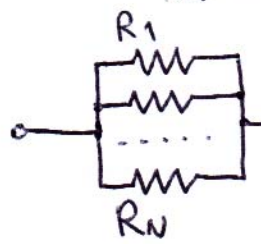

$G_T = \sum_k G_k$ add conductances, $R_T = G_T^{-1}$


give examples

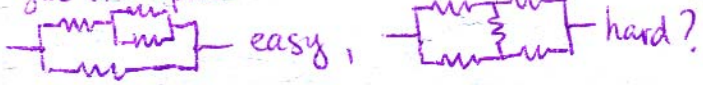


$R_T = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$

Y-Δ transformation

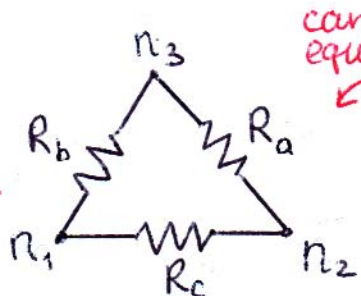$\Delta \rightarrow Y$: $R = R_a + R_b + R_c$
 $R_1 = \frac{R_b R_c}{R}$, $R_2 = \frac{R_c R_a}{R}$, $R_3 = \frac{R_a R_b}{R}$



can be made equivalent

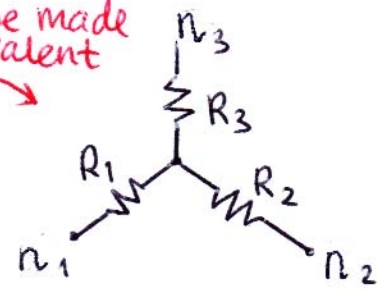

$Y \rightarrow \Delta$: $G = G_1 + G_2 + G_3$
 $G_a = \frac{G_2 G_3}{G}$, $G_b = \frac{G_3 G_1}{G}$, $G_c = \frac{G_1 G_2}{G}$

proof: HW