

Lecture 9s-plane

$s \equiv \sigma + j\omega$  - generalized complex frequency


$v(t) = V_0 e^{st}$  ;  $\text{Re}\{s\} < 0$  - exp. decay

$\text{Re}\{s\} > 0$  - exp. growth

if  $s = j\omega \Rightarrow$  AC sine steady case

Impedance in s-domain:  $Z_C = \frac{1}{sC}$  ,  $Z_L = sL$

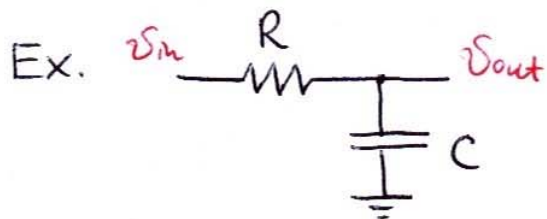$G(s) = \frac{V_{out}(s)}{V_{in}(s)}$  - gain (transfer fcn) in s-plane




Let:  $v_{in} = V_0 e^{st}$

$$G(s) = \frac{v_{in} \cdot \frac{1}{sC}}{R + \frac{1}{sC}} \cdot \frac{1}{v_{in}} = \frac{1}{sRC + 1}$$

$$G(\omega) : G(s \rightarrow j\omega)$$

$$G(s) : G(j\omega \rightarrow s)$$

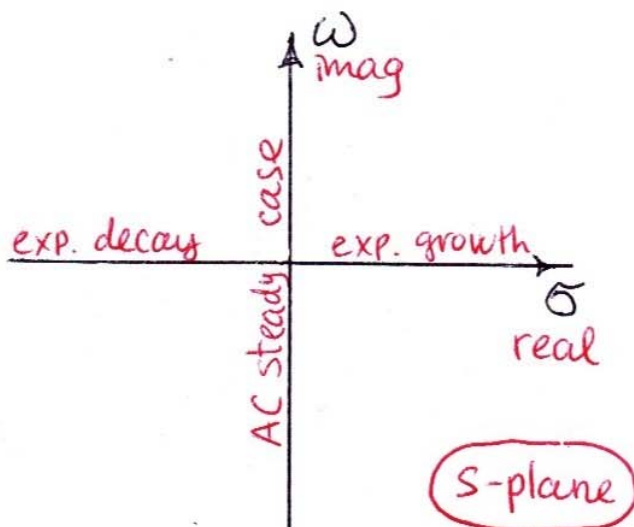

## Zero-pole form of transfer fcn

(2)

Most natural when using s-plane

$$G(s) = \frac{N(s)}{D(s)} = K \frac{(s-s_{z1})(s-s_{z2})\dots}{(s-s_{p1})(s-s_{p2})\dots}$$

$$\Rightarrow G(s) \approx \begin{cases} s_{z1}, \dots & \text{polynomial roots of } N(s), |G| \rightarrow 0 \text{ zeros} \\ s_{p1}, \dots & \text{polynomial roots of } D(s), |G| \rightarrow \infty \text{ poles} \end{cases}$$

- convenient representation that provides insight into circuit response

### Some properties

1) # poles  $\geq$  # zeros

Q: why?

A: otherwise  $|G(\omega \rightarrow \infty)| \rightarrow \infty$   
unphysical


2) circuit (filter) order:

degree of  $D(s)$  polynomial (= # poles)

Filter order matches # of L, C elements

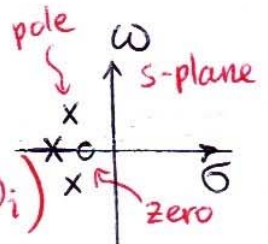3) zeros & poles must be real, or come

in complex conjugate pairs ( $z_{pi} = \sigma_i \pm j\omega_i$ )



4) poles  $\Rightarrow$  homogeneous response of the system

Q: why?

A: real coeff. of  $N(s), D(s)$  poly.


(some initial cond. but  $v_m \rightarrow 0$ )

$N(s)$  does not matter for homog. response


$$v_{out} = \sum_i c_i e^{s_{pi}t}$$

$\uparrow$  initial cond.

③

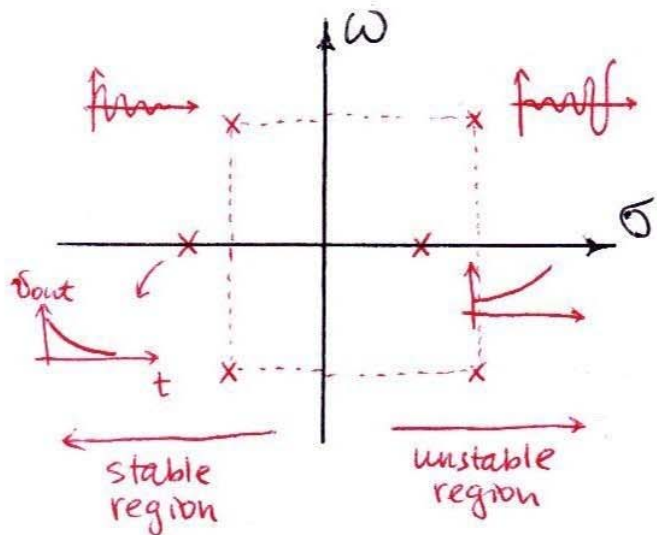

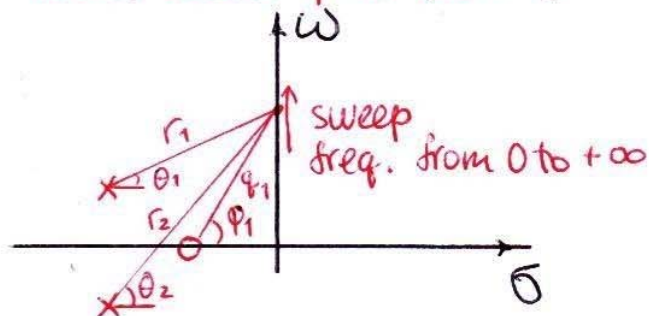Q: How to get  $G(\omega)$  from zero-pole form?



Bode Plots:



E.g. consider basic cases when zeros & poles are real & nonpositive

$$|G(\omega)| = K \frac{q_1 q_2 \dots}{r_1 r_2 \dots}$$

$$\Phi[G(\omega)] = (\phi_1 + \phi_2 + \dots) - (\theta_1 + \theta_2 + \dots)$$

⇒ on Bode plots:

add zeros & subtract poles

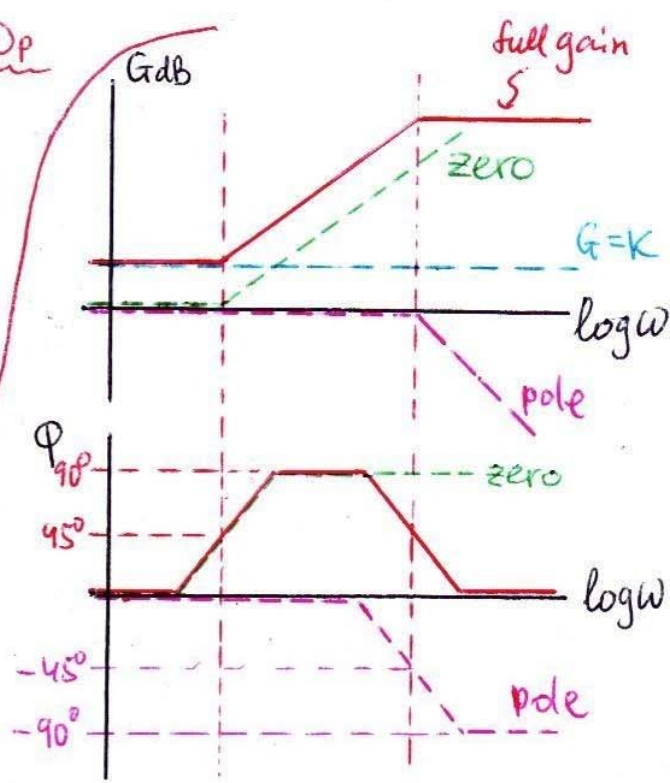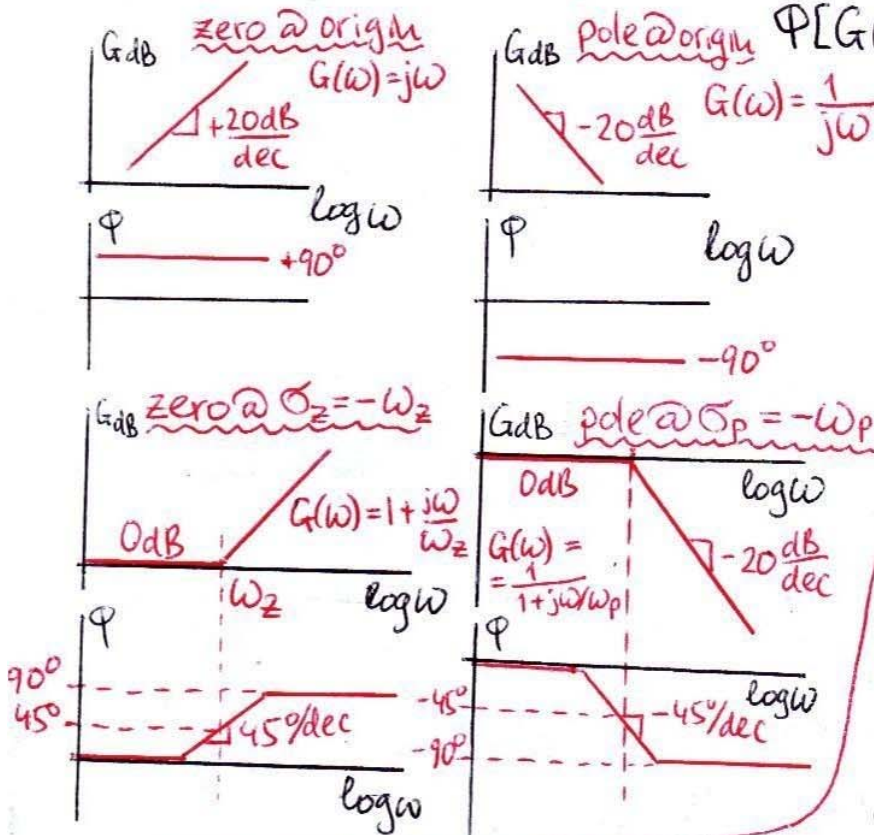


Ex.  $G = K \frac{1 + j\omega/\omega_z}{1 + j\omega/\omega_p}$   
 let  $\omega_z \ll \omega_p$

⇒

# Fourier Analysis (connect time & freq. domains)

(4)

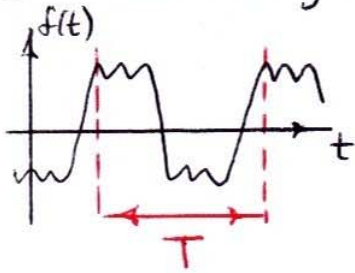

Basic idea: decompose periodic  $f(t)$  into harmonics

$$f(t) = \sum_{n=-\infty}^{\infty} c_n e^{jn\omega t}$$

$\omega = \frac{2\pi}{T}$  - fund. freq.;  $c_n$  - generally complex, corresponds to harm.  $n$

Definition:  $g(t)$  and  $h(t)$  orthogonal if

$$\int_a^b g(t) h^*(t) dt = 0$$

$\{e^{jn\omega t}\}$  forms orthogonal set:  $\int_{t_0}^{t_0+T} e^{jn\omega t} (e^{jm\omega t})^* dt = \begin{cases} 0, & m \neq n \\ T, & m = n \end{cases}$

$$\int_{t_0}^{t_0+T} e^{-jm\omega t} f(t) dt = \sum_{n=-\infty}^{\infty} c_n \underbrace{\int_{t_0}^{t_0+T} e^{-jm\omega t} e^{jn\omega t} dt}_{\text{orthogonal if } m \neq n} \Rightarrow \text{only } c_m \text{ survives}$$

$$\Rightarrow c_m = \frac{1}{T} \int_{t_0}^{t_0+T} e^{-jm\omega t} f(t) dt$$

If  $f(t)$  is real, the sum sym. with  $n$

$$f(t) = \text{Re} \left\{ \sum_{n=0}^{\infty} \tilde{c}_n e^{jn\omega t} \right\} \text{ with } \tilde{c}_0 = c_0 \text{ and } \tilde{c}_n = 2c_n, n > 0$$

Strategy

arbitrary periodic wave

1) source decomp. (superp.)

$$v_{in} = \sum_{n=0}^{\infty} \hat{v}_{m,n} e^{jn\omega t}$$

2) find response @ each harmonic  $n\omega$

$$\hat{v}_{out,n} = \hat{v}_{m,n} \underbrace{G(n\omega)}_{\text{network gain}}$$

3) find  $v_{out} = \text{Re} \left\{ \sum_{n=0}^{\infty} \hat{v}_{out,n} e^{jn\omega t} \right\}$

