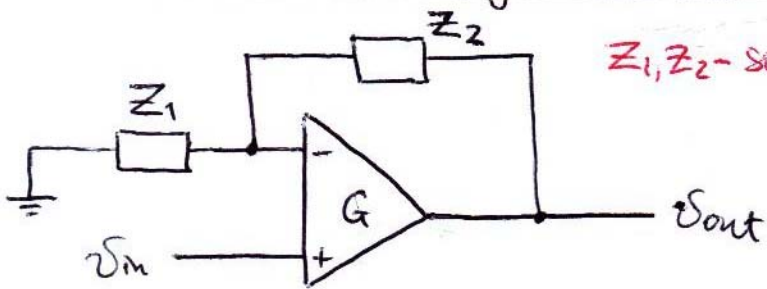


Lecture 11

Two basic configurations with negative feedback



$Z_1, Z_2$  - some impedances

"non inverting"  $v_m = v_+$

Same as what we looked at during last lecture.

"closed loop gain":  $G_{CL} \equiv \frac{v_{out}}{v_m}$

$$G_{CL} = \frac{G}{1+GH} = \frac{1}{H} \frac{1}{1 + \frac{1}{GH}}$$


$$G_{CL} \approx \frac{1}{H} \text{ if } |GH| \gg 1$$

"neg. F.B. transfer fcn":  $H = \frac{v_-}{v_{out}}$

$$H = \frac{Z_1}{Z_1 + Z_2}$$

"loop gain": gain for signal going around a closed loop

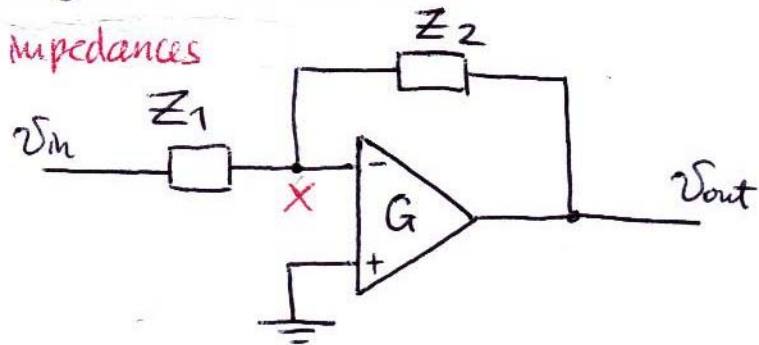GH - very important for stability (next lecture)



"inverting",  $v_m \rightarrow v_-$

1) 
$$v_x = v_m \frac{Z_2}{Z_1 + Z_2} + v_{out} \frac{Z_1}{Z_1 + Z_2}$$
 (superposition)

2) 
$$v_{out} = G(v_+ - v_-) = G(0 - v_x)$$

3) 
$$\Rightarrow G_{CL} = \frac{v_{out}}{v_m} = -\frac{GZ_2}{GZ_1 + Z_1 + Z_2}$$

4) introduce

$$H' = \frac{Z_1}{Z_2}, \Rightarrow G_{CL} = -\frac{1}{H'} \frac{1}{1 + \frac{1}{GH}}$$

"closed loop gain"

$$G_{CL} = -\frac{1}{H'} \frac{1}{1 + \frac{1}{GH}}$$


$$G_{CL} \approx -\frac{1}{H'} \text{ if } |GH| \gg 1$$

"loop gain" GH

# Applications of neg. feedback

(2)
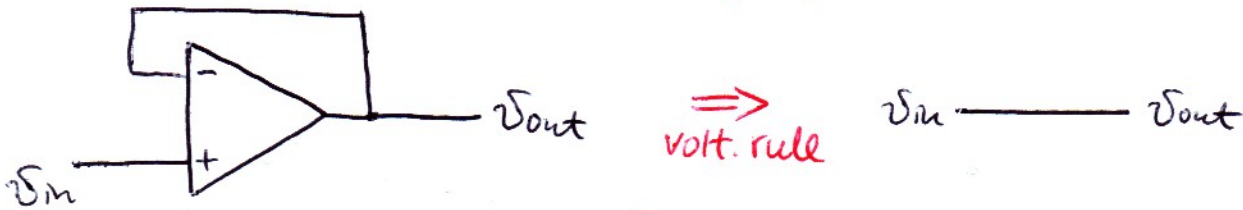
## ① voltage follower (amplifying buffer)



alt. method  $G_{CL} = \frac{G}{1+GH} \approx 1, G \gg 1$


741:  $G \sim 10^5, R_{in} \sim M\Omega, R_{out} \sim 80\Omega$

$$R_{in,CL} = R_{in} (1 + (1)G) \approx 10^{11} \Omega$$

$$R_{out,CL} = \frac{R_{out}}{1 + (1)G} \approx 10^{-3} \Omega$$

- draws no current (no loading)
- drive low  $Z$  load with high  $Z$  source (power gain)

## ② noninverting amplifier

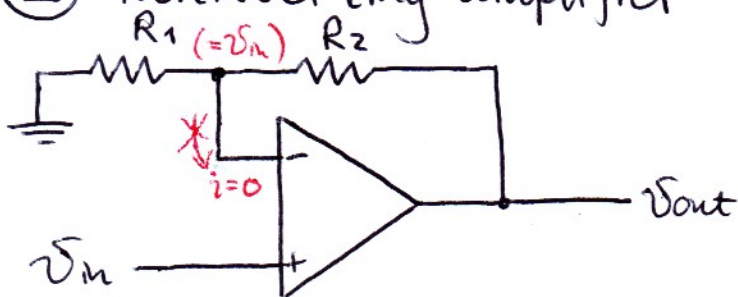

$$H = \frac{R_1}{R_1 + R_2} \Rightarrow$$

$$G_{CL} = \frac{R_1 + R_2}{R_1}$$


$v_- = v_{in}$  (voltage rule)

$R_{in,CL} = R_{in} (1 + GH)$  is large


$R_{out,CL} = \frac{R_{out}}{1 + GH}$  is very small

### ③ inverting amplifier

③

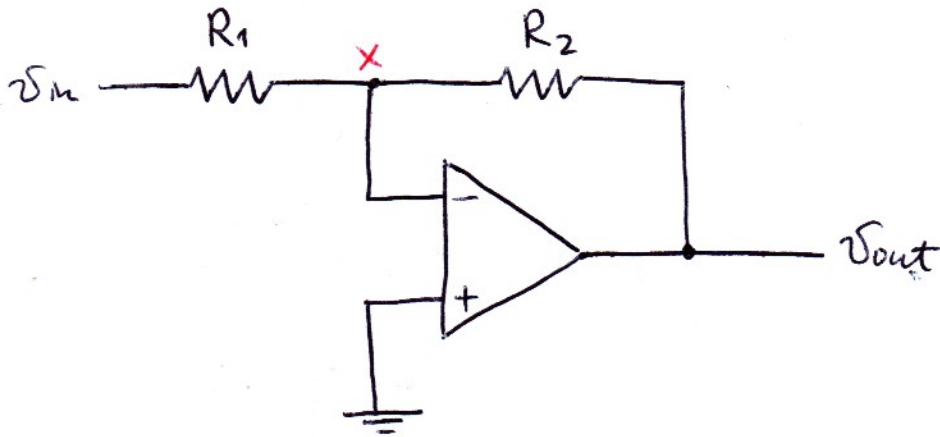

Note: cannot use

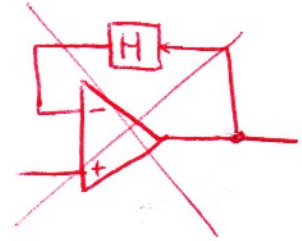

"X" - virtual ground (0V, by volt. rule);  $H' = \frac{R_1}{R_2}$

$$\Rightarrow G_{CL} = -\frac{1}{H'} = -\frac{R_2}{R_1}$$


Q: input impedance?

A:  $R_{in,CL} \equiv \frac{v_{in}}{i_{in}}$ ;  $i_{in} = \frac{v_{in} - 0V}{R_1}$  (virt. ground)  $\Rightarrow R_{in,CL} = R_1$

Q: output impedance?

$\Rightarrow$  HW problem (it's small)

### ④ summing circuit

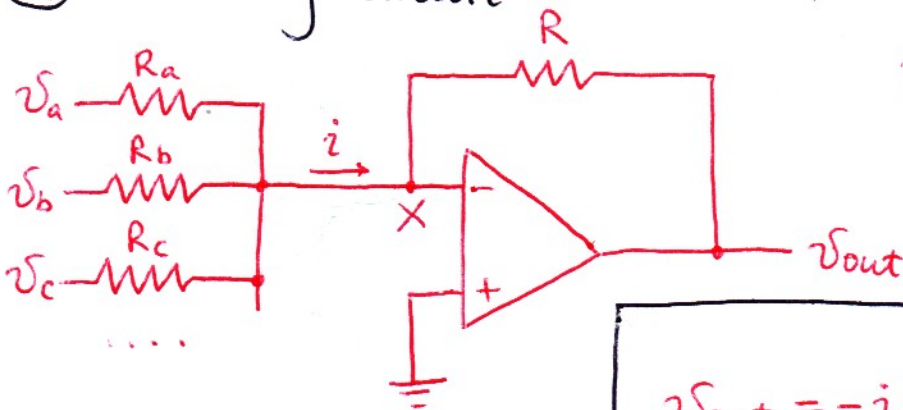

"X" - virtual ground

$$i = i_a + i_b + i_c + \dots$$


$$= \frac{v_a}{R_a} + \frac{v_b}{R_b} + \frac{v_c}{R_c} + \dots$$

$$v_{out} = -iR = -R \left( \frac{v_a}{R_a} + \frac{v_b}{R_b} + \dots \right)$$


Q: How to add without inversion (i.e. w/o "-" sign)?

(4)

A1: add another inverter at the end

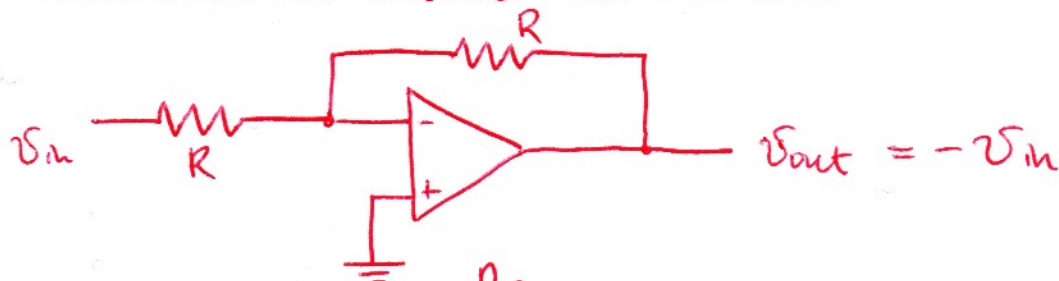

A2:

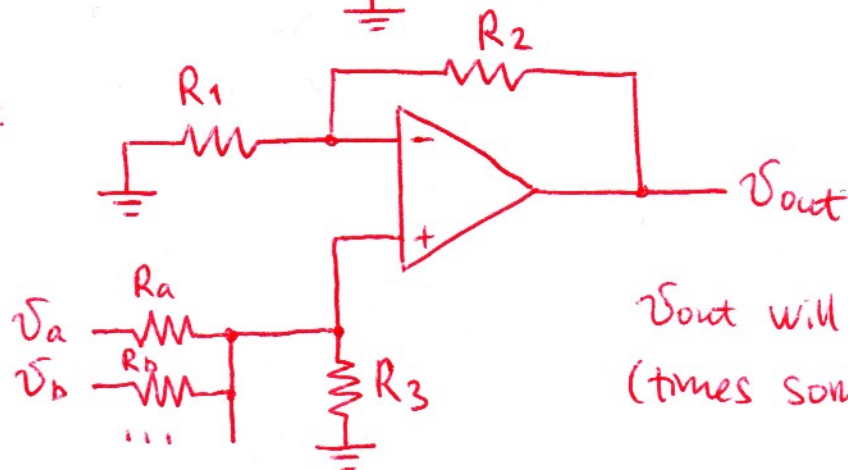

$V_{out}$  will be sum of  $V_a, V_b, \dots$   
(times some coeff.) w/o inversion.

## Active filters (next lecture)

Feedback network contains  $Z(\omega)$  (RLC-network)

Pros:

- gain can be  $> 1$
- $Z_{out}$  can be made very low
- can design high Q filters without inductors  
(i.e. bulky coils) HW

Cons:

- can go unstable

Q: ideal integrator & differentiator: poles & zeros of  $G(s)$ ?

A: pole @ origin      zero @ origin      (more next time)