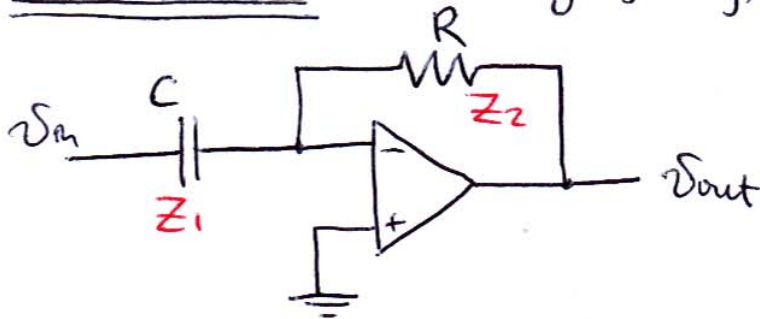


Example 1: stability of differentiator



Unstable if $\underbrace{GH = -1}$
appr. loop gain

$$\text{Here } H = \frac{Z_1}{Z_2 + Z_1} = \frac{1}{1 + j\omega RC}; \quad G = \frac{G_0}{1 + j\omega/\omega_0} \xrightarrow{\omega \gg \omega_0} \frac{G_0 \omega_0}{j\omega}$$

↑ bare op-amp


$$\Rightarrow GH \approx \frac{1}{j\omega RC} \frac{G_0 \omega_0}{j\omega} = -\frac{G_0 \omega_0}{\omega^2 RC} \quad \omega \gg (RC)^{-1}$$

We see that GH is headed to hit $GH = -1$ condition at


$$\omega = \sqrt{\frac{G_0 \omega_0}{RC}} \leftarrow \text{freq. of expected "ringing" on the output}$$

N.B.: check with measured behaviour in the lab.

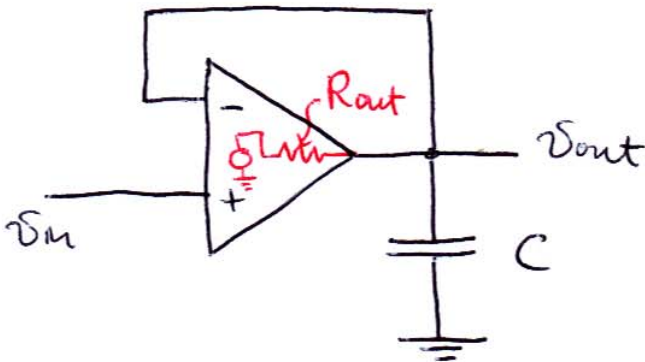Example 2 stability of voltage follower driving C




Rearrange circuit so that it looks as

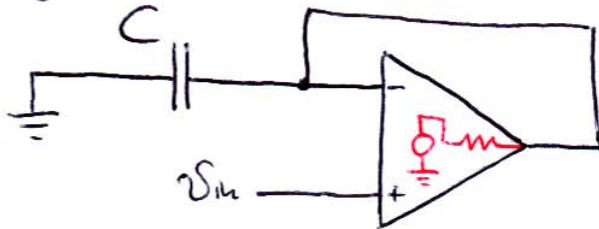

The loop gain is, $GH = \frac{G_o}{1+j\omega/\omega_o} \frac{Z_c}{Z_c+R_{out}}$

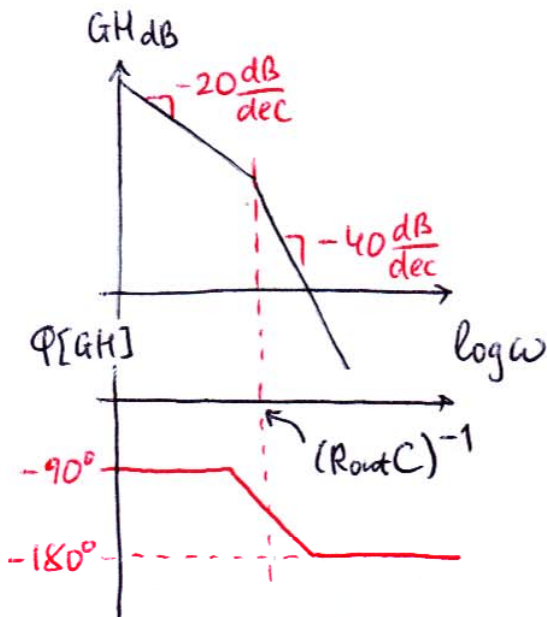for $\omega \gg \omega_o$ $GH \approx \frac{G_o \omega_o}{j\omega} \frac{1}{1+j\omega R_{out} C}$



$\phi[GH]$ hits -180° eventually.

The question is whether $|GH| \geq 1$ when that happens.

If $\omega_{cl} = \frac{1}{R_{out} C}$ is sufficiently large

$(C \ll \frac{1}{R_{out} G_o \omega_o})$, the circuit is stable.

E.g. $C \ll 100\text{pF}$ for 741