

Lecture 14

Diode Applications (contd.)





① rectifiers

recall filter capacitor

ripple: $\frac{dV}{dt} = \frac{I}{C}$, $\frac{\Delta V_{out}}{T} = \frac{I_{LOAD}}{C} \Rightarrow \Delta V_{out} = \frac{I_{LOAD}}{C} \frac{1}{f}$
3
60Hz

full wave rectifier

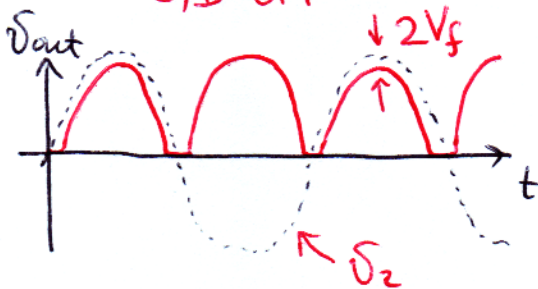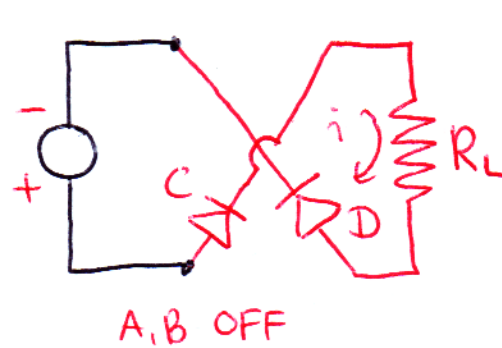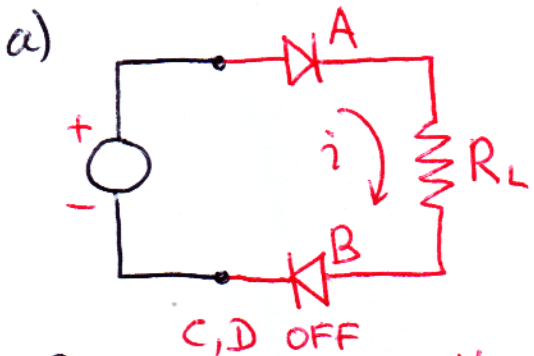
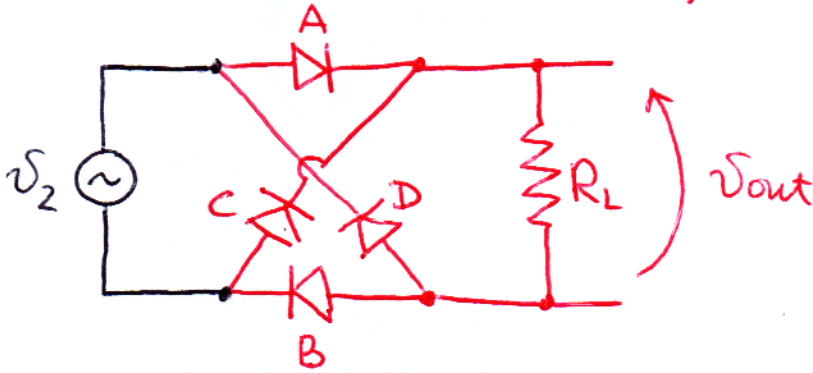
half-wave rect. wastes $\frac{1}{2}$ volt. cycles



- PROS:
- full wave used
 - ripple freq 120Hz (smaller ripple)


② Zener voltage reference

②

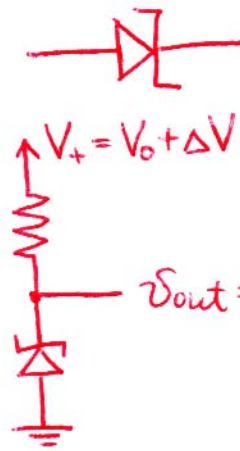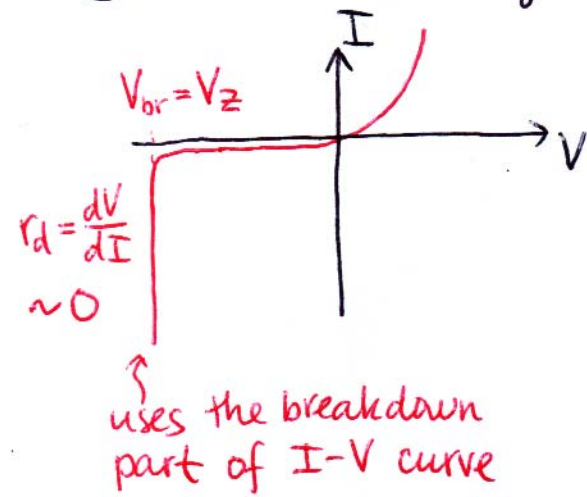

Zener diode symbol



$V_Z \sim 2-200V$ (buy)

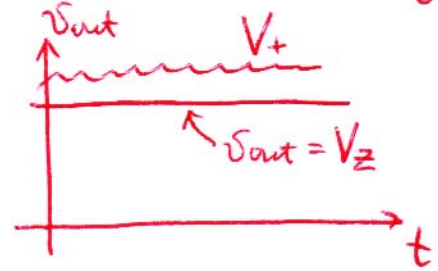

③ Clipping circuit (limiter or clamper)



$V_{out} < V_b + V_f$, \Rightarrow D is OFF
 $\Rightarrow V_{out} = V_{in}$

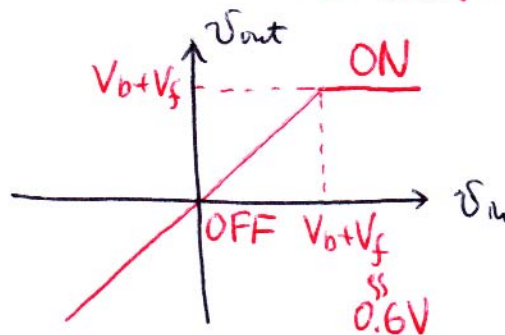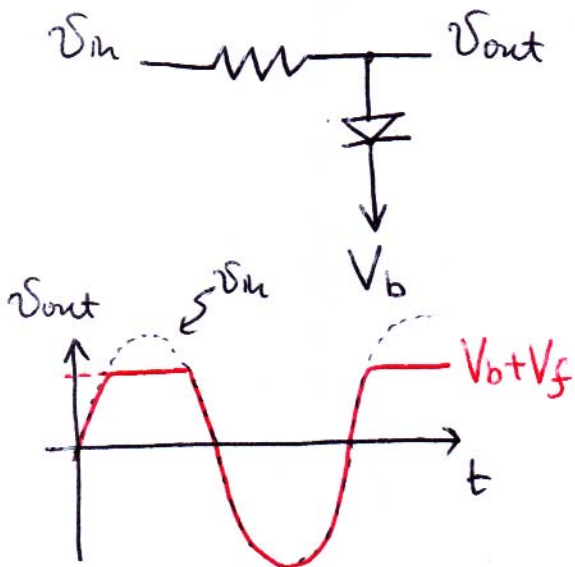
$V_{out} \geq V_b + V_f$, \Rightarrow D is ON
 $\Rightarrow V_{out} \approx V_b + V_f$



- e.g. use in IC overvoltage protection


④ Pickoff circuit

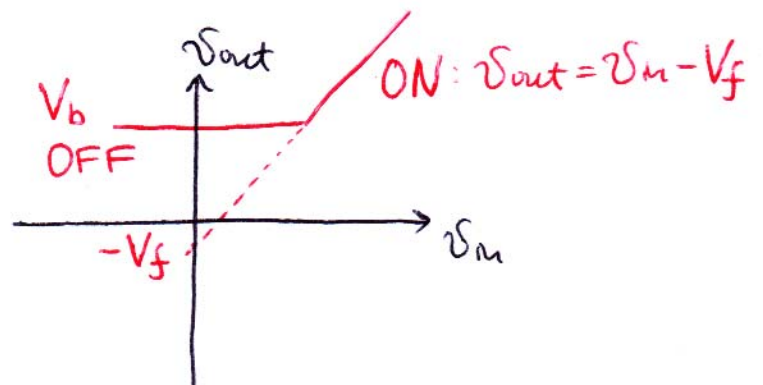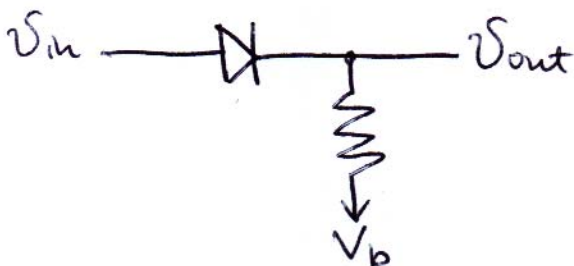

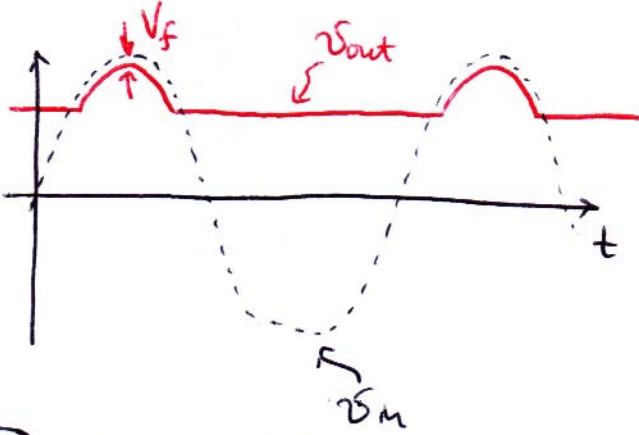

- e.g. set signal threshold ⁽³⁾

⑤ Voltage doubler

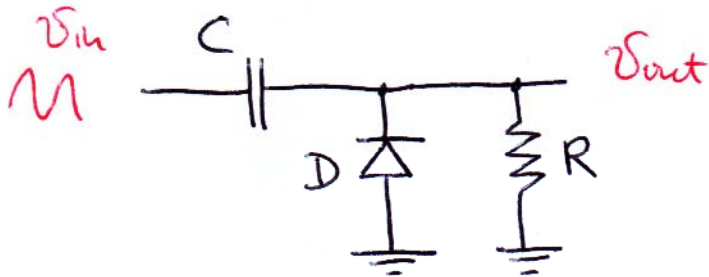

let $\frac{1}{2\pi RC} \ll f$

$v_m - v_c < -V_f \Rightarrow$ D is ON, R_D is small

v_c time const $\sim R_D C \ll RC$

$v_{out} \sim -V_f$ (0.6V)

$v_c = v_m + V_f$


$v_m - v_c > -V_f \Rightarrow$ D is OFF, R_D is large

v_c time const $RC \gg \frac{2\pi}{f}$

v_c stays const

$v_{out} = v_m - v_c$


const & negative

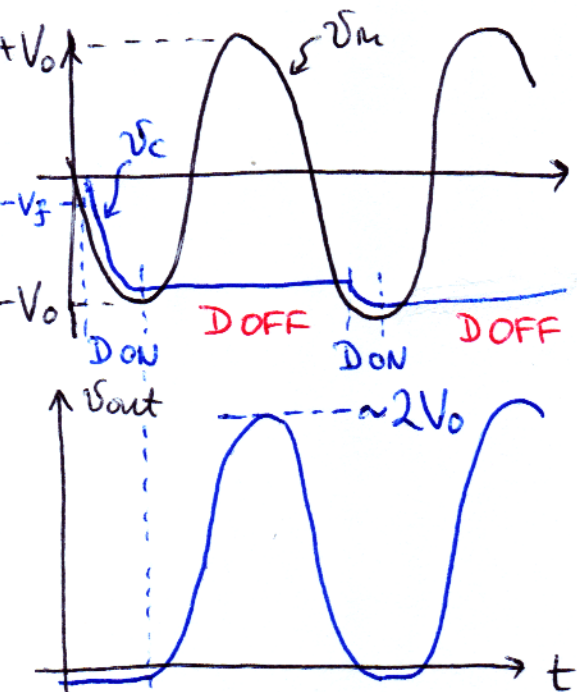


HW: Walton Cockraft generator
 ~ 1.5 MV proton accelerator
 $p + Li \rightarrow He + \dots$

⑥ DC restoration circuit (same circuit, different way to look at it)

④

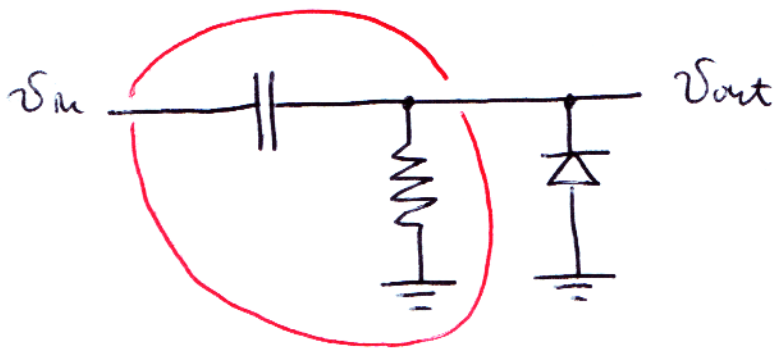

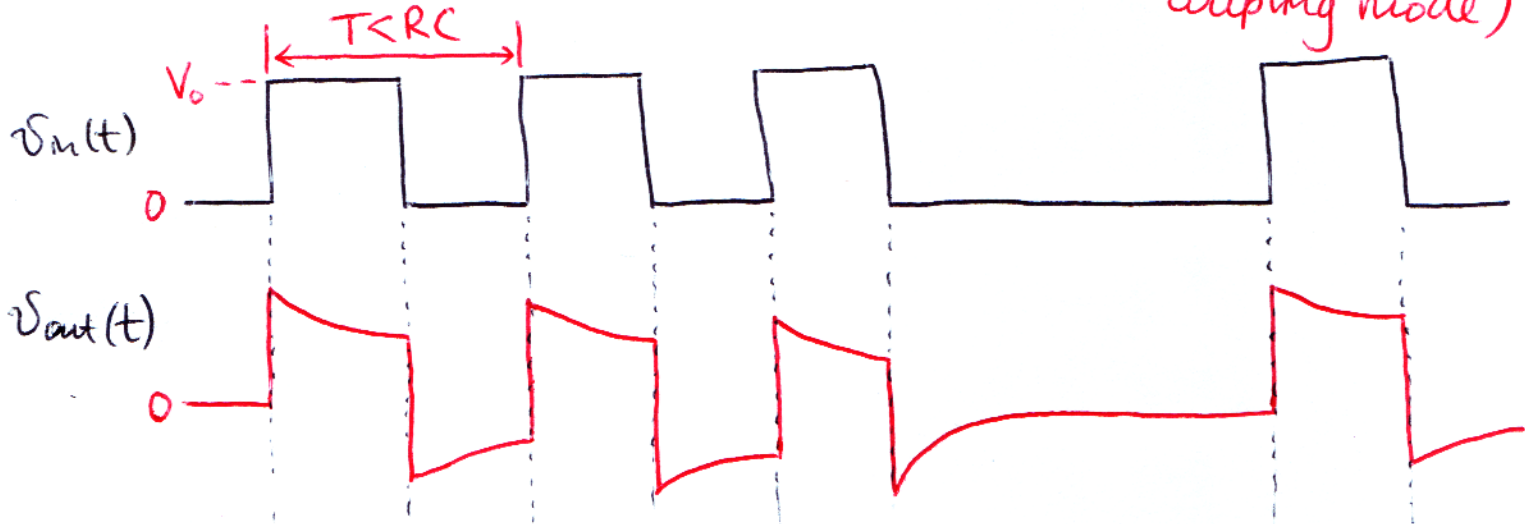RC form HP filter: C blocks DC of v_{in} (e.g. scope's AC coupling mode)



Problem: if pulse separation varies in time, DC level of output changes

Soln:



- RC const for " - "ve part of the waveform much shorter than for " + " part b/c D is ON