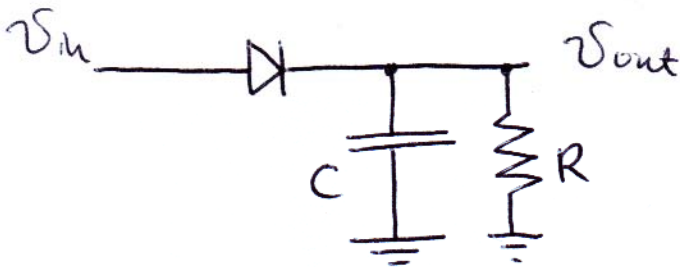


Lecture 15

Diode applications (contd.)

Last talked about DC restoration

⑦ Pulse stretcher




$V_{in} > V_{out} + V_f$  : D is ON

cap is charging up quickly

$V_{out} = V_{in} - V_f$


$V_{in} < V_{out} + V_f$  : D is OFF

the cap. discharges into R

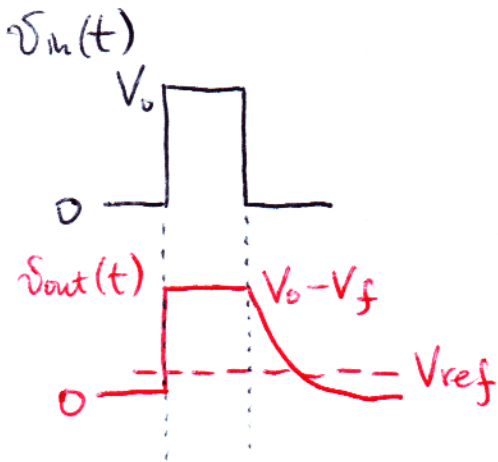

- e.g. use a comparator to generate a longer square pulse

⑧ Log amplifier

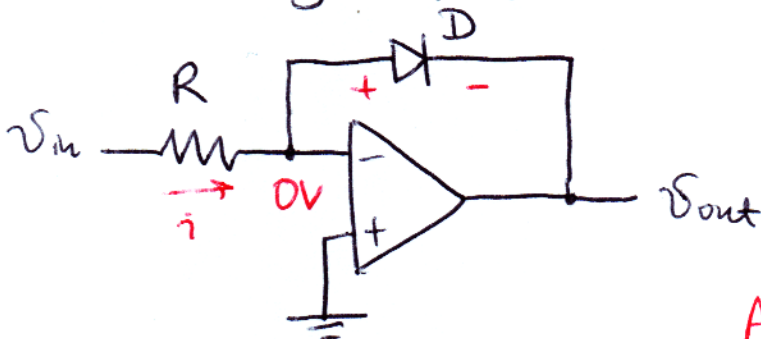

- if diode is a part of feedback network => "operational configuration"

Approx. model is no good here!

$$i = \frac{v_{in}}{R} ; v_{out} = -v_D ; i = I_0 e^{\frac{v_D}{V_T^*}} \text{ or } \quad (2)$$


$$v_D = V_T^* \ln \frac{i}{I_0}$$

$$\Rightarrow v_{out} = -V_T^* \ln \frac{v_{in}}{R I_0}$$


- use to transport large dynamic range signal  
"companding"

- use to multiply (divide), e.g.  $\ln A \cdot B = \ln A + \ln B$

### ⑨ Anti-log amplifier

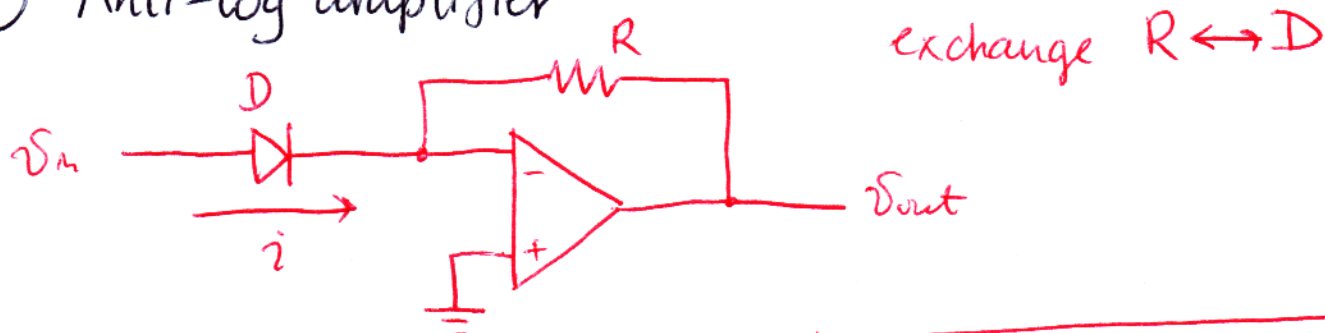
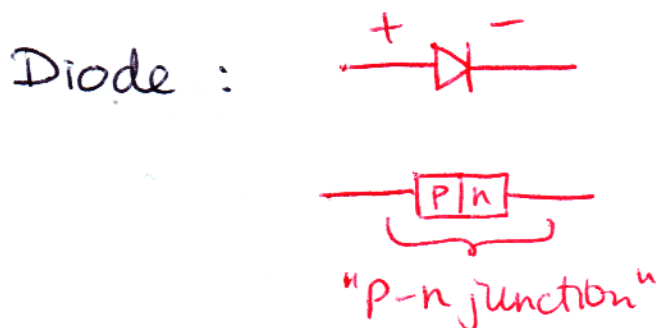
$$v_D = v_{in}, i \approx I_0 e^{\frac{v_{in}}{V_T^*}}, v_{out} = -iR = -I_0 R e^{\frac{v_{in}}{V_T^*}}$$



positive carriers } thru  
negative carriers } dopants  
added to  
Si

Transistor :


- 3 terminal nonlinear device
- response between 2 terminals is modified by input supplied to the 3rd.

# Bipolar junction transistor (BJT)



③

back-to-back pn junctions fabricated in a single semiconductor crystal


2 types

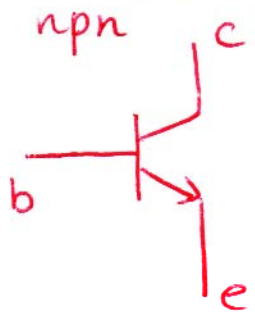

2N3904

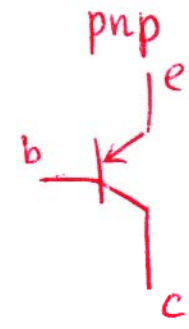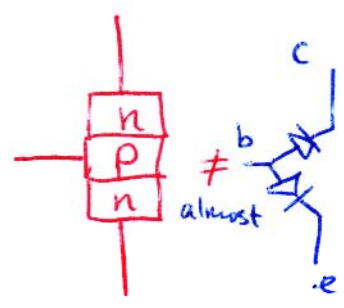

2N3906

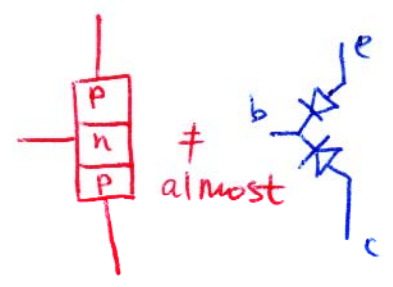

b = base      e = emitter      c = collector


arrow on emitter : direction of current flow when b-e junction is forward biased

nnp ↔ pnp if all voltages and currents reversed  
will only discuss npn

npn

normal operation

$$V_{ce} \gg V_{be} \approx 0.6V$$

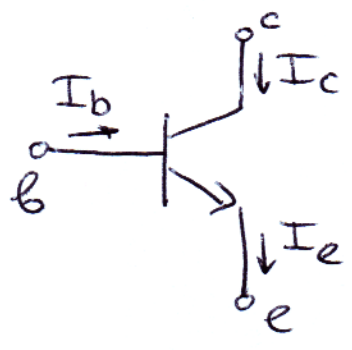

b-e junction is forward biased  
 $V_b - V_e \approx V_D$  (used to be called  $V_f \sim 0.6V$ )

b-c junction is reversed biased  
 $V_b - V_c \approx V_D$

KCL :  $I_e = I_b + I_c$

For diode "analog" such biasing would result in


$I_c \sim 0, I_e \approx I_b, \Rightarrow \frac{I_c}{I_e} \approx 0$

But in transistor  $\frac{I_c}{I_e} \equiv \alpha \sim 1$  (slightly less than 1)

$I_e = \frac{I_c}{\alpha} = I_b + I_c, \frac{I_c}{I_b} \equiv \beta = \frac{\alpha}{\alpha - 1} \gg 1$

$\frac{I_e}{I_b} = 1 + \beta$

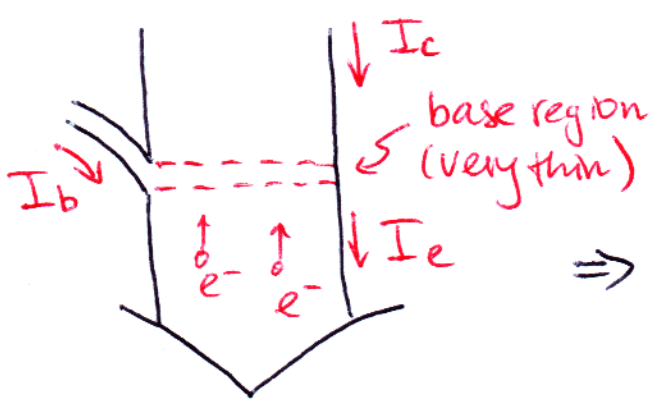Typical values:  $\alpha \sim 0.99 ; \beta \sim 100$



Large  $I_c$  is controlled by small  $I_b$

$\Rightarrow$  transistor in normal operation behaves as current controlled current source

base region is so thin that  $e^-$ 's reaching it are swept into collector without reaching the base

N.B. transistor not symmetric with respect to e and c e.g. circuits with e, c exchanged

