

P3360/AEP 3630


①

Lecture 16



Transistors (BJT's)

3 terminals

input characteristics

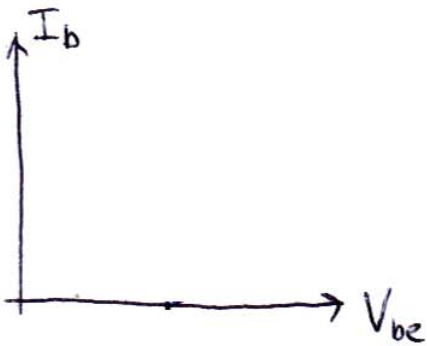

output

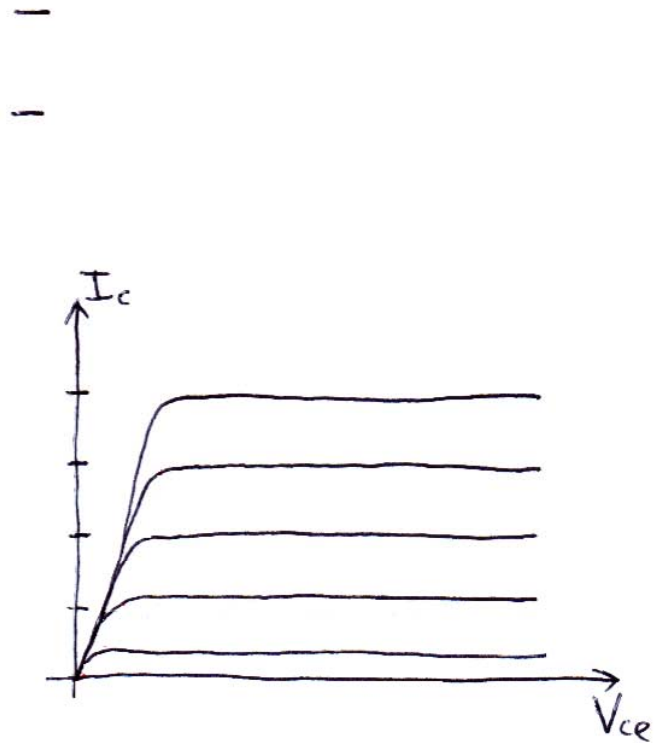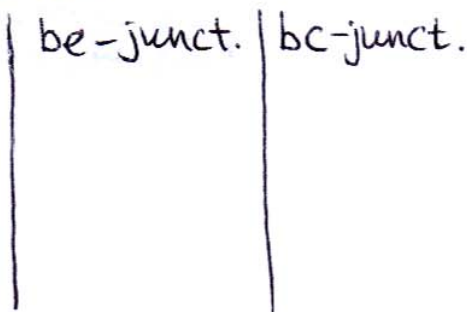

I cutoff

②

II active


III saturation

Important notes:


$\beta -$

# Transistor circuits


③

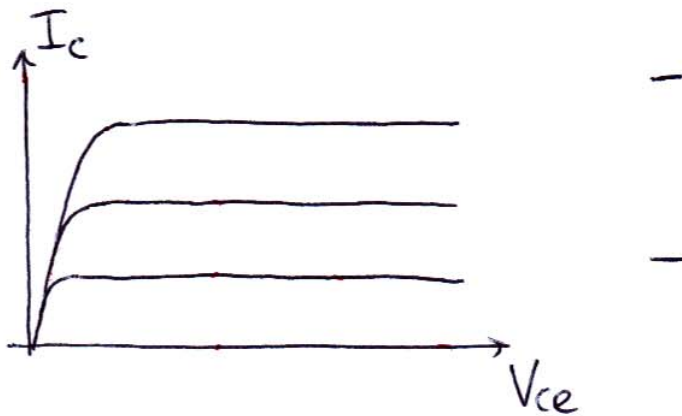



Transistor switch

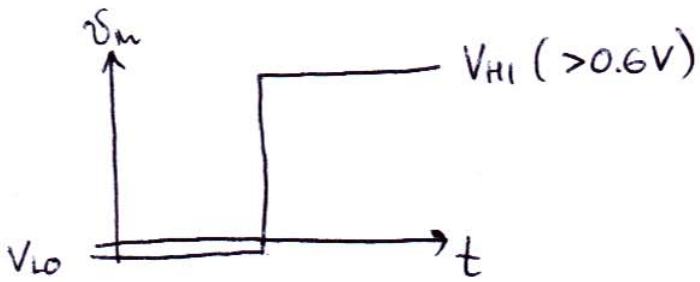

Important :

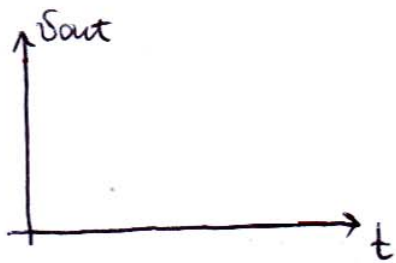


## Lecture 17

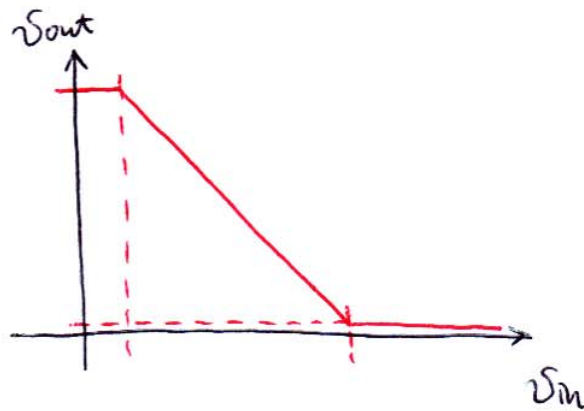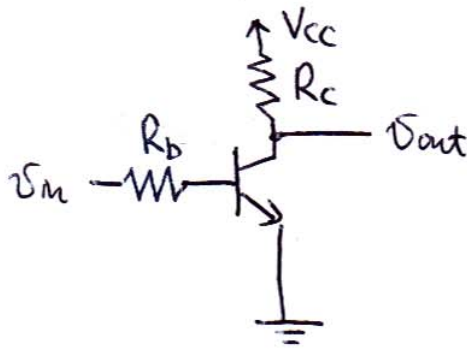Transistor circuits (contd)Transistor amplifier

suppose  $i_b = I_{b0} + i_{b1} \sin \omega t$

②

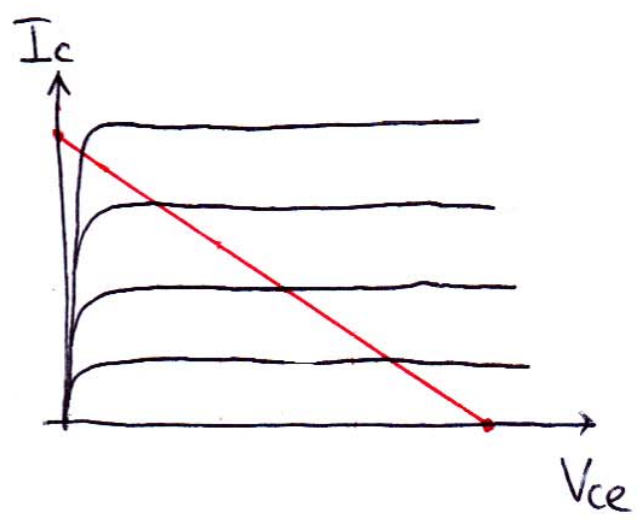


—  
—

Transistor biasing

=

simple

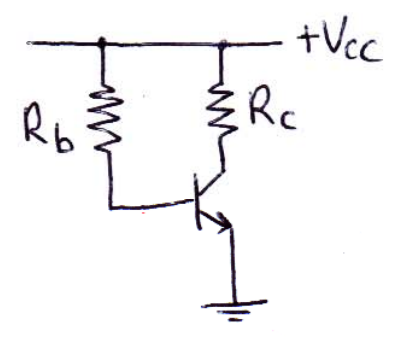

Problem:


Solution:

H-biasing


Transistor small signal equivalent

Recall  $I_b = f(V_{be})$

④

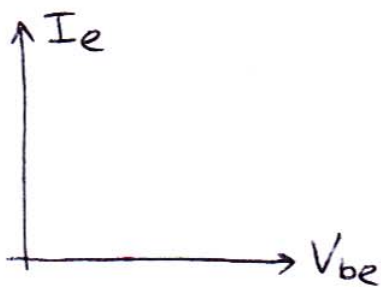

equivalent circuit

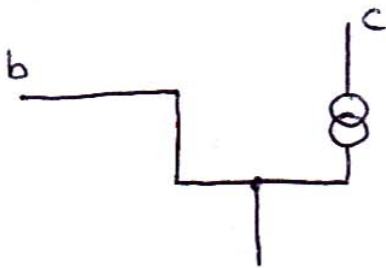

### Transistor circuit analysis

usually  $\left| \frac{\Delta V}{V_{ce}} \right| \ll 1$ , then analysis can be separated

1)

2)



P3360 / AEP 3630


①

Lecture 18

Transistor analysis

Two parts

①

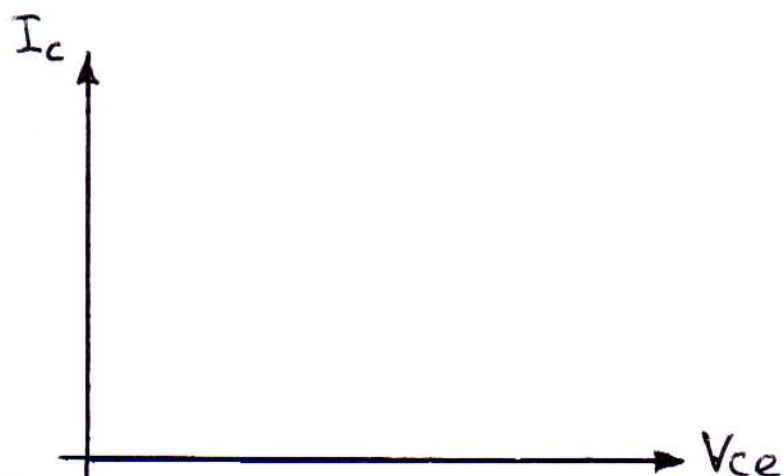


②

②

-  
-  
-

Example: large signal analysis

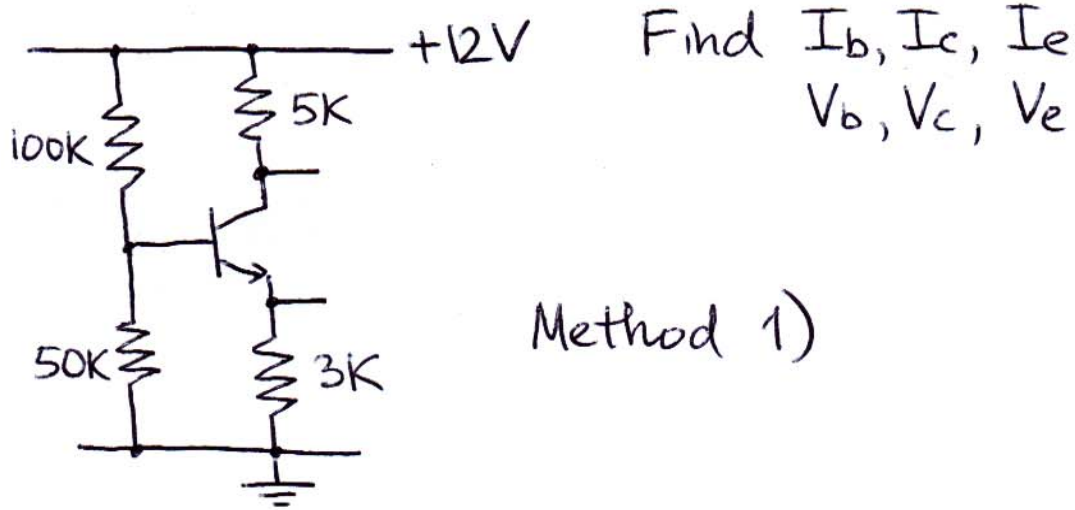

Method 1)

Method 2)

# PHYS3360/AEP3630


## Four Basic Transistor Amplifier Configurations

The four basic single transistor amplifier configurations are as following: common collector (CC), common base (CB), common emitter (CE), and unbypassed emitter resistor variant of CE amplifier (UBER). These provide basic building blocks that can be combined to obtain the needed input and output characteristics (gain,  $R_{in}$ ,  $R_{out}$ ). The following table summarizes the properties of the four basic configurations of the transistor amplifiers.

Configuration	$G$	$R_{in}$	$R_{out}$
CC	$\sim 1$	large	small
CB	large, non-inverting	small	moderate
CE	large, inverting	moderate	moderate
UBER	moderate, inverting	large	moderate
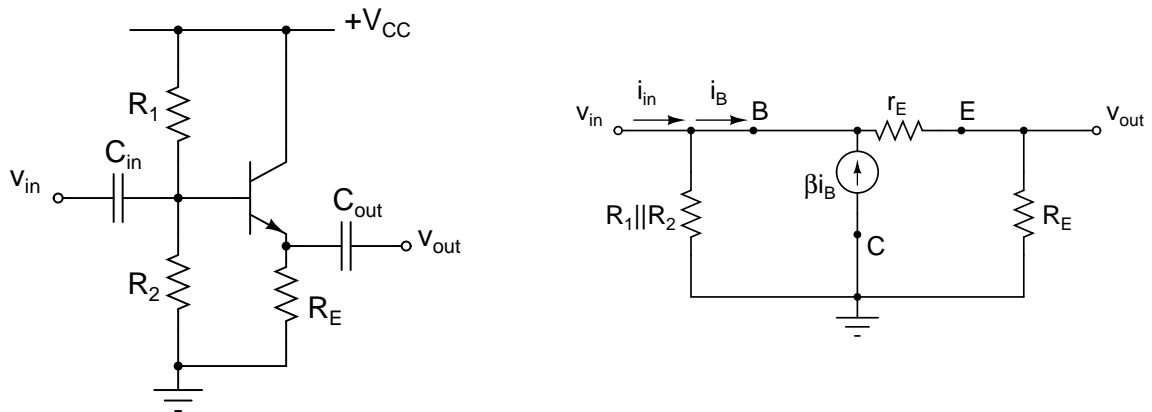
### Common Collector Amplifier (Emitter Follower)

The circuit is shown on the left, and its small-signal equivalent is on the right. Here, and in other circuits capacitors are chosen such that their impedances are sufficiently small for input frequencies of interest that they can be ignored in small-signal equivalent circuits.



From the small-signal equivalent circuit we find that  $v_{out} = i_E R_E = i_B (\beta + 1) R_E$ , and  $v_{in} = i_E (r_E + R_E) = i_B (\beta + 1) (r_E + R_E)$ . Thus, the voltage gain is

$$G = \frac{v_{out}}{v_{in}} = \frac{R_E}{R_E + r_E} \approx 1.$$

Input resistance is given by  $R_{in} = (R_1 || R_2) || R'_{in}$ , where the parallel to  $(R_1 || R_2)$  resistance  $R'_{in} = v_{in} / i_B = (\beta + 1) (r_E + R_E)$ . Thus,

$$R_{in} = R_1 || R_2 || (\beta + 1) (r_E + R_E).$$


Output resistance is given by  $R_{out} = v_{oc} / i_{sc}$ , where  $v_{oc}$  is the open-circuit voltage across the output terminal and the ground  $v_{oc} = v_{out} = v_{in} R_E / (r_E + R_E)$ , and  $i_{sc}$  is a short-circuit current, which is simply  $i_{sc} = v_{in} / r_E$ . Thus,

$$R_{out} = r_E || R_E.$$

We note that  $R_{in}$  can be made quite large, while  $R_{out}$  is small ( $< r_E$ ).
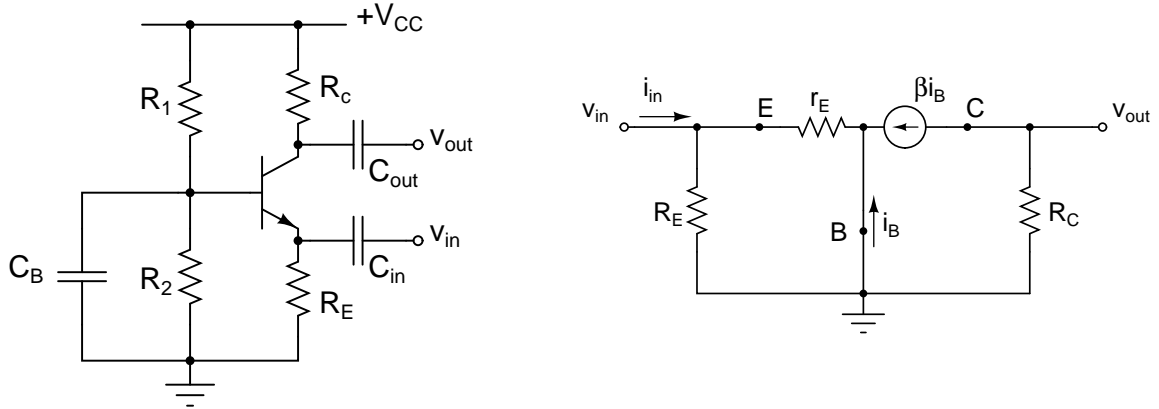
## Common Base Amplifier

The circuit is shown on the left, and its small-signal equivalent circuit is shown on the right.



We write for the output  $v_{out} = -i_C R_C = -\beta i_B R_C$ . The input  $v_{in} = -i_E r_E = -(\beta + 1) i_B r_E$ . The resultant gain

$$G = \frac{\beta}{\beta + 1} \frac{R_C}{r_E} \approx \frac{R_C}{r_E}.$$


We can write immediately for input and output resistances:

$$R_{in} = r_E || R_E, \text{ and } R_{out} = R_C.$$

We see that  $R_{in}$  is necessarily small ( $< r_E$ ), and that the gain can be made large.
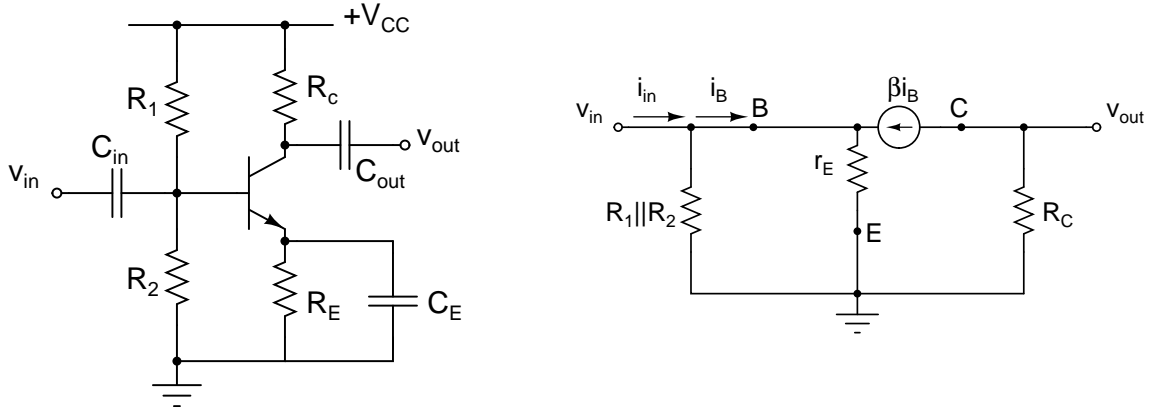
## Common Emitter Amplifier

The circuit is shown on the left, and its small-signal equivalent circuit is shown on the right.



$v_{out} = -i_C R_C = -\beta i_B R_C$  and  $v_{in} = i_E r_E = (\beta + 1) i_B r_E$ . The resultant gain

$$G = -\frac{\beta}{\beta + 1} \frac{R_C}{r_E} \approx -\frac{R_C}{r_E}.$$


The input and output resistances are given by:

$$R_{in} = R_1 || R_2 || (\beta + 1) r_E, \text{ and } R_{out} = R_C.$$

Note: the gain is similar to the CB amplifier except CE amplifier is inverting.
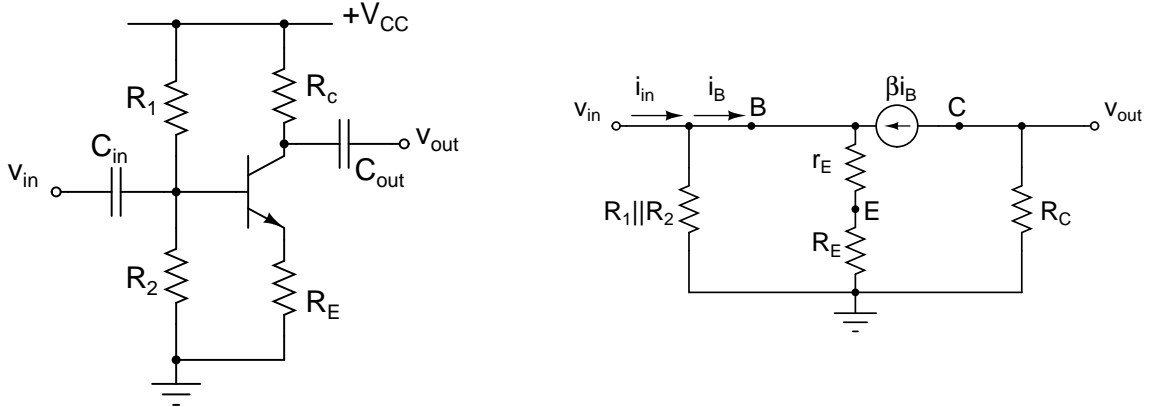
# Upbypassed Emitter Resistor Amplifier

The circuit is shown on the left, and its small-signal equivalent circuit is shown on the right. Note: this is equivalent to CE amplifier except for  $R_E$  present in small-signal equivalent circuit.



$v_{out} = -i_C R_C = -\beta i_B R_C$  and  $v_{in} = i_E (r_E + R_E) = (\beta + 1) i_B (r_E + R_E)$ . The resultant gain

$$G = -\frac{\beta}{\beta + 1} \frac{R_C}{r_E + R_E} \approx -\frac{R_C}{R_E}$$


The input and output resistances are given by:

$$R_{in} = R_1 || R_2 || (\beta + 1)(r_E + R_E), \text{ and } R_{out} = R_C.$$
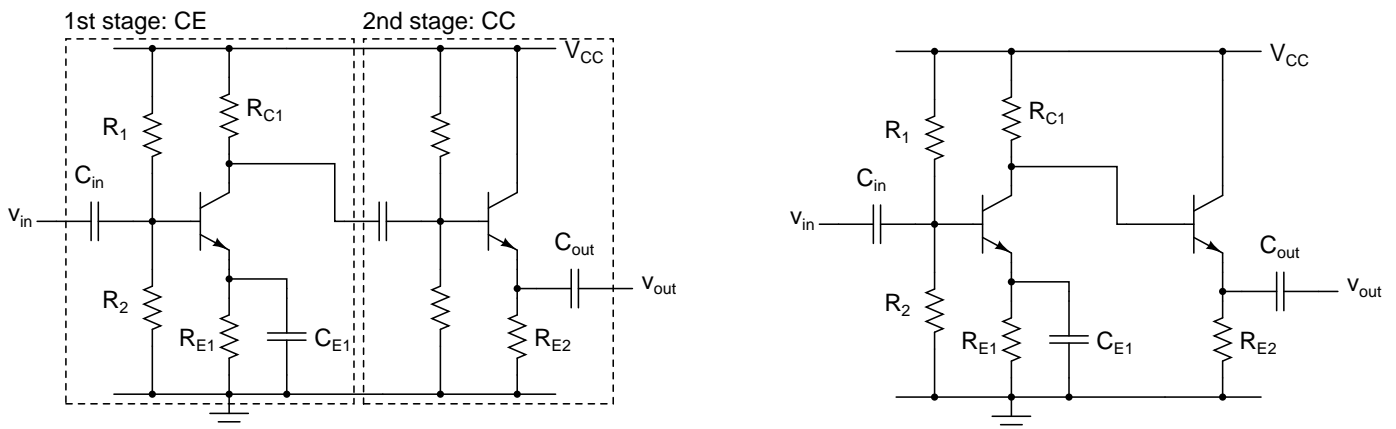
## Combining Multiple Stages


Oftentimes, no single configuration of the four basic types is sufficient to meet a particular application's requirement in terms of the desired gain, input, and output impedances.

Suppose you would like to have a high  $G$  low  $R_{out}$  amplifier. One can achieve so by combining common emitter and common collector configurations. To connect the two stages, each biased using H-configuration, one can insert a capacitor between them so that the output of the first stage is transferred to the second stage without affecting biasing in each stage (see the circuit on the left). Generally, such an approach is less than ideal because the addition of intermediate capacitors degrades amplifier frequency response and requires more components. Instead, one can directly couple the stages as shown in the schematic below to the right. In this case the collector of the first stage is connected directly to the base of the second stage. Provided  $I_{B2} \ll I_{C1}$ , biasing of the first stage will be unaffected by the second stage.


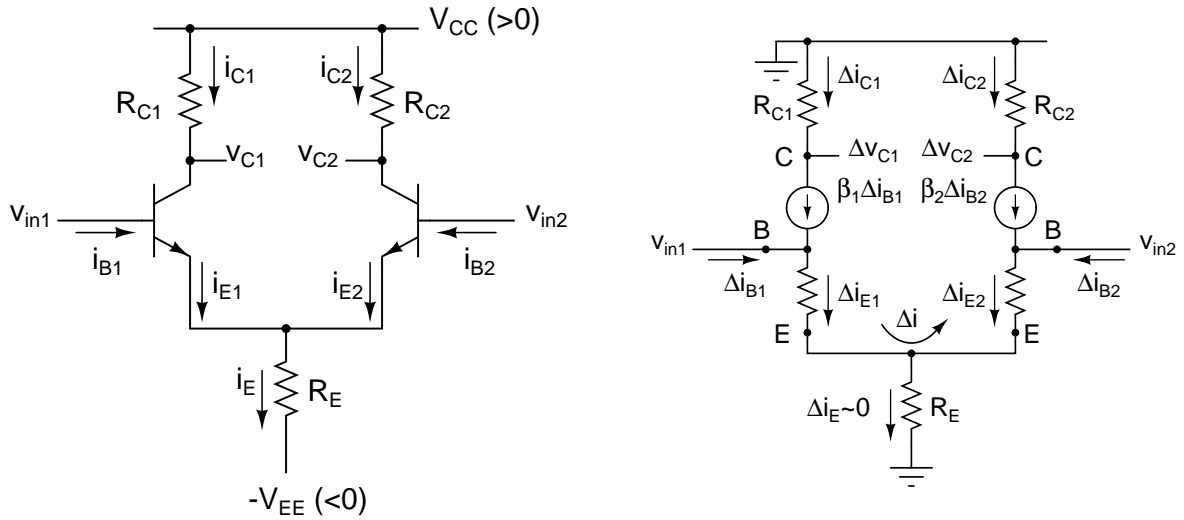
## Difference Amplifier

This circuit is also known as an emitter-coupled pair. See the circuit and its small-signal equivalent below. Two small voltage inputs are supplied to bases of the two transistors. The circuit has two outputs,  $v_{C1}$  and  $v_{C2}$ .



The power supply voltage  $V_{EE}$  is chosen to be large enough so that the emitter voltages fluctuations due to  $v_{in1}$  and  $v_{in2}$  do not change the current flowing through  $R_E$  resistor. That current, which is roughly  $(V_{EE} - 0.6V)/R_E$  assuming  $v_{in1}$  and  $v_{in2}$  are small signals, is to a very high degree independent of the input voltages.

Next, we proceed to the small-signal circuit analysis.  $R_E \gg r_{E1,E2}$ , so little of the small signal current that flows between the two inputs through  $r_E$ 's gets diverted to  $R_E$ . We can imagine replacing  $R_E$  by an open circuit (the small-signal part of  $i_E$ ,  $\Delta i_E$ , is much less than  $\Delta i_{E1}$ ,  $\Delta i_{E2}$ , etc.) and then writing the *small-signal current* circulating in the loop formed by the transistors

$$\Delta i = \Delta i_{E1} = -\Delta i_{E2} \approx \Delta i_{C1} = -\Delta i_{C2} = \frac{v_{in1} - v_{in2}}{r_{E1} + r_{E2}} = \frac{v_{diff}}{r_{E1} + r_{E2}}$$

The output voltage could be taken from either transistor's collector, providing both inverting and non-inverting outputs.

$$\Delta v_{C1} = -\Delta i R_{C1} = -\frac{R_{C1}}{r_{E1} + r_{E2}} v_{diff}$$

$$\Delta v_{C2} = \Delta i R_{C2} = \frac{R_{C2}}{r_{E1} + r_{E2}} v_{diff}$$

The ratio in front of  $v_{diff}$  defines differential gain, which can be made very large. The actual value is determined by specific  $r_E$ 's, which are in turn determined by the Q points of each of the transistors. It is possible to include additional external emitter resistors to make the gains independent from  $r_{E1,E2}$ . A circuit similar to this one is used as an input stage for op-amps such as 741.