
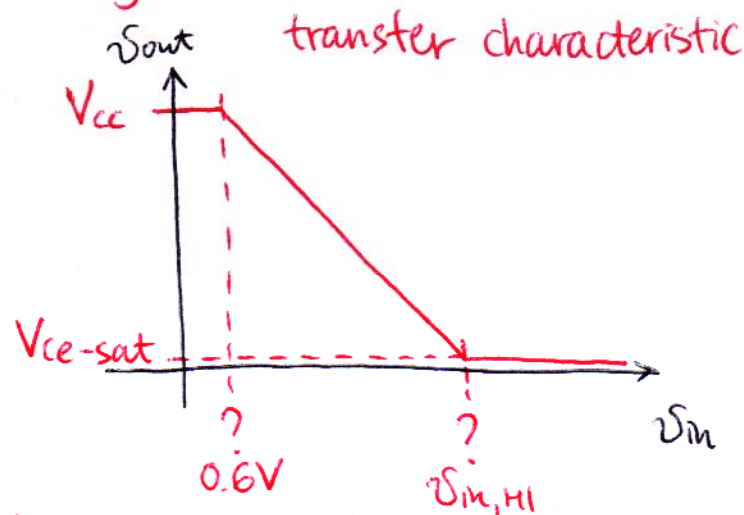


Lecture 17

Transistor circuits (contd)

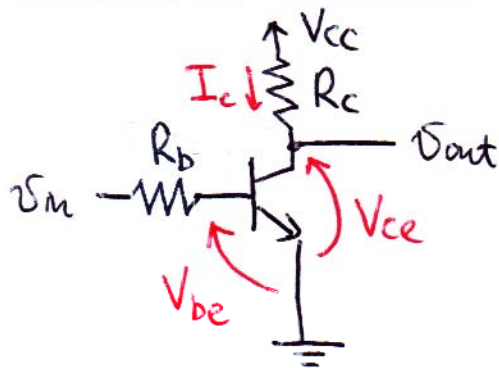Recall: we are looking @ common emitter config.



$v_{in,HI}$: point where transistor goes from active to saturation, i.e. $\beta \cdot I_b = (I_c)_{max}$

$$\beta \frac{v_{in,HI} - 0.6V}{R_b} = \frac{V_{cc} - V_{ce-sat}}{R_c}$$






$$\Rightarrow v_{in,HI} \approx 0.6V + \frac{V_{cc}}{\beta} \frac{R_b}{R_c}$$

Transistor amplifier

suppose $i_b = \underbrace{I_{b0}}_{\text{bias}} + \underbrace{i_{b1} \sin \omega t}_{\text{signal}}$

Q: what about $v_{out} = V_{ce}$?

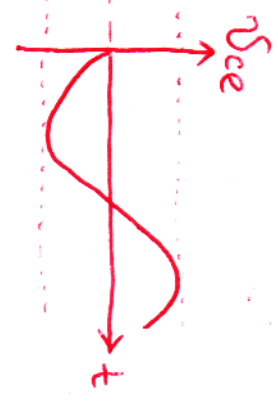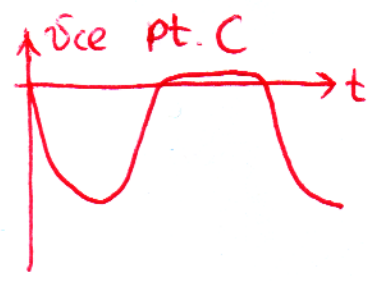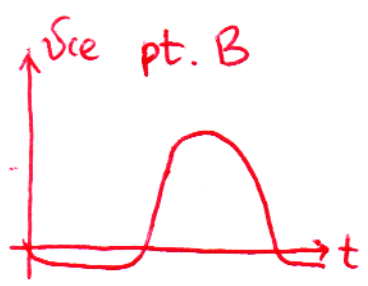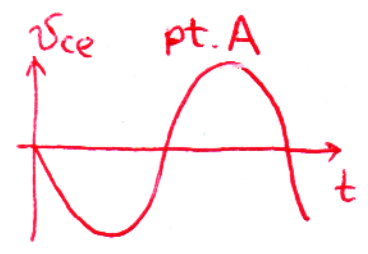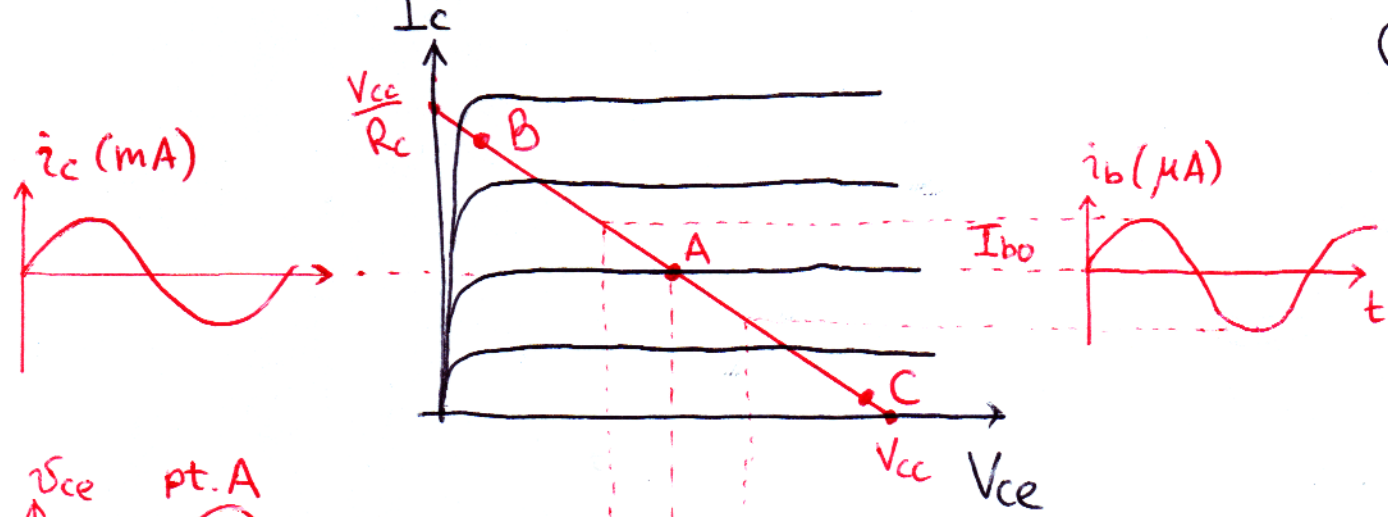A: constrained to lie on "load line" + I_c



- pts. B & C distort the signal
- choose Q-pt so that max input swing produces output with no distortion


Transistor biasing

= setting Q-pt (DC values I_b, I_c, V_{ce})

simple-minded approach: fix I_b

$(I_c)_{min} \sim 0$
 $(I_c)_{max} \sim \frac{V_{cc}}{R_c}$

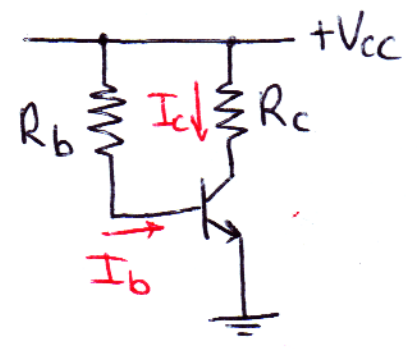} set Q-pt in the middle $I_c \sim \frac{1}{2} \frac{V_{cc}}{R_c}$



$$\Rightarrow I_b = \frac{I_c}{\beta} = \frac{1}{2\beta} \frac{V_{cc}}{R_c}, \text{ or choose } R_b = \frac{V_{cc} - 0.6V}{I_b} \quad (3)$$


$$I_b \approx \frac{1}{2\beta} \frac{V_{cc}}{R_c}$$

R_b fixes I_b , which fixes I_c & V_{ce} .

Problem: Q-pt sensitive to β ! E.g. $\beta(T=80^\circ C) \sim 2\beta(T=20^\circ C)$
 $\Rightarrow I_c(80^\circ C) = 2I_c(20^\circ C) = (I_c)_{sat}$!

Solution: fix I_c (I_e) instead of I_b

H-biasing

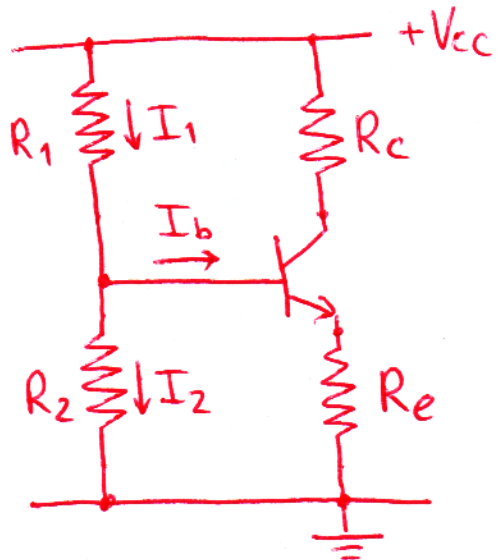

In active range $V_e = V_b - 0.6V$

$$\text{and } I_e = \frac{V_e}{R_e} = \frac{V_b - 0.6V}{R_e}$$

Fix V_b : this fixes V_e and I_e

$$I_b \ll I_1, I_2 \text{ (e.g. } I_1 \approx I_2 \approx 10I_b)$$

$$\text{volt. divider } (V_b)_Q = \frac{R_2}{R_1 + R_2} V_{cc}$$

R_e provides negative feedback stabiliz. I_e against var. in β

Let $\beta \uparrow$, then $I_e = (\beta + 1)I_b \uparrow$ and $V_e = R_e I_e \uparrow$. Since


V_b is held const, $V_{be} = V_b - V_e \downarrow$. $I_b(V_{be}) = \text{diode eqn}$, so

$V_{be} \downarrow$ brings down I_b , and $I_b \downarrow$ produces $I_e \downarrow$

Transistor small signal equivalent

Recall $I_b = f(V_{be})$ diode eqn; $I_e \approx I_b(\beta + 1) = f'(V_{be})$ ^{diode eqn.}
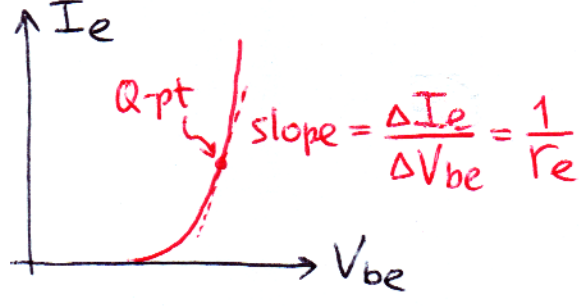
$$I_e \approx I_o e^{\frac{V_{be}}{V_T^*}}$$




For small signals only

$$r_e = \left(\frac{\partial I_e}{\partial V_{be}} \right)^{-1} = \left(\frac{I_o}{V_T^*} e^{\frac{V_{be}}{V_T^*}} \right)^{-1} = \frac{V_T^*}{I_e} \approx \frac{V_T^*}{I_c}$$

e.g. if $I_e \approx 4\text{mA}$, \Rightarrow
 $r_e \approx \frac{40\text{mV}}{4\text{mA}} = 10\Omega$ (small)

equivalent circuit (Q=active)

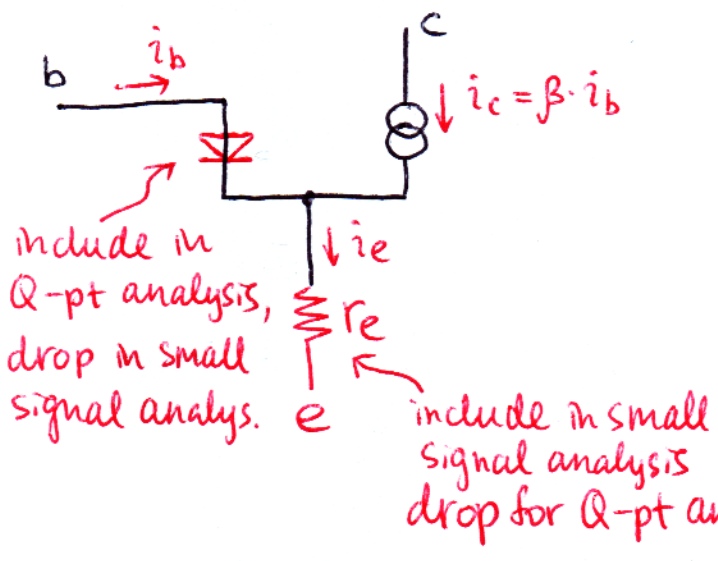

- dynamic small-signal r_e inside the transistor
- ignore r_e for Q-pt analysis

Transistor circuit analysis (amplifiers)

usually $\left| \frac{\Delta V}{V_{ce}} \right| \ll 1$, then analysis can be separated into two simpler parts (~indep.)

- 1) Set $\Delta V_{in} = v_{in} = 0$. Solve for DC to find I_{Q} 's & V_{Q} 's (transistor should be active if amplifier) non-linear
- 2) Add small $v_{in} \neq 0$. I_{Q} 's & V_{Q} 's remain the same. Set DC values to zero. Treat small signals as pert.
 Superposition works for linearized circuits
 $r_e = r_e(Q_{pt})$ $v_{tot} = V_Q + v_{ss}$