



Computer Modeling of Electronic Circuits with LTSPICE

PHYS3360/AEP3630

Lecture 20/21


SPICE

Simulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis

- Originally developed at EE Berkeley
- Uses mathematical models to describe circuit elements
- **SPICE3** is the latest variant.
 - It allows **DC and time transient analysis of nonlinear circuits** (transistors, diodes, capacitors, etc., also digital circuitry)
 - **Command line** driven interface
 - Available in **public domain** (written in C)
 - Has become de-facto the **industry standard**
 - **Many spin-offs** exist (use modified SPICE2 or SPICE3 as their engine), such as HSPICE, PSPICE, WinSPICE (commercial)

Netlist

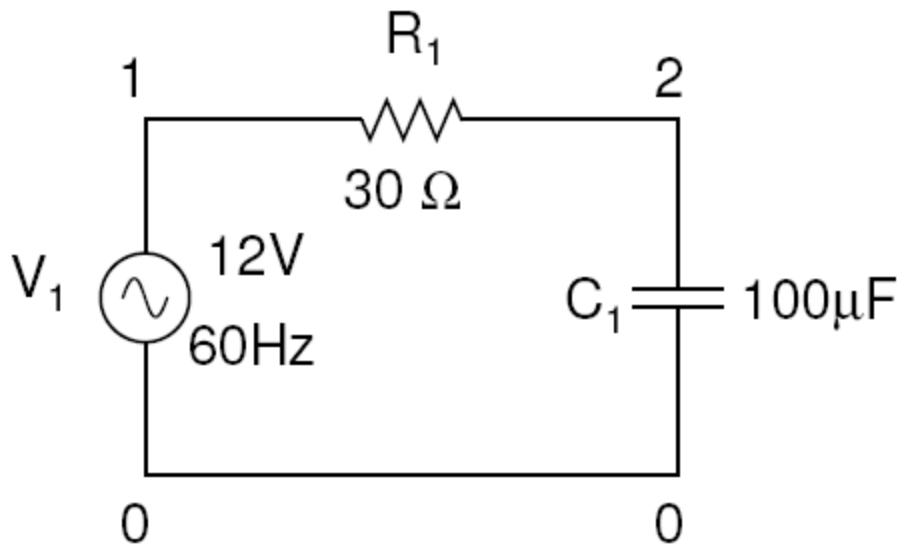SPICE **Netlist** – text file containing circuit description



INPUT

```
* Demo of a simple AC circ.  
v1 1 0 ac 12 sin  
r1 1 2 30  
c1 2 0 100u  
.ac lin 1 60 60  
.print ac v(2)  
.end
```

OUTPUT

--- AC Analysis ---

frequency: 60 Hz

V(2): mag: 7.94876 phase: -48.5171 voltage

Netlist (closer look)

* Demo of a simple AC circ.

Circuit description

```
v1 1 0 ac 12 sin ; v1 is an AC source of 12V amp.  
r1 1 2 30 ; r1 is 30 Ohm between nodes 1 and 2  
c1 2 0 100u ; c1 is 100uF between nodes 2 and 0  
.ac lin 1 60 60 ; directive to perform AC analysis  
.print ac v(2) ; print out the voltage from node 2  
.end ; anything after .end will be ignored
```

SPICE directives

Commands starting with dot (**.ac**, **.end**, etc.) are known as **SPICE directives**




LTspice IV

- A **freeware** circuit simulator (Windows or *nix/Wine)
- Netlist syntax is powerful but hard to visualize
- LTspice has **schematic capture** and is much **easier to use** than traditional text-based SPICE. The user can enter a circuit to be simulated via a **graphical user interface**
- Has **virtual scope**, makes Bode plots, performs FFT, etc.
- Worth learning about
 - It is fast, expandable, powerful, and free
 - **Most widely used** noncommercial CAD electronics software

中文网站 日本サイト Quality Careers Contact Us MyLinear

LINEAR TECHNOLOGY

PRODUCTS SOLUTIONS DESIGN SUPPORT PURCHASE COMPANY

Search 
ADVANCED SEARCH →

Home > Design Support > Design Simulation > LTspice/SwCAD III

LTspice/SwCAD III

- > Design Simulation
 - > **LTspice/SwCAD III**
 - > PScope (Quick Eval-II)
 - > Quick Eval System
 - > FilterCAD
 - > LT1568 Filter Design
 - > The Configurator
 - > Spice Models
 - > BodeCAD
 - > Noise
- > Quality and Reliability
- > Packaging Information
- > Lead Free Program
- > Reference Design Support
- > Solutions Brochures
- > Application Notes
- > Cross Reference Information
- > Passive Component Suppliers


+ MyLinear Sign Up
For a MyLinear Account >

Before You Download, Register for SwitcherCAD Updates


SwitcherCAD/LTspice is updated with new features, performance enhancements and device models on a regular basis. To receive email notification whenever a new SwitcherCAD version is released, just register as a Linear Insider today. In addition to SwitcherCAD news and updates, you'll receive notification of new product releases, the latest technical documents and more.

- [Register for a new MyLinear account.](#)
Your download will begin immediately upon completion of the registration.
- [No thanks, I'll download the software.](#)


SITE HELP SITE MAP SITE INDEX SEND US FEEDBACK
© 2007 Linear Technology | Terms of Use | Privacy Policy

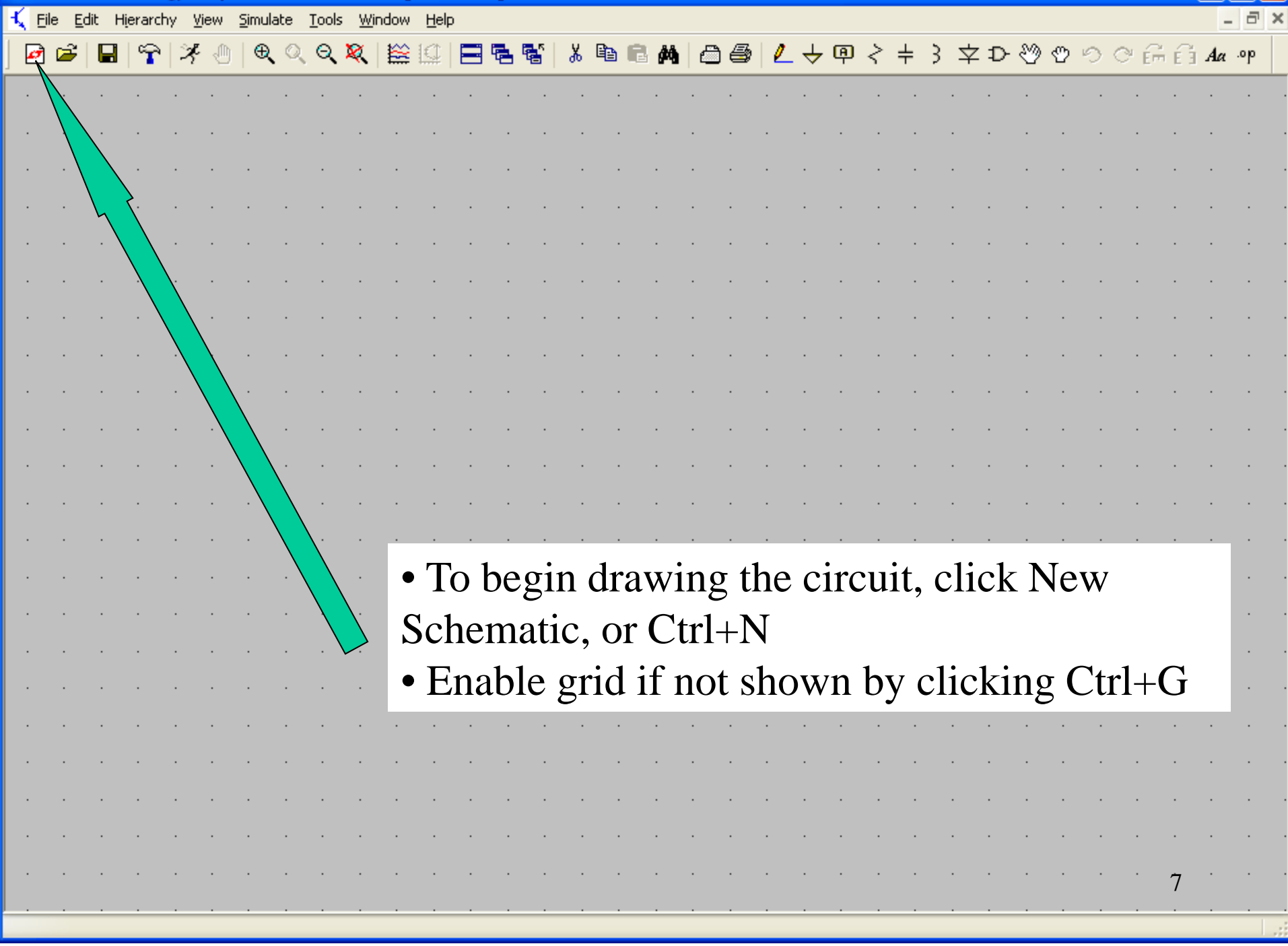

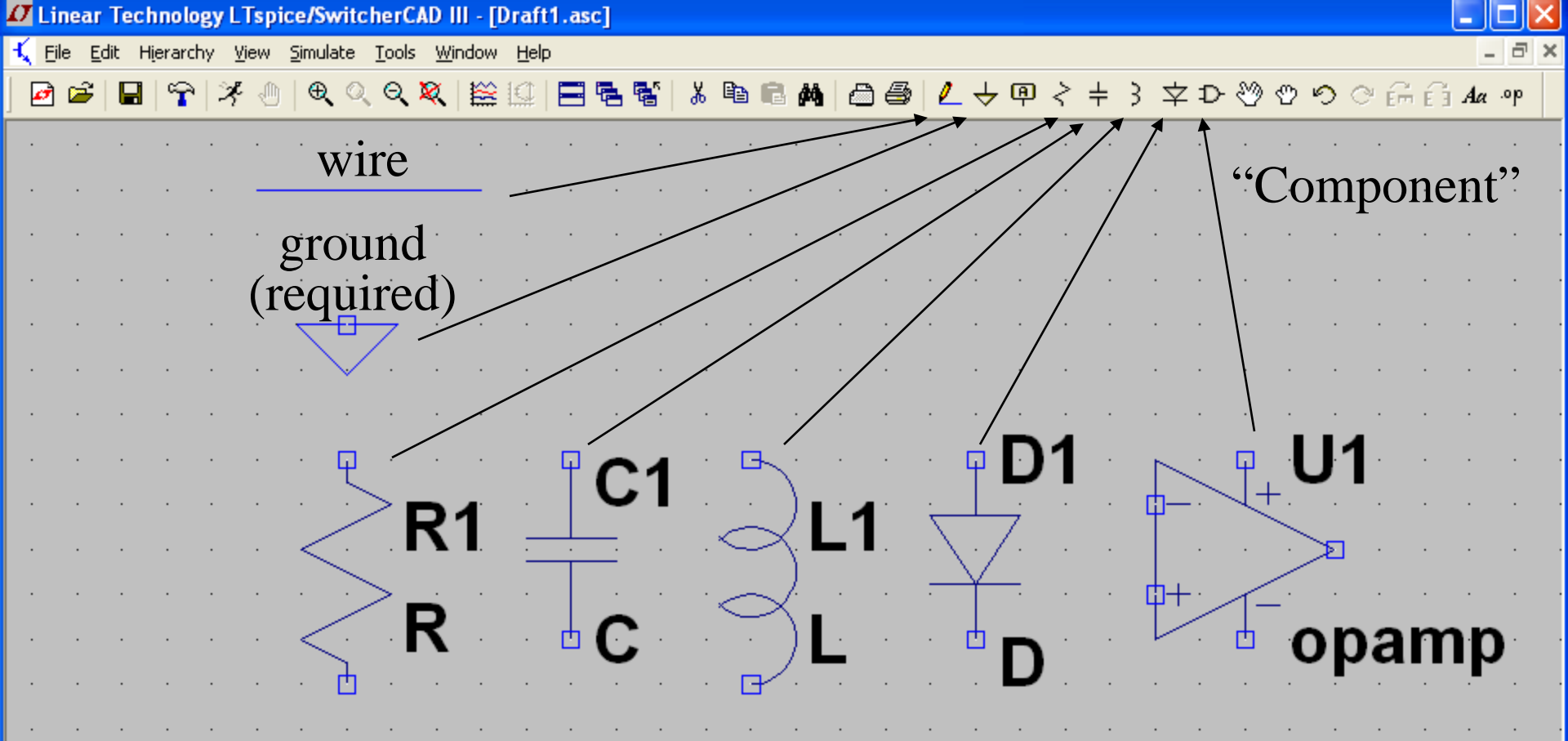
- To begin drawing the circuit, click New Schematic, or Ctrl+N
- Enable grid if not shown by clicking Ctrl+G



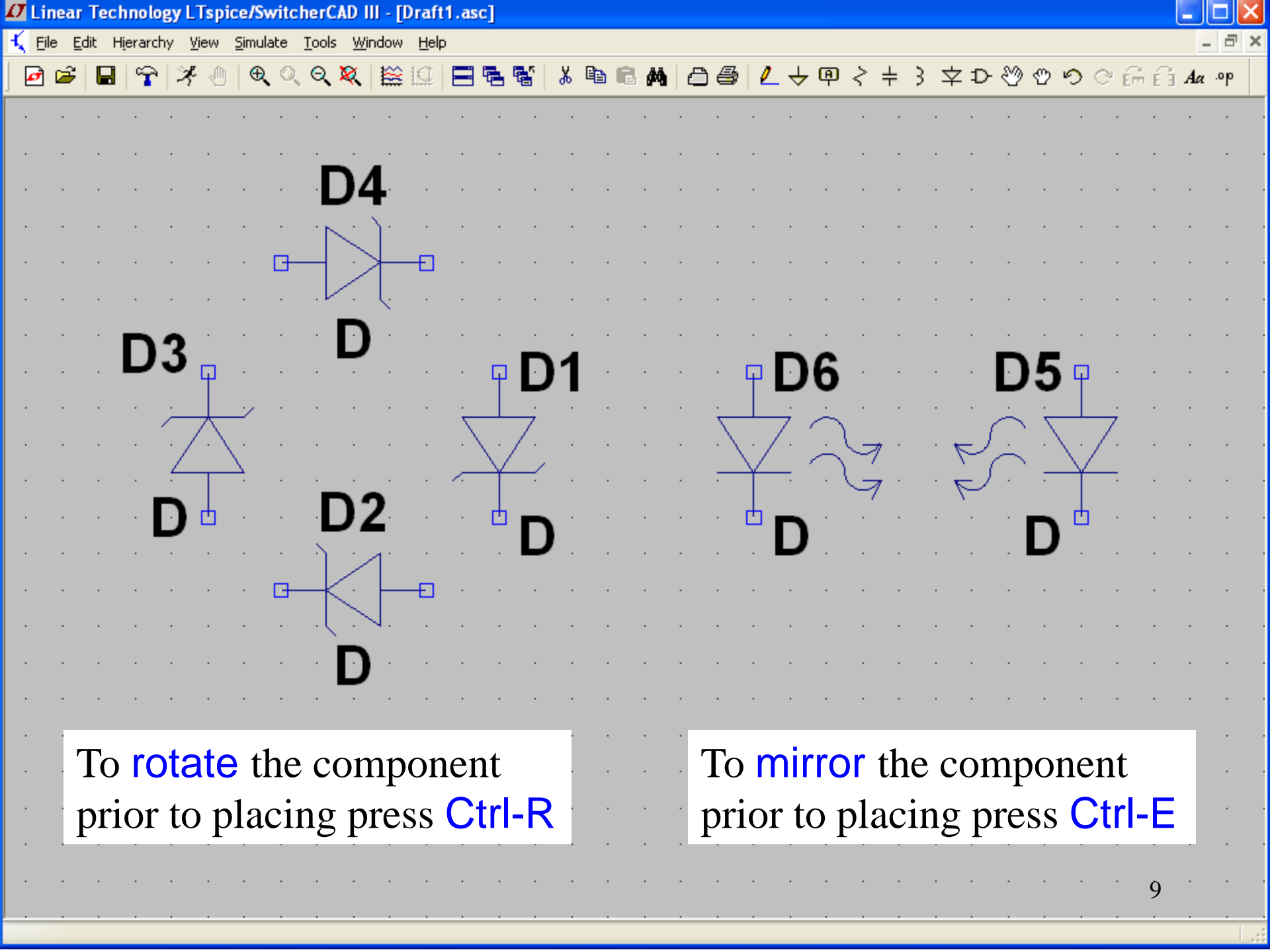- To add a component, click on the corresponding icon
- **Component** button contains slew of predefined components: voltage and current sources; transistors; opamps; gates; user-defined stuff
- You can Delete (F5 or Ctrl-X) and Move (F7) components, as well as Drag (F8) them (keep the wires connected)




D4

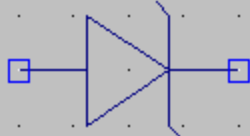


D

D3

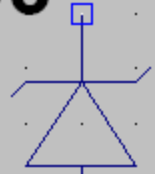


D

D1

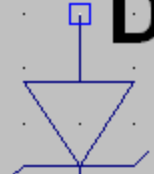

D

D6

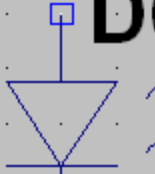


D

D5



D

D2

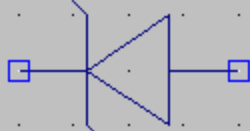


D

To **rotate** the component prior to placing press **Ctrl-R**

To **mirror** the component prior to placing press **Ctrl-E**


Toolbar Summary

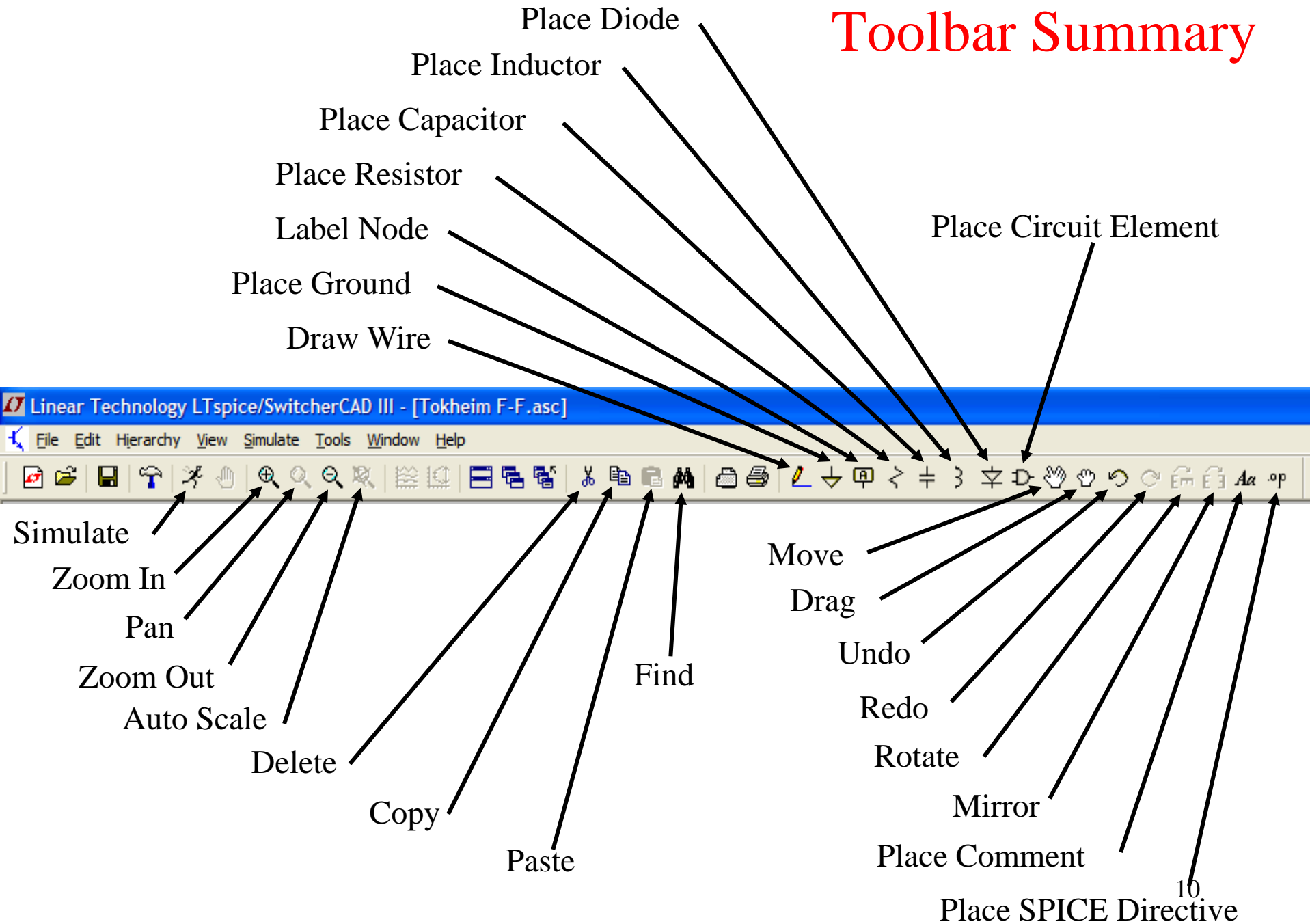

Prefixes are *case insensitive*: T = t, G = g, and so on

- T = terra = 10^{12}
- G = giga = 10^9
- MEG = meg = 10^6
- K = kilo = 10^3
- M = milli = 10^{-3}
- U = micro = 10^{-6}
- N = nano = 10^{-9}
- P = pico = 10^{-12}
- F = femto = 10^{-15}

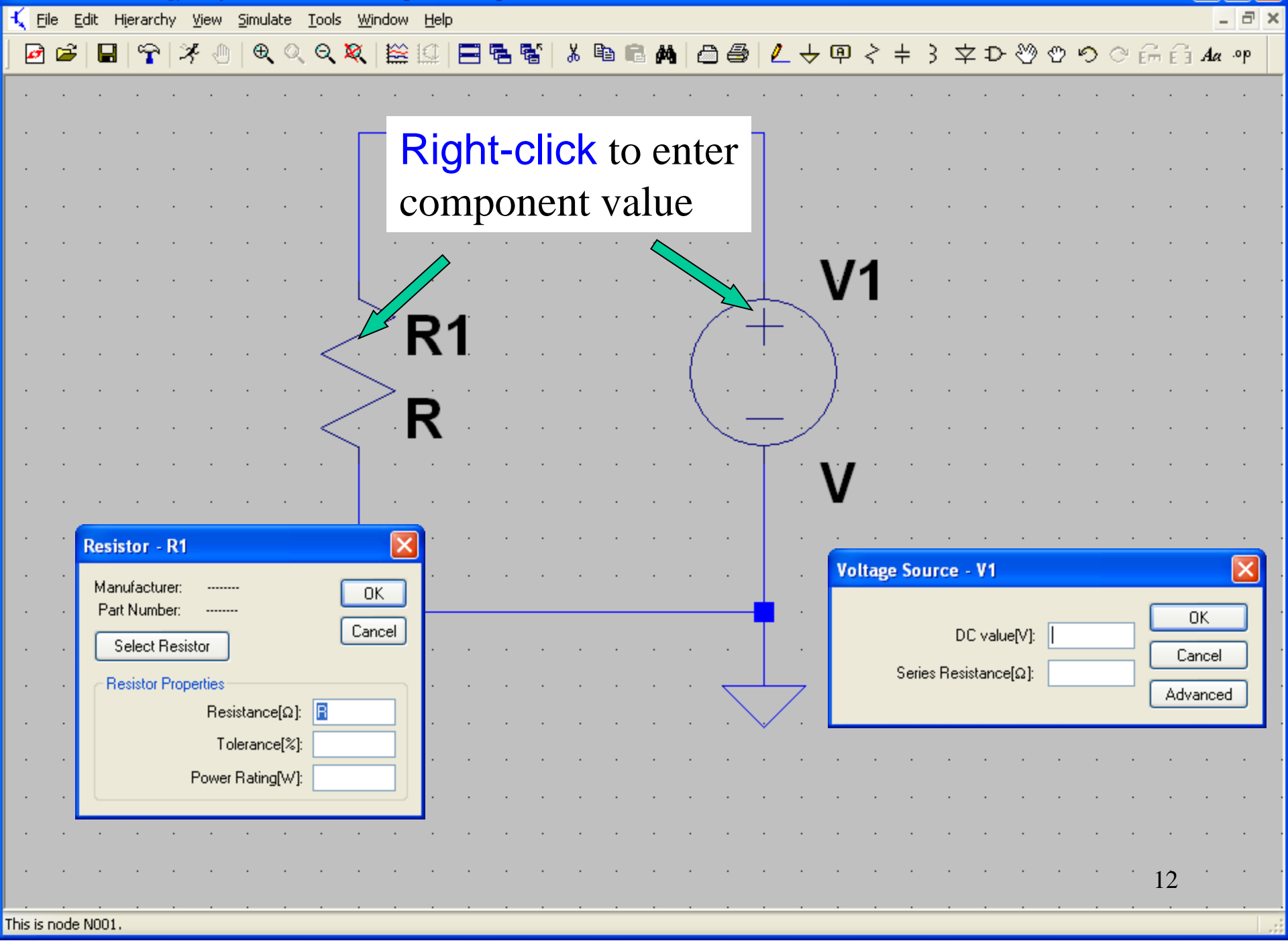No need to enter units, they are assumed (e.g. “1M” is 1mV if entered for voltage, 1ms if entered for time, etc.)



Right-click to enter component value

R1
R

V1
V

Resistor - R1

Manufacturer: -----

Part Number: -----

Resistor Properties

Resistance[Ω]:

Tolerance[%]:

Power Rating[W]:

Voltage Source - V1

DC value[V]:

Series Resistance[Ω]:


SPICE analysis

“Draw” your circuit, then specify all of the components, then select Simulate → Edit Simulation Cmd



Your choices:

- Transient analysis
- AC small signal analysis
- DC sweep
- Noise analysis
- DC transfer function
- DC operating point (Q-pt)

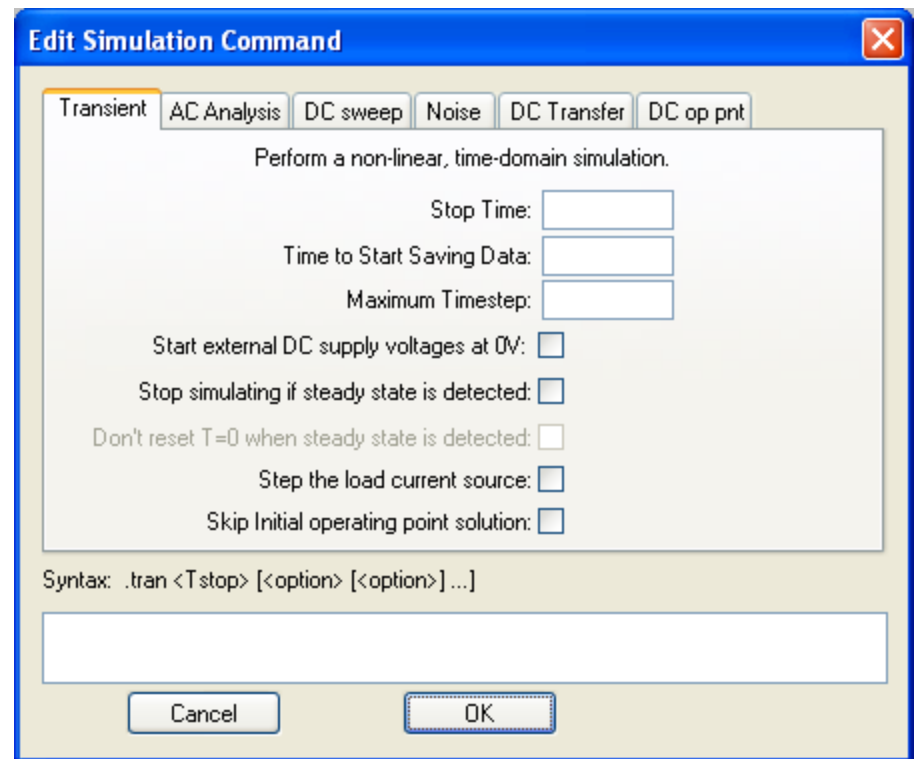Highlighted is what you will be using in this course



Adding SPICE directives

- After setting up the simulation command, you are set to go. Simply click **Run** button 
- Run command is a SPICE directive itself `.ac dec 50 1 1000`
- You can **add** other SPICE commands **directly** by clicking on Spice Directive button 
- Refer to HELP for details on the syntax

SPICE use in this course

- Your **home assignment** for this week includes working your way through **Supplement Part 1** (a tutorial) then working home problems using LTspice.
- Install LTspice on your own computer. LTspice is installed on all lab computers and in A&EP computer room
- **Supplement Part 2** contains **LTspice experiments**. They will start after the break and are to be done in the same way as the usual lab experiments, but using LTspice. Print out results using the lab printers, attach them to your lab report, etc.
- You can do LTspice experiments anywhere you have access to LTspice, not just in the lab

Two examples

- We will look at how to setup two examples
 - Example1: crossover corrected push-pull amp (ex6.10)
 - Example2: active filter
- Any **additional files** not included with LTspice but required for this course are found under Spice models **on the Blackboard**.



The screenshot displays the Blackboard interface for Cornell University. At the top, the Cornell University logo and name are visible, along with navigation links for Home, Help, and Logout. Below this, there are tabs for 'My Courses' and 'All Blackboard Courses'. A sidebar on the left contains a menu with options: Course Info, Discussions, Course Docs, Assignments, SPICE Models (highlighted with a yellow arrow), Misc Links, and Tools. Below the menu are buttons for Control Panel, Refresh, and Detail View. The main content area shows the breadcrumb path: ELECTRONIC CIRCUITS (PHY S3360-AEP3630-BAZAROV-SPRING2010) > SPICEMODELS. Under the heading 'SPICE Models', there is a section titled 'Salt & Pepper' with an icon of a document and two salt and pepper shakers. At the bottom, there is a section for 'LTspice Library Files' with a download icon, a link to 'SPICE.zip (200.218 Kb)', and a note: 'Files needed for LTspice experiments and home assignments.'

First example demonstrates transient analysis

- **Next**, specify component values for resistors, DC voltages by right-clicking on the elements (be careful, sometimes you may click on the name thinking you are changing the value).


```
.include LM741.MOD  
.tran 0.1
```

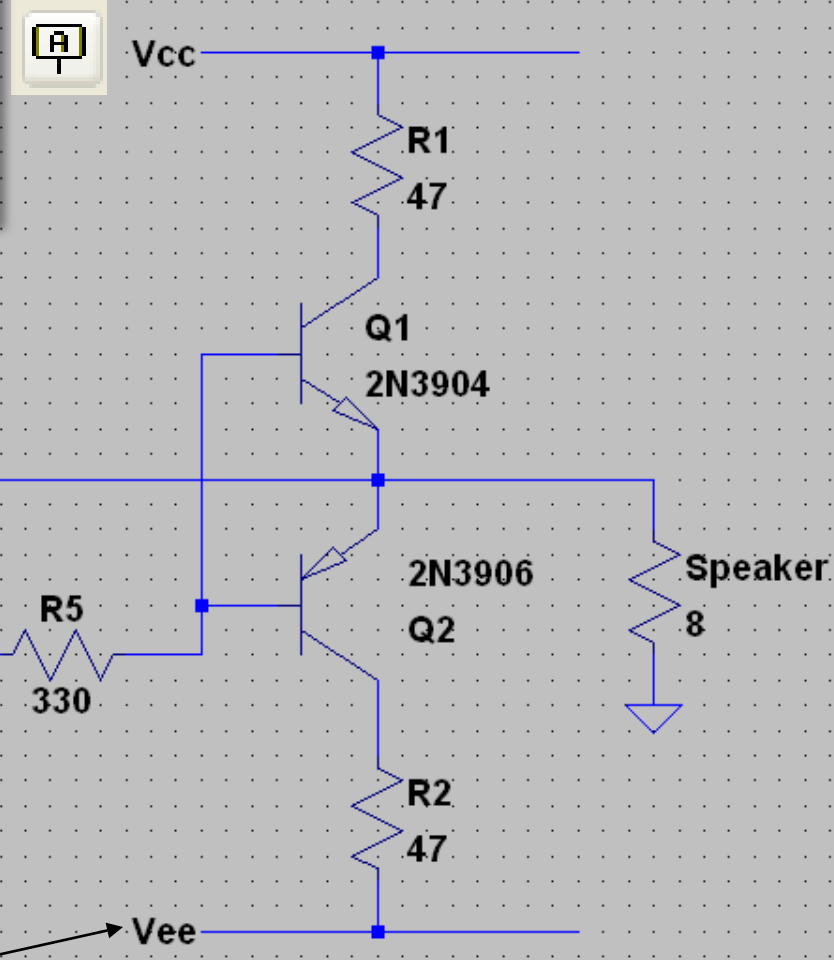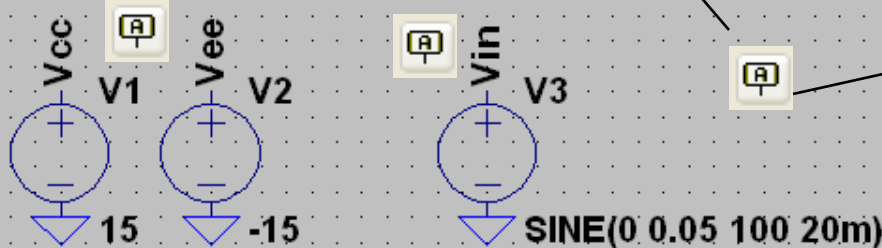- **First**, create the circuit (you may want to use Ctrl-E, Ctrl-R to mirror and rotate the symbols for best orientation)





Assigning Vin

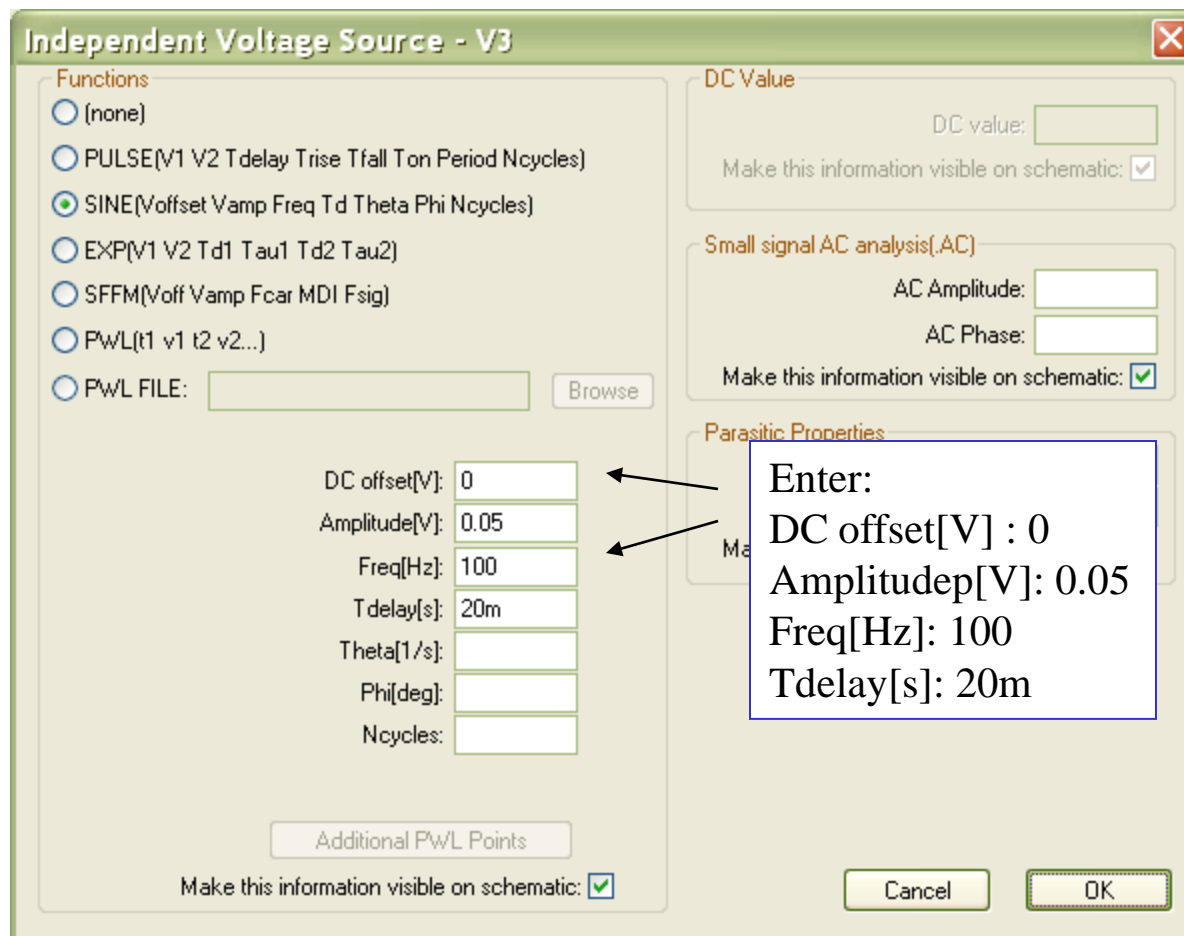- Right-click on Vin, then click Advanced. You will see a window like this. Choose SINE Function.



Assigning Diodes and Transistors

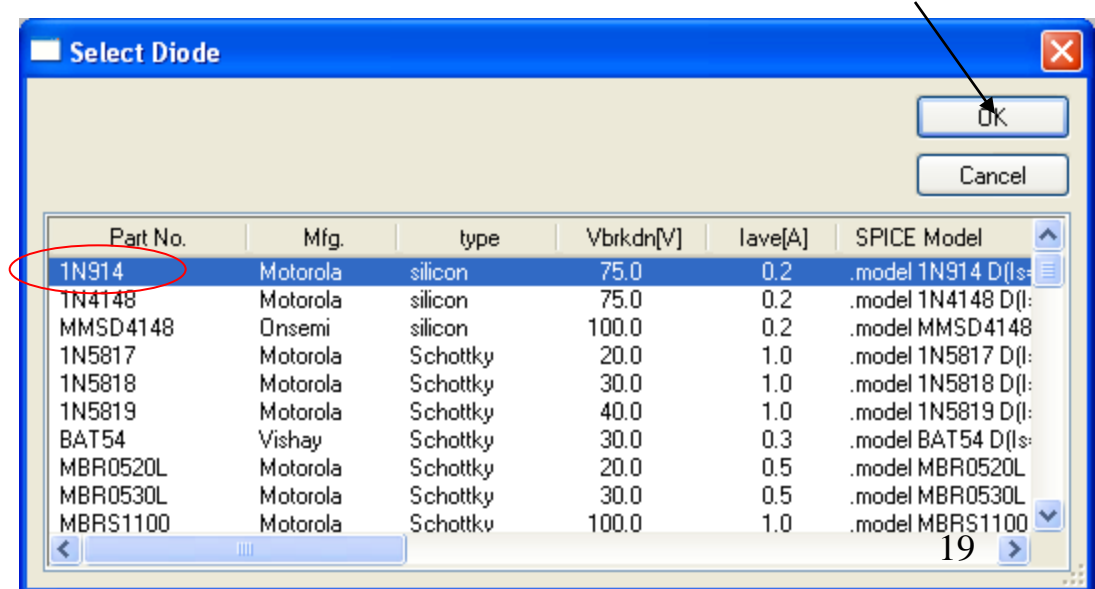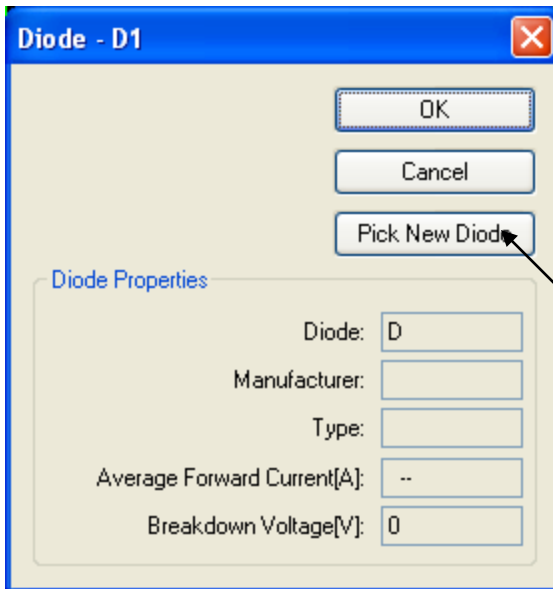If you do not assign diode and transistors, LTspice will use some default models. It may be OK for a simple circuit like the one we are looking at. Real-life situations require more accurate model specific to the actual component being used. E.g. to assign a specific diode model, right-click on it, then click “Pick New Diode” and choose IN914.



Assigning Transistors and opamp

- Similarly, assign the transistors to be 2N3904 and 2N3906
- Note: you will find some familiar **components** missing (e.g. LM741 op-amp); you have to **add** them to **LTspice**
- All major manufacturers will have **SPICE** model files **online**

The screenshot shows the National Semiconductor website for the LM741 Operational Amplifier. The browser address bar displays <http://www.national.com/mpf/LM/LM741.html>. The page header features the National Semiconductor logo and navigation links: [Select](#), [Design](#), [Buy](#), [Explore](#), [Contact Us](#), [Analog University](#), [WEBENCH](#), [Tools](#), [My Profile](#), and [Sign-On](#). Below the header is a search bar and buttons for [Order Parts](#) and [Cross-Ref](#). The breadcrumb trail reads: [Products](#) > [Amplifiers/Buffers/Comparators](#) > [Operational Amplifiers](#) > [General Purpose](#) > [LM741](#). The main heading is **LM741 - Operational Amplifier**, accompanied by a **RoHS Compliant** logo. A navigation menu includes [Datasheet](#), [Packaging](#), [Samples & Pricing](#), [Reliability](#), [Design Tools](#), [Models](#) (circled in red), [Application Notes](#), and [Knowledge](#). The **General Description** section states: "The LM741 series are general purpose operational amplifiers which feature improved performance over industry standards like the LM709. [More...](#)". The **Typical Application** section shows a circuit diagram of an LM741 op-amp configured as a voltage follower. The non-inverting input (+) is connected to the output, and the inverting input (-) is connected to ground through a 10 kΩ resistor. The output is labeled "OUTPUT". A note above the diagram says "*click for larger image". The **Also Recommended** section lists three alternative op-amps: **LM8261** (Higher Bandwidth, faster Slew Rate, higher Output Current, Sm Package), **LMV721** (Wider Bandwidth, Lower Noise, Power), and **LM7301** (Improved Bandwidth And Slew Rate, Lower Supply Current, Rail-to-rail Input & Output). The **Additional Resources** section includes a link to [Design Tools \(see below\)](#).

How to add LM741

- Google for LM741, you will get to the manufacturer's web-site with link to Model file [LM741.MOD](#)
- Download it, it is an ASCII file in SPICE format:

```
*//////////////////////////////////////
* (C) National Semiconductor, Inc.
* Models developed and under copyright by:
* National Semiconductor, Inc.

*//////////////////////////////////////
* Legal Notice: This material is intended for free software support.
* The file may be copied, and distributed; however, reselling the
* material is illegal

*//////////////////////////////////////
* For ordering or technical information on these models, contact:
* National Semiconductor's Customer Response Center
*           7:00 A.M.--7:00 P.M.   U.S. Central Time
*           (800) 272-9959
* For Applications support, contact the Internet address:
*   amps-apps@galaxy.nsc.com



*//////////////////////////////////////
*LM741 OPERATIONAL AMPLIFIER MACRO-MODEL
*//////////////////////////////////////
*
* connections:      non-inverting input
*                   |   inverting input
*                   |   |   positive power supply
*                   |   |   |   negative power supply
```

it comes from National Semiconductor

component model describes frequency response, input and output impedance, etc. can be a subcircuit that includes other elements

How to add LM741

- Place this file where LTspice will look for it, preferably in **the local directory** (where your circuit file is saved)
- Add generic opamp (**opamp2**) to your circuit
- Right-click on the symbol to invoke **Component Attribute Editor**
- Enter Value = **LM741/NS**
(must match the first line in LM741.MOD file, which is not a comment, i.e. not preceded by *, something like .SUBCKT LM741/NS ...)
- Add **SPICE directive**

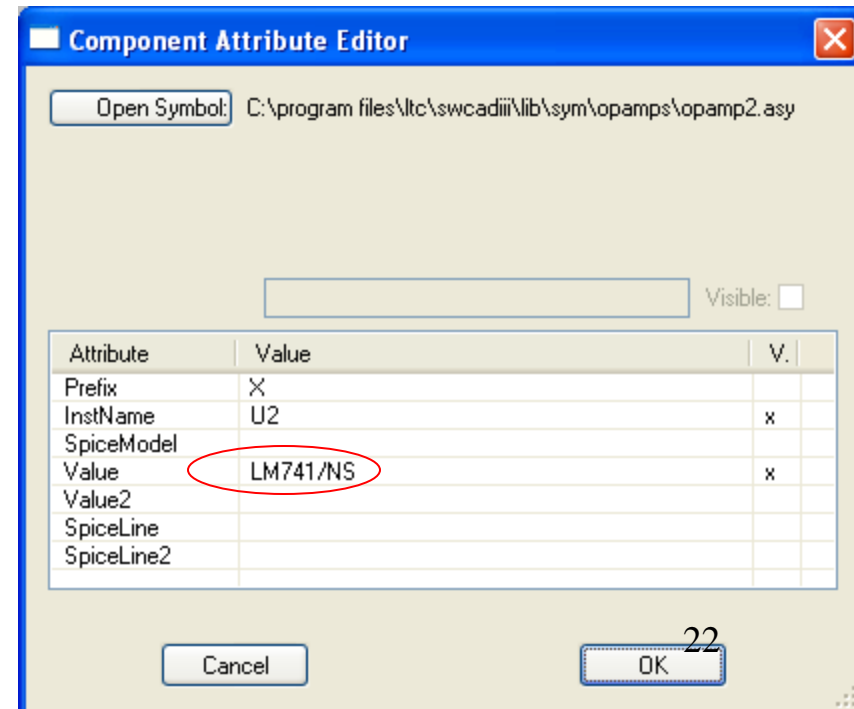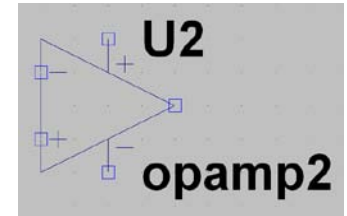


.lib LM741.MOD

Time Transient Analysis



- Choose **Simulate** → **Edit Simulation Cmd**
- Indicate Stop Time of 0.1 s
- Click OK and place SPICE directive somewhere on your circuit


.tran 0.1

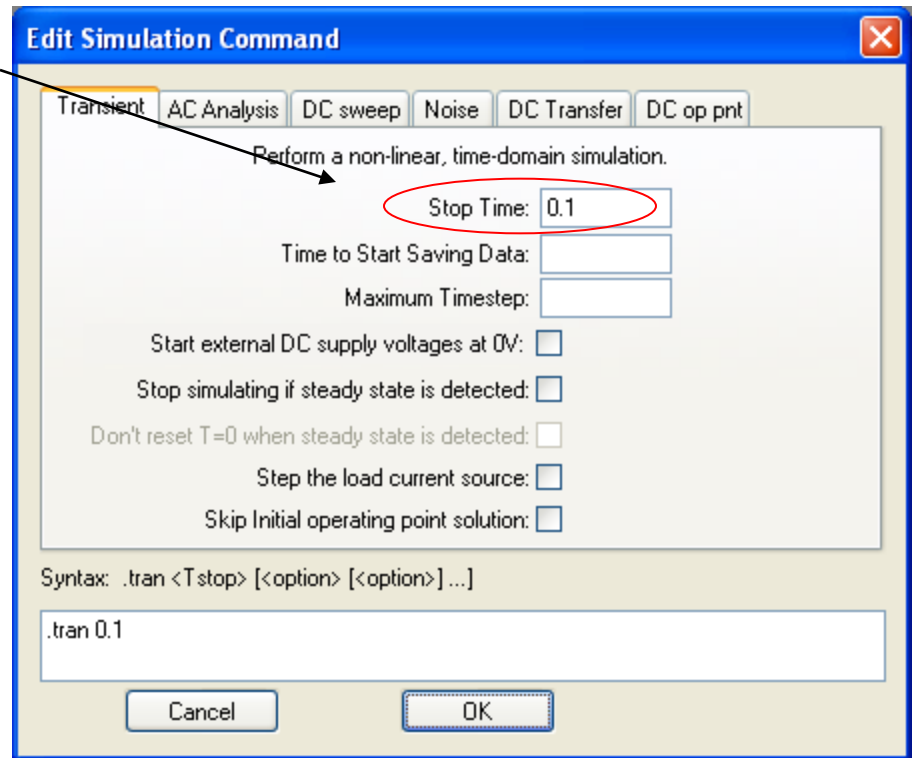- Ready to go!



Looking at the result


- LTspice has nice tools to look at the **waveforms**, voltages or currents, **FFT** (Fourier Analysis), **gain amplitude and phase** (in AC analysis)
- You can open **multiple panes**, plot **signals versus time** or **signal versus another signal**
- You can **zoom in**, **zoom out**, also activate scope-like **cursor(s)** for more accurate measurements on waveforms
- By default the mouse cursor transforms into **voltage probe**  , however, when hovering over a component (or pressing Alt over wire), it transforms into **current probe** 
- Pressing **Alt** over an element will report instantaneous **power drawn by the element** (thermometer icon)

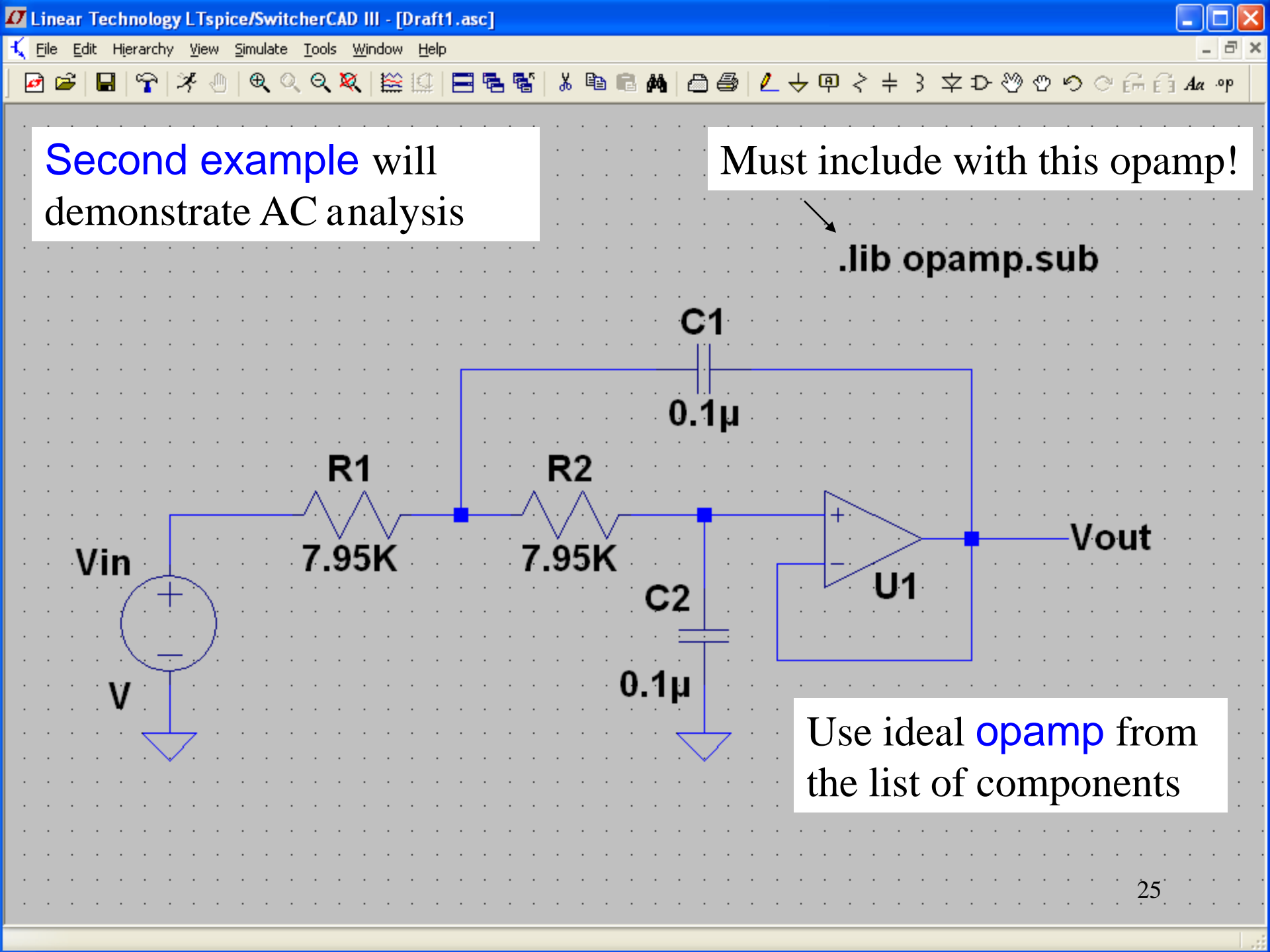

Second example will demonstrate AC analysis

Must include with this opamp!


.lib opamp.sub

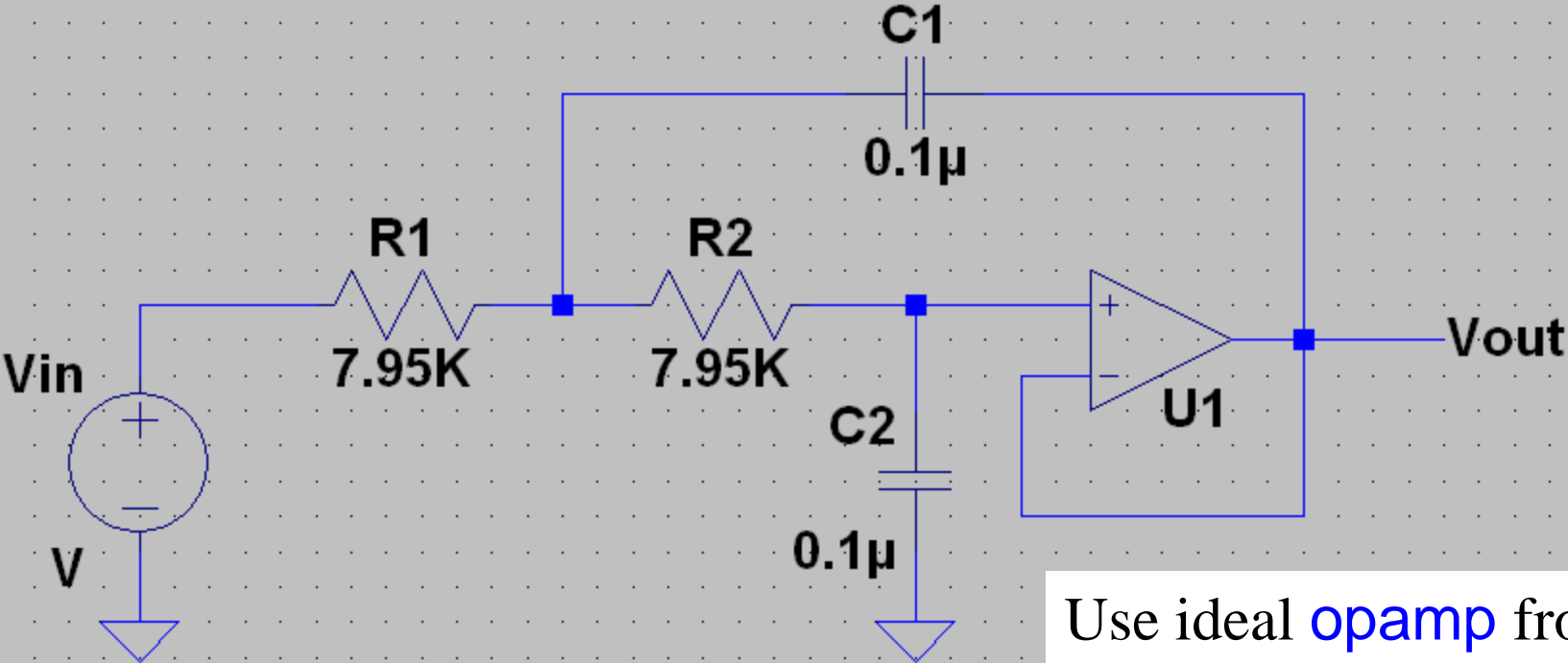

Use ideal opamp from the list of components

Assigning Vin

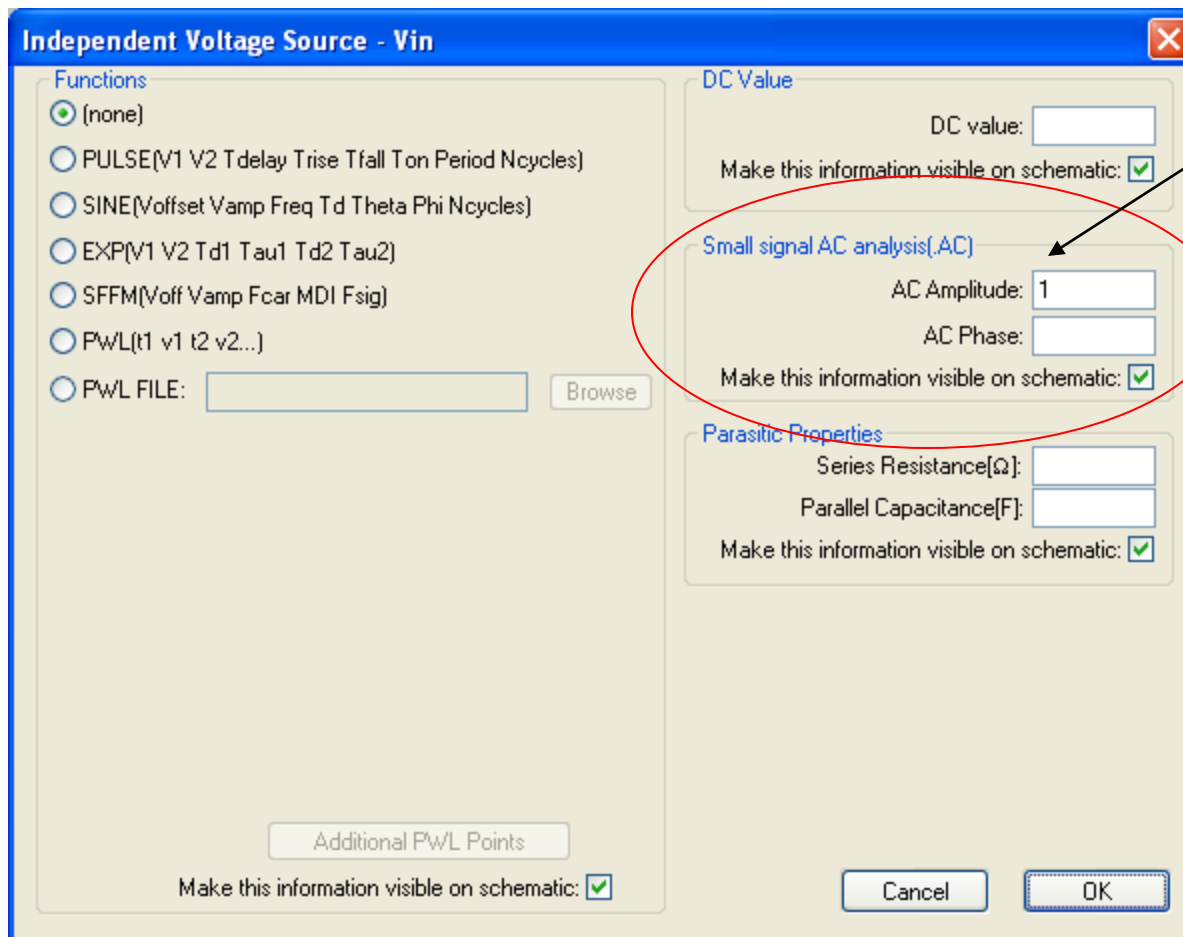- Right-click on Vin, then click Advanced. Use **Small signal AC analysis** section.




AC amplitude
1 volt

AC Analysis




- Choose **Simulate** → **Edit Simulation Cmd**
- On **AC analysis tab** specify type of sweep (decade), number of points per decade, initial and final frequencies
- Click OK, plant SPICE directive somewhere

```
.ac dec 50 1 10K
```

- Ready to go!

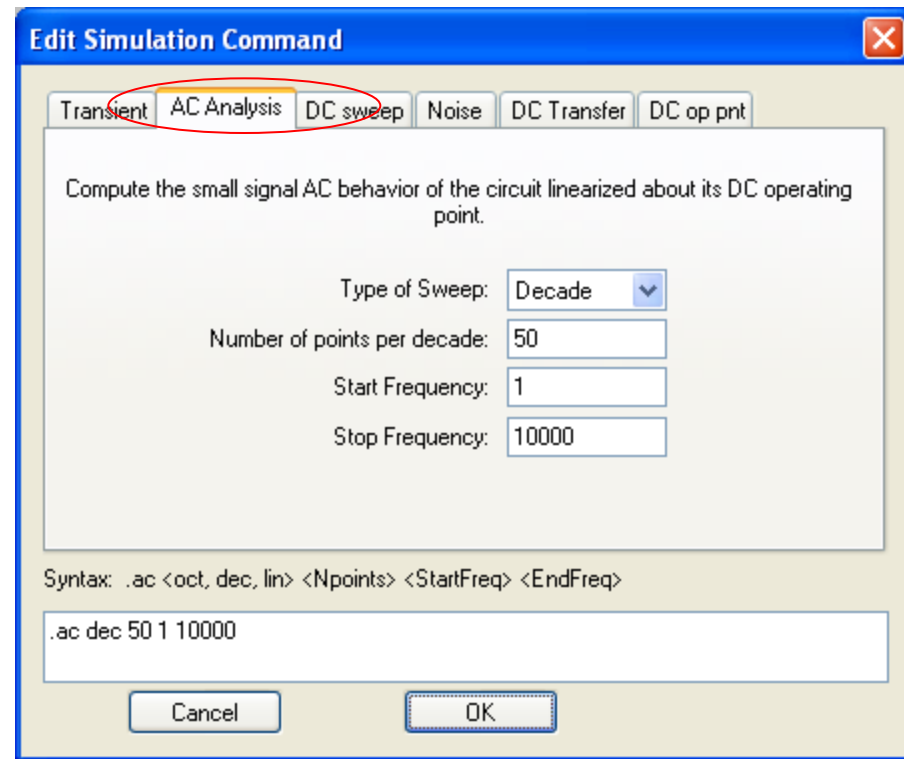

• Click on Vout to display Bode plot

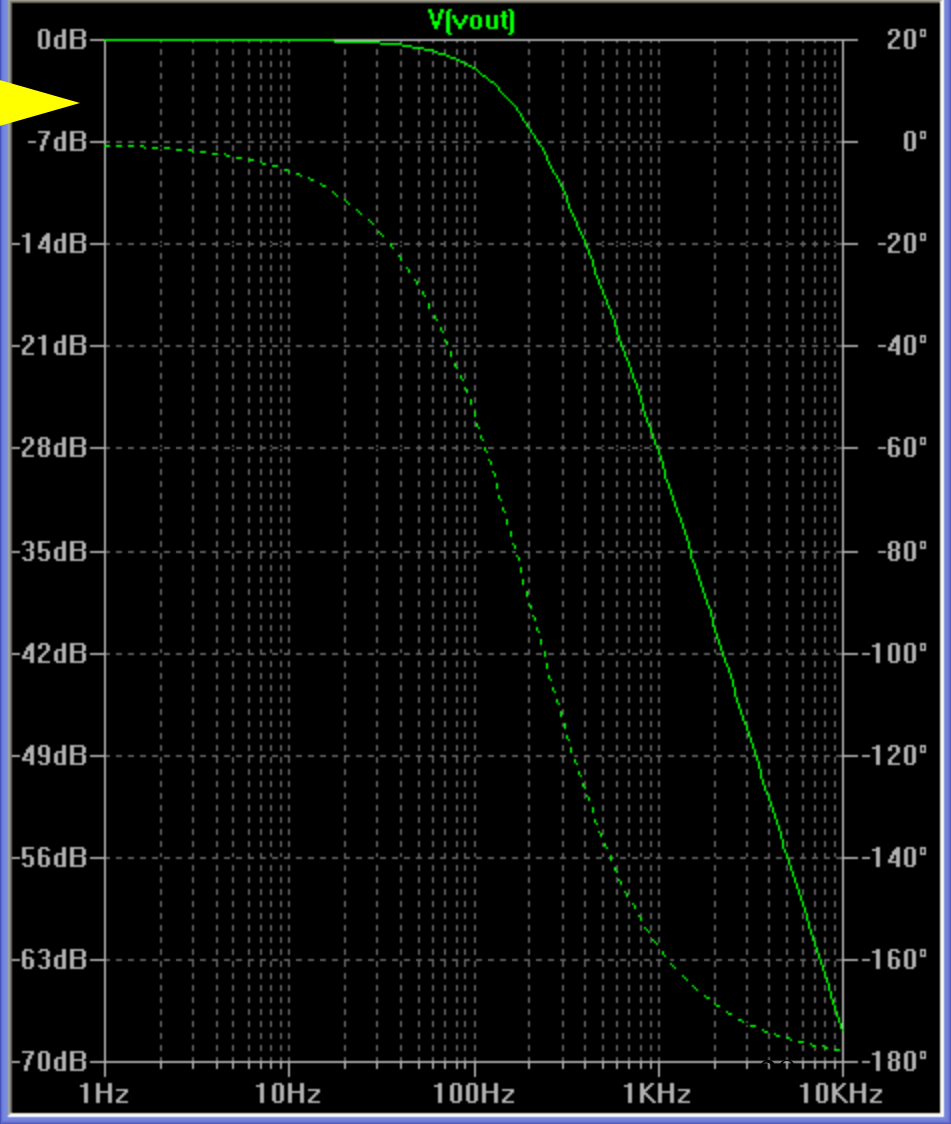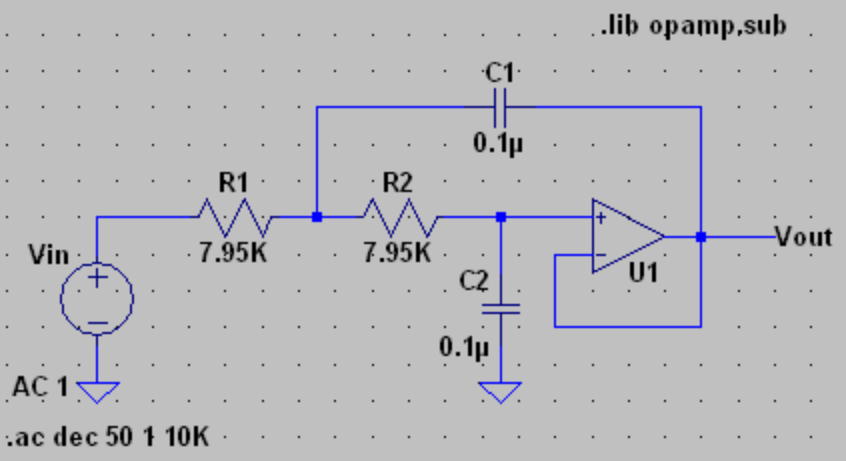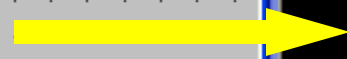

Few gotchas

- “M” and “m” are interpreted the same by SPICE. Thus, a resistor value of 10M is the same as 10m (ten milliohms)
 - Use 10MEG (or 10E6) to specify ten megohms
- Do not enter “1F” or “1f” as the capacitance for a one-farad capacitor (enter “1”). “F” and “f” designate the prefix femto (10^{-15})
- When simulating astable circuits (multivibrator), specify some small nonzero initial voltage in the positive feedback to seed the oscillations

Initial conditions SPICE directive

.IC V(vi) = 1u

Additional resources

- [LTspice Supplement](#) (read Part 1 Tutorial this week)
- [Documentation](#) and examples [installed with LTspice](#)
- Our PHYS3360 mailing group
- [Yahoo! LTspice group](#) (great resource, kept active by many thousands of users)