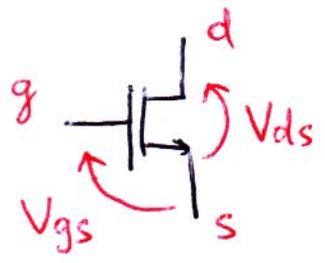



P3360/AEP 3630

Lecture 21

MOSFET modes (n-channel)



$I_d = I_s$

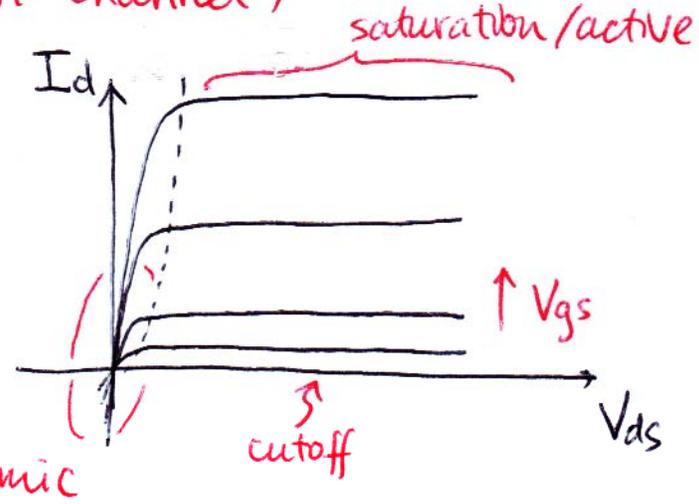

mathematical model

If $V_{gs} < V_T$, \Rightarrow cut off ($I_d = 0$)

Else if $V_{ds} < V_{gs} - V_T$, \Rightarrow ohmic

$$I_d = K(2(V_{gs} - V_T)V_{ds} - V_{ds}^2)$$


else, saturation

$$I_d = K(V_{gs} - V_T)^2 \neq f(V_{ds})$$


$[K] \sim \frac{mA}{V^2}$ $[V_T] \sim V$

e.g. $100 \frac{mA}{V^2}$ and $2V \rightarrow$ const's specific to a MOSFET

Ohmic region

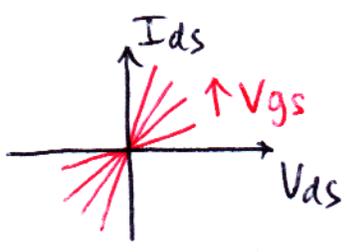


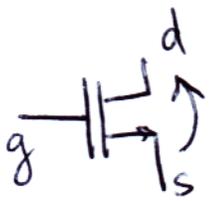- volt. controlled R
- use for automatic gain control




$$R_{ds} = \frac{V_{ds}}{I_d} \sim \frac{1}{2K(V_{gs} - V_T)}$$

for small V_{ds}

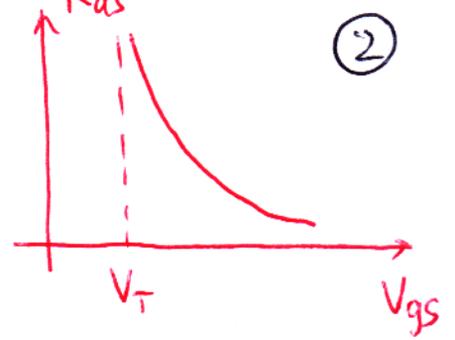


saturation (= active) region

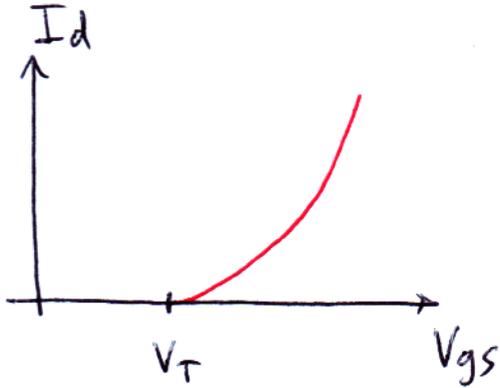

$$I_d = K(V_{gs} - V_T)^2 \quad V_{ds} > V_{gs} - V_T$$


I_d is indep from V_{ds}

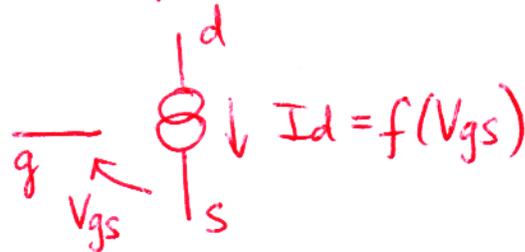

- volt. controlled current source

MOSFET circuit analysis

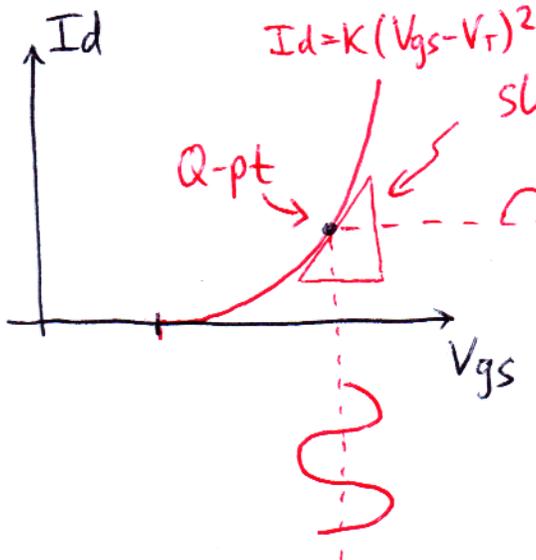- ① large signal or Q-pt determination
- ② small-signal analysis (if amplification)



$$I_d = K(V_{gs} - V_T)^2$$

slope = $g_m \left(\frac{1}{\Omega} \right) =$ "transconductance"

$$g_m = \left(\frac{\partial I_d}{\partial V_{gs}} \right)_{Q-pt} = 2K(V_{gs}|_{Q-pt} - V_T)$$

$$g_m = 2\sqrt{K I_d}|_{Q-pt}$$