
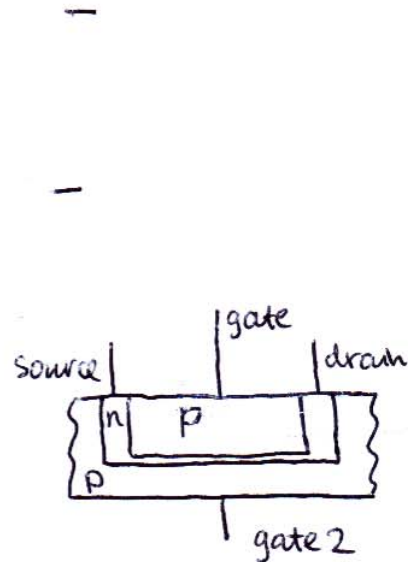


Lecture 22

MOSFET circuits

-
- 1)
-
-
- 2)
-
-


FET variants

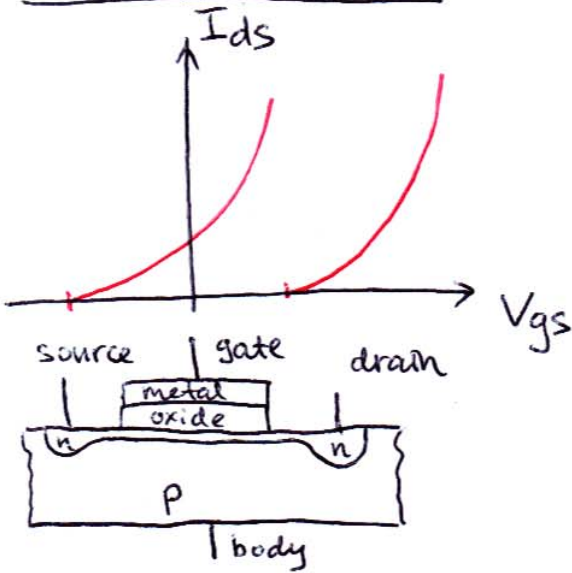

MOSFET pros & cons (vs BJT's)

- | | | |
|---|---|---|
| + | + | - |
| + | | - |


MOSFET analysis example

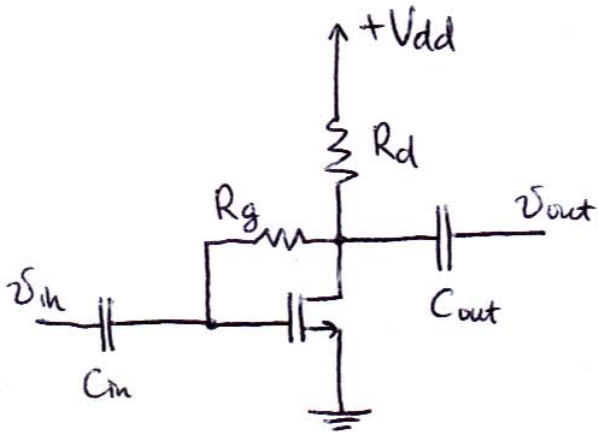

Suggestions

- This biasing is called


① Find Q-pt.

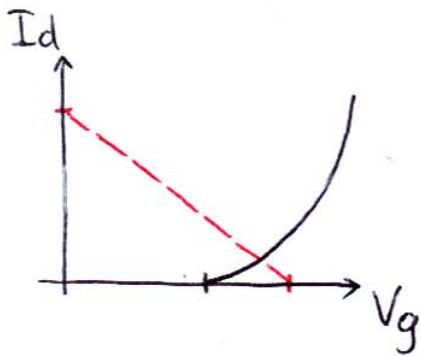

Approximately

(3)

② small-signal equivalent

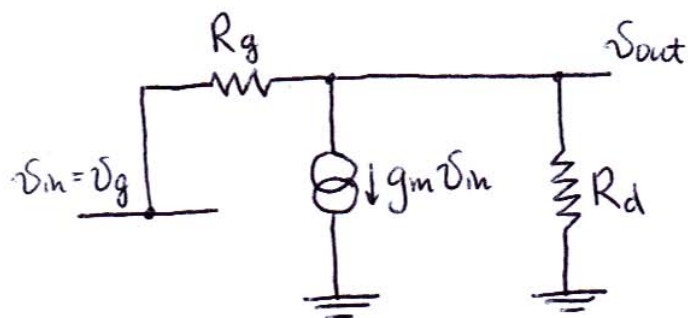

KVL & KCL :

input impedance : $R_{in} = \frac{v_{in}}{i_{in}}$

output impedance : $R_{out} = \frac{v_{out}}{i_{out,sc}}$

choosing caps :

P3360/AEP3630

Lecture 23

Analog signals

-

-

Digital signals




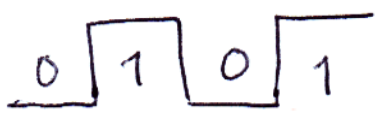
-

-

-

-

-

	analog	digital
original signal (vs. time)		
signal + noise		
recovered?		
arbitrary shapes?		

Digital representation of info

1

2

a)

-
-

b)

3


decimal

binary


Gray code

0
1
2
3
4
5
6
7

Types of digital circuits

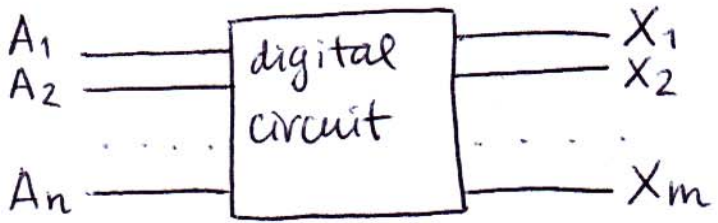

—

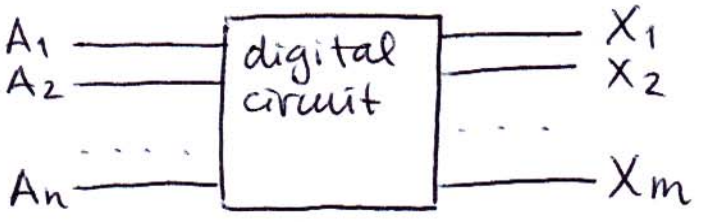

—

Truth table

P3360/AEP 3630

①

Lecture 24

Boolean operations & gates

All digital operations can be reduced to

Gates =

—

—

—

NOT


AND

Multiple inputs AND

OR

Multiple inputs OR

Application of time dependent signal

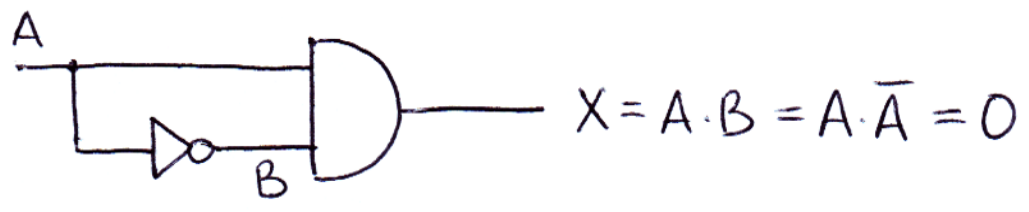

- any complicated fcn

-

-

Universal gates

-

-

-

NAND

NOR

De Morgan Theorem

(4)

Alternatively

-

Rules of Boolean algebra