

Lecture 22

MOSFET circuits

- analogous to BJT's

1) switching

- analog (e.g. "power MOSFETs" can drive ~kW loads)


- digital (e.g. complimentary MOS = "CMOS" digit. family)

LM Ch. 8


2) amplifiers

- common (drain, source, gate) } like ~ BJT's
 - differential amplifier

FET Variants

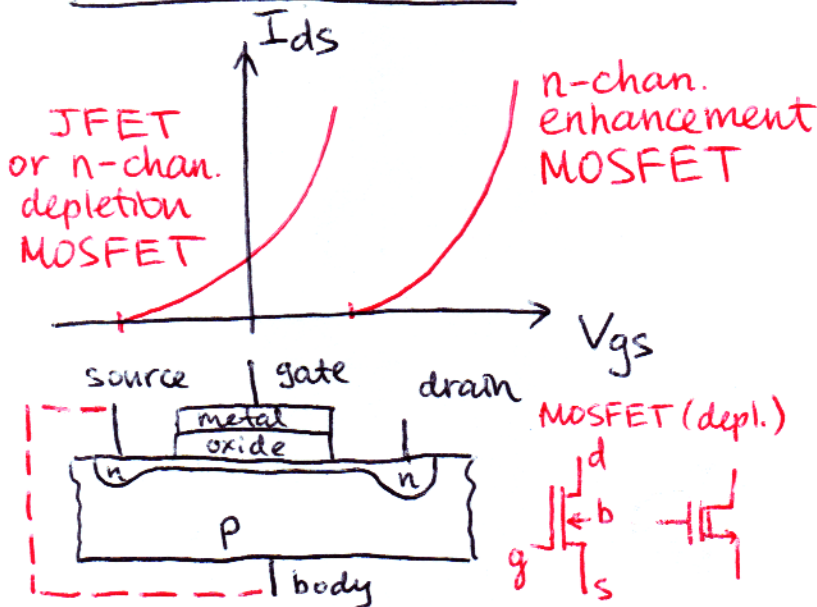

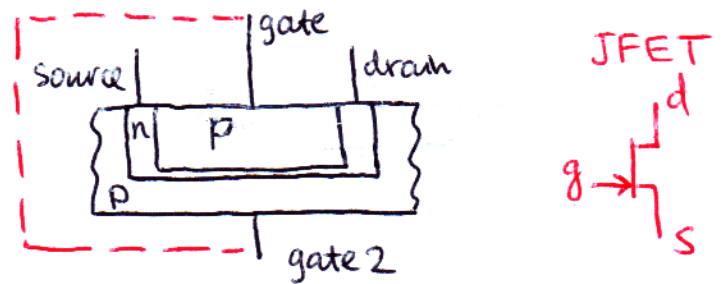- depletion n-chan. MOSFET
 - $V_{gs} = 0$, then n-channel ON
 - junction FET (JFET)




MOSFET pros & cons (vs BJT's)

- + $Z_m \sim$ huge
- + better rad. hardness
- + less T dep.
- more distortions
- Q-pt depends on K, V_T

MOSFET analysis example

②

Exp. 7.3

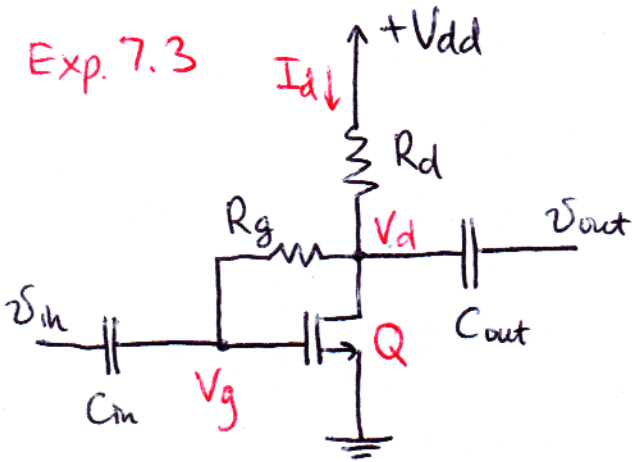

Q: what amp. configuration?

A: common source

Suggestions in the LM

$$V_{dd} = +5V$$

$$R_d = 270\Omega$$


$$R_g \sim 1M\Omega$$

- This biasing is called "self-bias", and R_g - "bias resistor"

Q: why? A: No current thru R_g , $\Rightarrow V_d|_{Q-pt} = V_g|_{Q-pt}$

① Find Q-pt.
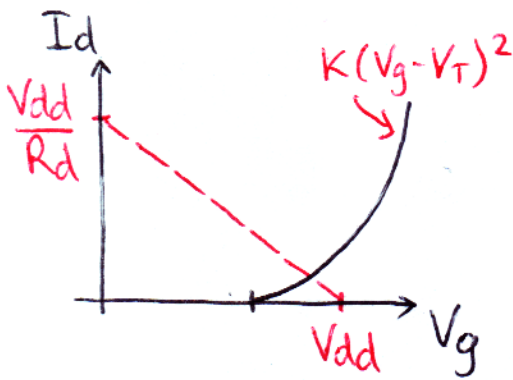
$$\left. \begin{aligned} I_d &= K(V_g - V_T)^2 \\ I_d &= \frac{V_{dd} - V_g}{R_d} \end{aligned} \right\} \text{can solve for } I_d, V_g$$



- for "large" K , $V_g|_{Q-pt} \approx V_T$

typical $K \approx 100 \frac{mA}{V^2}$, $V_T \sim 2V$
(varies from trans. to trans. but not so much with temperature)


Approximately (too lazy to solve quadr. equ.)

$$V_g \approx V_T : I_d = \frac{5V - 2V}{270\Omega} \approx 11mA$$

$$g_m \equiv \left. \frac{\partial I_d}{\partial V_{gs}} \right|_{Q-pt} = 2\sqrt{K I_d}|_{Q-pt}$$

$$g_m = 2\sqrt{100 \frac{mA}{V^2} \cdot 11mA} = 0.065\Omega^{-1} = (15\Omega)^{-1}$$

② small-signal equivalent

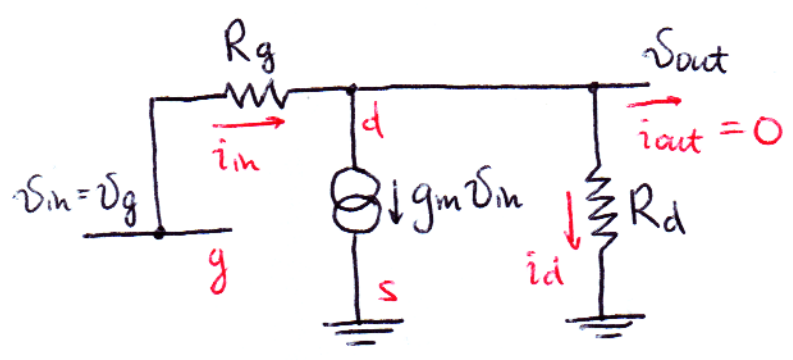

KVL & KCL:

$$i_{in} = \frac{v_{in} - v_{out}}{R_g} = g_m v_{in} + \underbrace{i_d}_{\frac{v_{out}}{R_d}}$$

$$v_{in} \left(\frac{1}{R_g} - g_m \right) = \frac{v_{out}}{R_d \parallel R_g}$$

$$G = \frac{v_{out}}{v_{in}} = R_d \parallel R_g \left(\frac{1}{R_g} - g_m \right), \text{ using } R_g \gg R_d \quad G \approx -g_m \cdot R_d$$

$$G = -(15\Omega)^{-1} (270\Omega) = -18$$

input impedance: $R_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in} \cdot R_g}{v_{in} - v_{out}} = R_g \frac{1}{1 - G} \approx 53 k\Omega$

output impedance: $R_{out} = \frac{v_{out}}{i_{out,sc}} = \frac{v_{out}}{\frac{v_{in}}{R_g} - g_m v_{in}} = \frac{G}{\frac{1}{R_g} - g_m} \approx 270\Omega$

choosing caps:

$$|Z_{cin}| \ll R_{in}, \quad |Z_{cout}| \ll R_{out}$$

E.g. for 1kHz sine wave:

$$C_{in} \gg 0.003 \mu F, \text{ e.g. } C_{in} \approx 0.1 \mu F$$

$$C_{out} \gg 0.59 \mu F, \text{ e.g. } C_{out} \approx 20 \mu F$$

- 1) Build LTspice circuit (2N7000)
- 2) perform Q-pt analysis (.op)
- 3) transient analysis (.tran)
- 4) ac small signal

} check gain.
 why different?
 $K \sim 300 \text{ mA/V}^2$
 $V_T \sim 3V$
 } LTspice 2N7000