


Lecture 24

Boolean operations & gates

All digital operations can be reduced to operations on "0"s and "1"s = boolean operations


Gates = basic building blocks that perform simple boolean operations, e.g. AND, OR, NOT, etc.

- gates can still be quite complicated inside (transistors, diodes, caps, etc.)
- no need to worry about their internals
⇒ higher level abstraction
- see spec. sheets for pinout, etc.

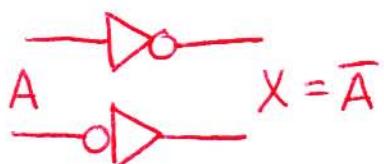NOT (complement, inverter)

truth table


A	X
1	0
0	1

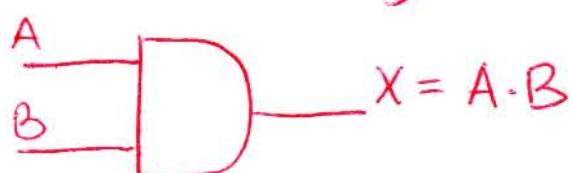AND binary or more inputs

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1


(2)

Multiple inputs AND

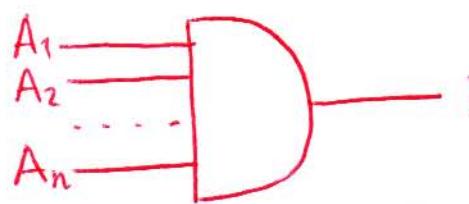

$$X = A_1 \cdot A_2 \cdot \dots \cdot A_n \Leftrightarrow \text{TRUE iff all inputs TRUE}$$


OR

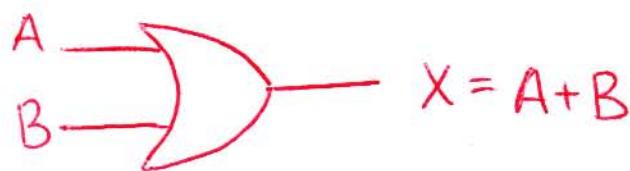

$$X = A + B$$


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

Multiple inputs OR

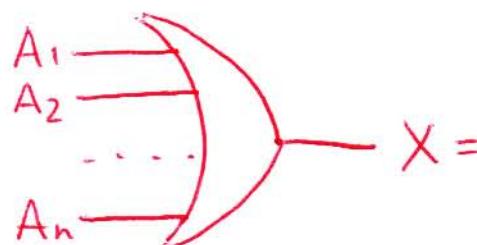


$$X = A_1 + A_2 + \dots + A_n \Leftrightarrow \text{TRUE iff any input TRUE}$$

Application of time dependent signal

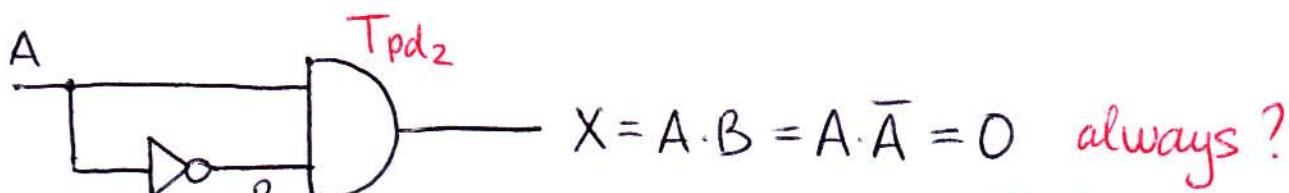

No, b/c of propagation delay

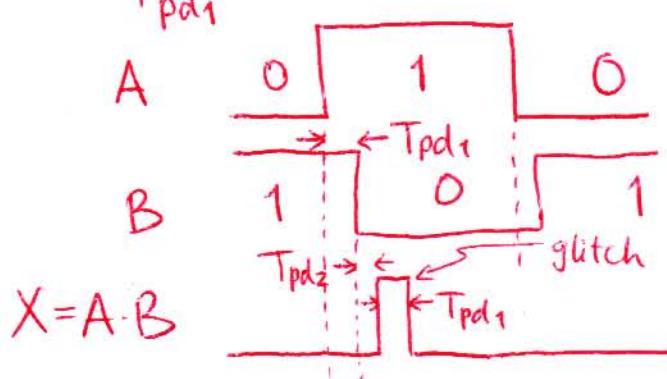

Refer to LTspice example
Simple-digital.asc


(3)

- any complicated fcn can be implemented using the basic gates
- IC's usually come with several copies of gates, e.g. quad 2-in AND's on a single chip
- AND, OR, NOT are not very efficient b/c typically one needs to reuse (mix) different IC's with spare/unused gates

Universal gates


- single type allows to implement arbitrary fcn
- more efficient (fewer chips) \Rightarrow more popular
- two basic types: NAND and NOR

NAND

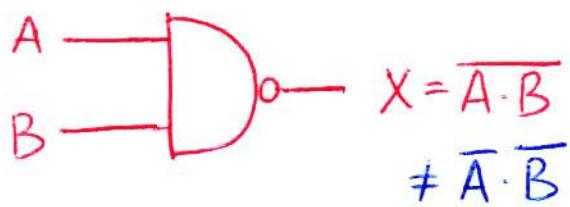


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

A	B	$\overline{A \cdot B}$
0	0	1
0	1	0
1	0	0
1	1	0

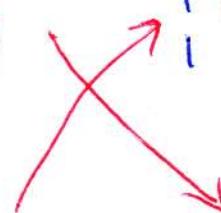

NOR

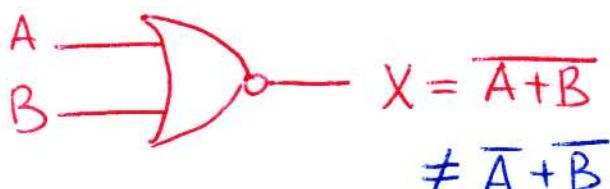

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

A	B	$\overline{A + B}$
0	0	1
0	1	1
1	0	1
1	1	0

(4)

De Morgan Theorem



$$\overline{A+B} = \overline{A} \cdot \overline{B} \quad \text{or} \quad \overline{A \cdot B} = \overline{A} + \overline{B}$$

Alternatively $\overline{\overline{A \cdot B}} = A + B$ or $\overline{\overline{A+B}} = A \cdot B$

two steps to transform digital circuit into an equivalent

- 1) swap AND with OR and vice versa
- 2) invert all inputs and outputs

Examples

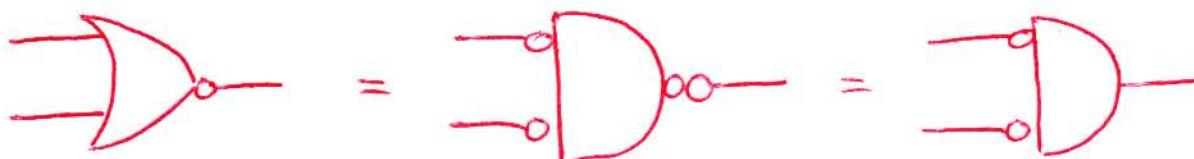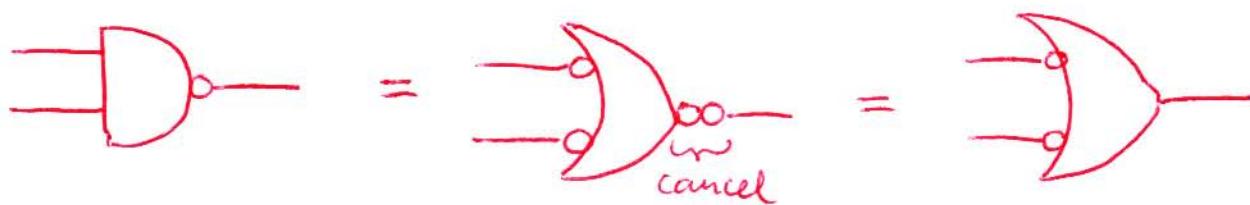

- use to convert one gate type into the other

Rules of Boolean algebra

$$A \cdot \overline{A} = 0$$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A + \overline{A} = 1$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A \cdot B = B \cdot A$$

$$A + B = B + A$$

$$A(BC) = (AB)C$$

$$A + (B+C) = (A+B) + C$$

$$\overline{\overline{A}} = A$$

$$A(B+C) = A \cdot B + A \cdot C$$

$$A + B \cdot C = (A+B)(A+C)$$

prove it using
Boolean algebra rules