 


## Lecture 25

XOR gate

A	B	X
0	0	
0	1	
1	0	
1	1	

Design procedure for combinational logic circuits

1) assign symbols

2) obtain boolean fcn

②

a)

b)

3) [optional]

4) draw the schematic

T	P	S	H
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

minterms -

maxterms -

output =

output =

# Simplifying boolean expressions with Karnaugh maps (3)

Consider 2-input fcn

A	B	minterm
0	0	
0	1	
1	0	
1	1	

$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
$A \cdot \bar{B}$	$A \cdot B$

$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
$A \cdot \bar{B}$	$A \cdot B$

3-input fcn

4-input fcn


-

-

TP  
00 01 11 10  
S<sup>0</sup>  
1

Programmable logic devices

- used to implement

 


- can generate

-  
-

- some PLD types :


Lecture 27

Combinational Logic

 

— outputs depend \_\_\_\_\_  
on present values of inputs


Sequential Circuit

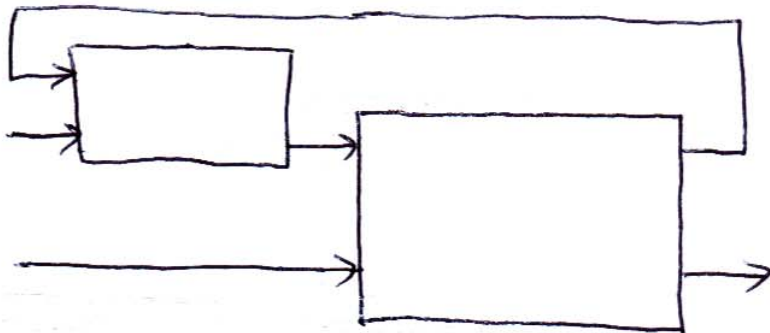



—  
—

RS latch

recall NOR gate

 

2

  


S	R	Q	$\bar{Q}$
0	0		
0	0		
0	1		
0	0		
1	0		
0	0		
1	1		
0	0		

S	R	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

- latch has \_\_\_\_\_ response ,

- contrary to \_\_\_\_\_

③

 


- similar to ball analogy, need a \_\_\_\_\_ to send the latch from one stable state into another
- there exists a min pulse length needed for switching

## Flip-flop

problems with latches :

### Improvements


1) clocked RS flip-flop

 

2) triggering

# Master-slave configuration

(4)

 

CLK  
S  
R  
Y  
Q



Symbol

## 3) direct inputs

