

Lecture 25


XOR gate

not universal but quite useful ; used for addition, parity checking




A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Q: how is it made ?

 

 uses 5 gates (inverter do costs same as AND, OR)



uses only 4 NAND gates (20% cost savings)

① de Morgan
 $\overline{A \cdot B} = \overline{A} + \overline{B}$
 $\overline{A + B} = \overline{A} \cdot \overline{B}$

② $A + B \cdot C = (A + B)(A + C)$
 for any A, B, C

$C = \overline{A \cdot B}$

$D = \overline{A \cdot C} = \overline{A \cdot \overline{A \cdot B}} = \overline{A + \overline{A \cdot B}} = \overline{A} + A \cdot B = \overline{A} + B$

$E = \overline{B \cdot C} = \overline{B \cdot \overline{A \cdot B}} = \overline{B + \overline{A \cdot B}} = \overline{B} + A \cdot B = \overline{B} + A$

Q: prove ?

$F = \overline{A + B} \cdot \overline{B + A}$

$= \overline{A \cdot B} + \overline{B \cdot B} + \overline{A \cdot A} + \overline{B \cdot A} = \overline{A \cdot B} + \overline{B} + \overline{A} + \overline{B \cdot A} = \overline{A \cdot B} + \overline{B} + \overline{A} + \overline{B \cdot A}$

Design procedure for combinational logic circuits

1) assign symbols (bits) to inputs/outputs

- 2) obtain boolean fcn relating inputs/outputs either ②
 - a) by transforming a verbal description
 - b) from input/output truth table
- 3) [Optional] simplify to minimize # of gates
- 4) draw the schematic using (available) gates

E.g. stay Home if Tired but no Prelim or Sick

$$H = T \cdot \bar{P} + S$$

Q: what if just handed a truth table

T	P	S	H	minterms	maxterms
0	0	0	0		$T + P + S$
0	0	1	1	$\bar{T} \cdot \bar{P} \cdot S$	
0	1	0	0		$T + \bar{P} + S$
0	1	1	1	$\bar{T} \cdot P \cdot S$	
1	0	0	1	$T \cdot \bar{P} \cdot \bar{S}$	
1	0	1	1	$\bar{T} \cdot P \cdot \bar{S}$	
1	1	0	0		$\bar{T} + \bar{P} + S$
1	1	1	1	$T \cdot P \cdot S$	

minterms - "1"s in truth table for a unique comb. ("0" otherw.)

maxterms - "0"s for a unique comb. ("1" otherwise)

output = "1" if any of minterms is "1" = \sum_{OR} minterms

= "sum of products"

$$H = \bar{T} \cdot \bar{P} \cdot S + \bar{T} \cdot P \cdot S + T \cdot \bar{P} \cdot \bar{S} + \bar{T} \cdot P \cdot \bar{S} + T \cdot P \cdot S$$

output = "0" if any of maxterms is "0" = \prod_{AND} maxterms

= "product of sums"

$$H = (T + P + S)(T + \bar{P} + S)(\bar{T} + \bar{P} + S)$$



Simplifying boolean expressions with Karnaugh maps (3)

Consider 2-input fcn


A	B	minterm
0	0	$\bar{A} \cdot \bar{B}$
0	1	$\bar{A} \cdot B$
1	0	$A \cdot \bar{B}$
1	1	$A \cdot B$

		B	
		0	1
A	0	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
	1	$A \cdot \bar{B}$	$A \cdot B$

  rearranged truth table
a.k.a. Karnaugh map



e.g. Karnaugh map

 

for $A \cdot B + A \cdot \bar{B} + \bar{A} \cdot B$

3-input fcn $X = f(A, B, C)$

		AB			
		00	01	11	10
C	0				
	1				


gray code

4-input fcn $X = f(A, B, C, D)$

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				


- Karnaugh maps can be used with up to 6 variable
- use computer if more inputs

our example

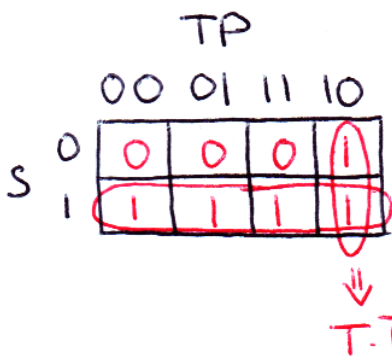

Programmable logic devices (PLDs)

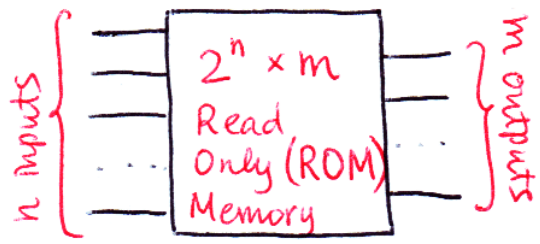- used to implement complicated logic (both combinational & sequential)



- can generate arbitrary truth table of a given size by generating the needed minterms

- usually done by breaking the links, can be reversible or irreversible; stored in "memory"
- e.g. EPROM: erasable programmable ROM: uses charge on tiny caps to store info about the logic; non-volatile (preserved between power cycles); erasable by UV light
- some PLD types:
 - PAL - programmable array logic one-time prog. (OTP), few 100 gates
 - CPLD - complex PLD; ≤ 10 's of thousand gates
 - FPGA - field programmable gate arrays \leq millions of gates; ext. ROM more complex architecture than "sum of products"

see LTspice Exp. 8.2