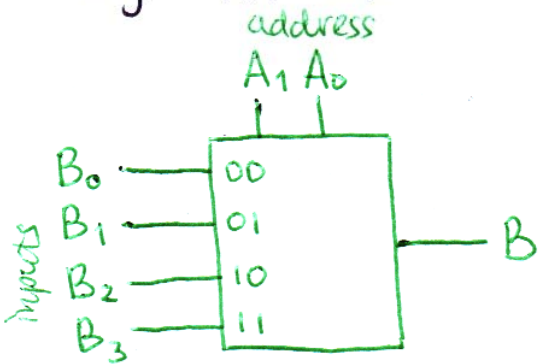


Lecture 28


Multiplexer / Demultiplexer (mux/demux)

- combinational logic used to combine/distribute  $2^n$  inputs/outputs addressed by  $n$  select lines into/from a single line

E.g. 4:1 MUX




1:8 DEMUX

 


Applications

1) sharing bus (= data line)

 


- Mux combines multiple inputs into a single data stream  
Demux splits the data stream into the orig. multiple signals

Also : can use 3-state logic

 

P<sub>1-4</sub> - some peripheral logic devices

 - cannot share usual O/I devices without confusion
- each device must have tristate buffer, which effectively removes all but one device from the bus




3 states:  
 { 0/1 logic  
 { Z high Z (open circuit)

### 2) Arbitrary logic implementation (cf. PLD)

2<sup>n</sup>:1 mux can represent arbitrary n-input fcn

E.g. XOR

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

 

### 3) Encoding / decoding (encoder/decoder - another name for mux/demux)


- turn one form of digital info representation into another / and back

BCD ↔ binary  
 Gray ↔ decimal  
 .....

Example

Priority encoder

e.g. HW2 problem 3

 


output from parallel ADC



$X_2 X_1 X_0$	$Y_1 Y_0$
000	00
001	01
011	10
111	11

Need to convert to binary  
(= priority encoder)

implementation  
with two 8:1 muxes

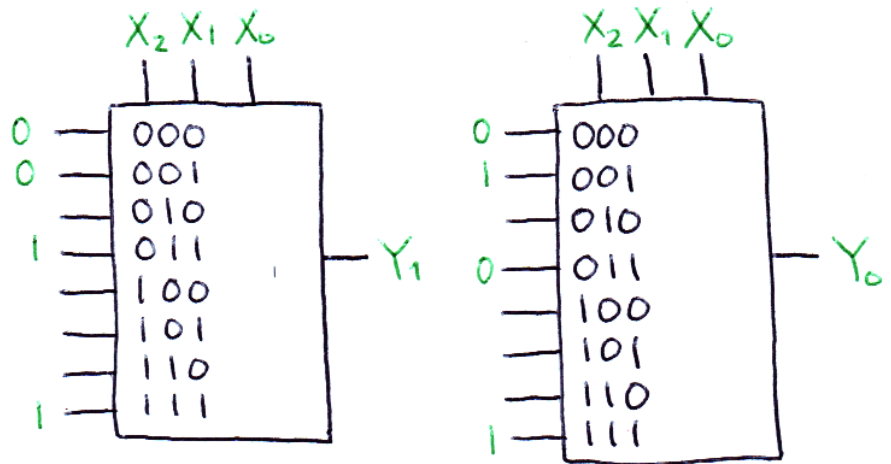

  
Priority decoder? E.g. strength bar display



# Flip-flops (contd.)


so far discussed RS flip-flop

## D flip-flop (data - 1 bit memory)

 


D	$Q_{n+1} \leftarrow$ clock tick #
0	0
1	1

## JK flip-flop

 

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\overline{Q_n}$

## T flip-flop (toggle)

 

$$Q_{n+1} = \overline{Q_n} \text{ when } EN = 1$$

- any type of FF (+ combinational gates)  
 can be converted into any other type

