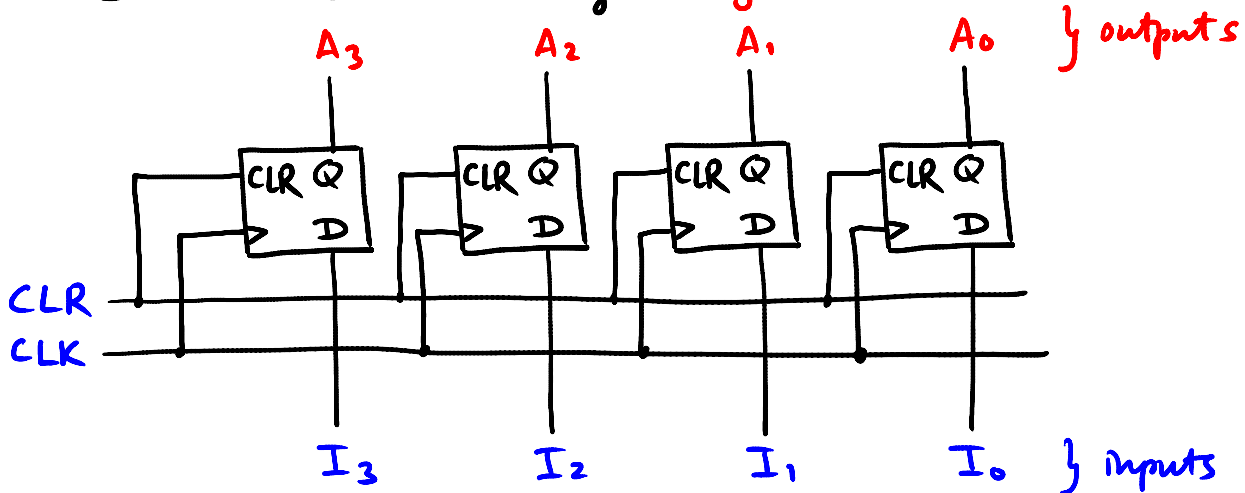


P3360/AEP3630
Lecture 29

FF applications


① Parallel data storage : register



* inputs ($I_0 - I_3$) at \uparrow edge of CLK are stored in the register

* CLR input clears the data asynchronously

② Shift register

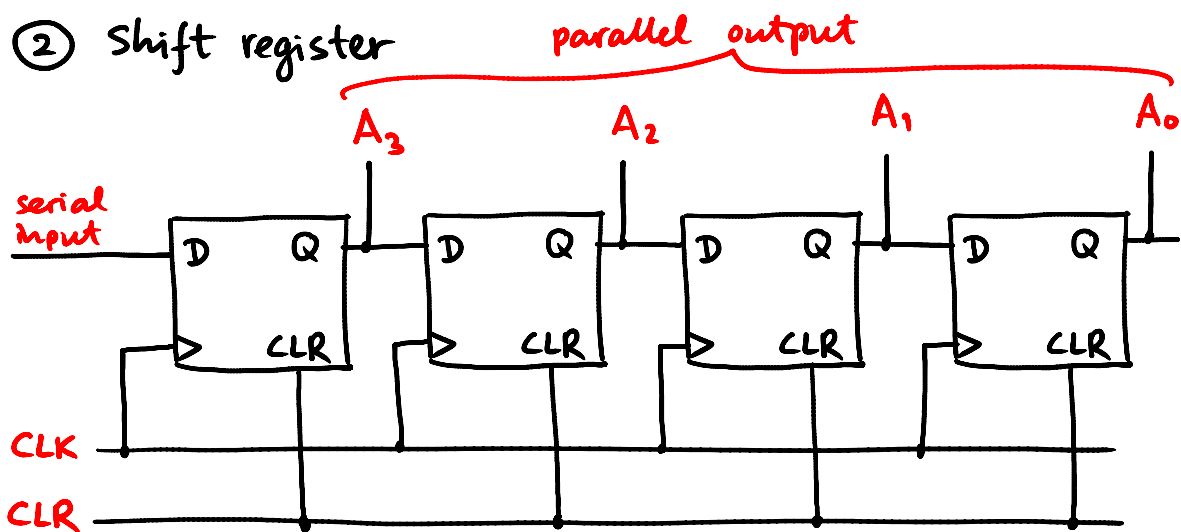

* data shifts right after each CLK pulse

Apps :

- * serial to parallel data conversion
(transmit digit. info over serial connection)
- * divide / multiply by 2
(same as shift right / left)
- * programmable delay

Timing terminology

transition time = time for FF output to go
 $0 \rightarrow 1$ or $1 \rightarrow 0$ after the
input change (c.f. prop. delay)

setup time = min time inputs must be stable
before clock pulse enables FF (~20ns)

hold time = min time inputs must be stable
after the clock pulse enables FF
(~100ps, essentially 0)

③ Counters, ripple counters (asynchronous)

T flip-flops ganged together

asynchronous vs. synchronous counters

↙ "domino effect" :
see LT spice ex.


0111 \rightarrow 1000

actually can work as

0111 \rightarrow 0110 \rightarrow 0100 \rightarrow 0000 \rightarrow 1000
← glitch →

Timing circuits & clocks

 - * many cases when one needs to output a pulse at/after some event



- * clocks are important to synchronize sequential circuits


(need stable period, sharp rise/fall time)

Q: why need a precise clock?

A: E.g. watch "Longitude" (about John Harrison)


555 Timer

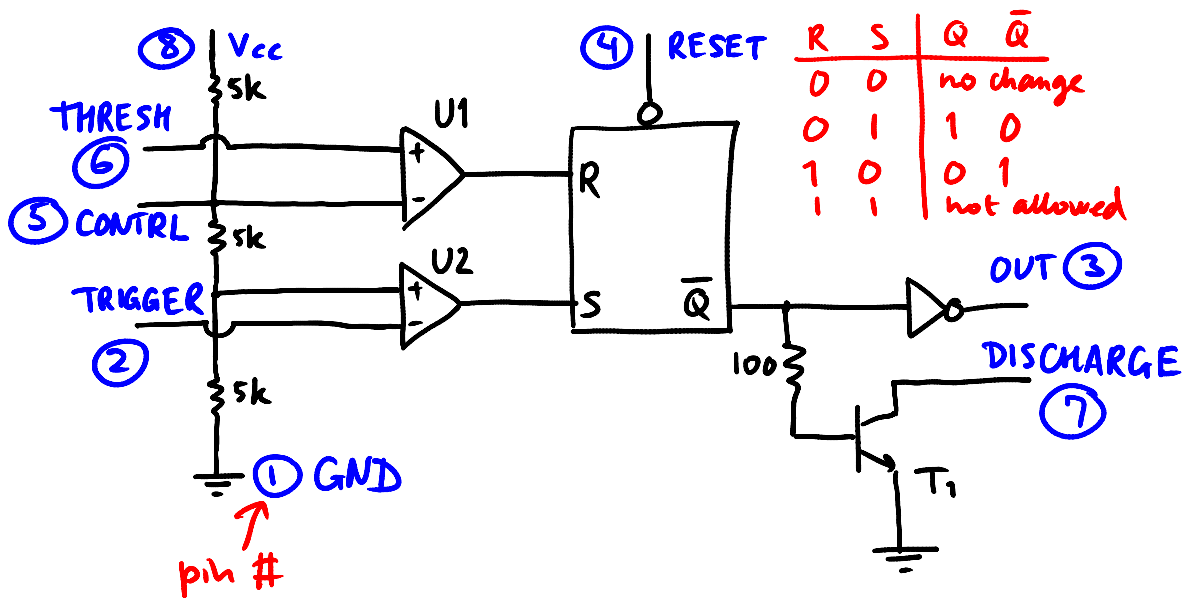- * 8 DIP package (like 741 op-amp)
- * in part analog, in part digital
- * can be wired as one-shot
or as a clock (not very precise)



2 comparators $\frac{2}{3}V_{cc}$ & $\frac{1}{3}V_{cc}$ RS latch saturated switch
 $T_1 = ON$ if $\bar{Q} = 1$
 $T_1 = OFF$ if $\bar{Q} = 0$

Simplified symbol

 

supply voltage
 $4.5V \leq V_{cc} \leq 16V$
 output current
 $(I_{out})_{max} \sim 200mA$
drives small loads all by itself

✖ as a one-shot : $T_w \sim 1\mu s \rightarrow 100s$
 ✖ as a clock : $f \sim 0.01Hz \rightarrow 1MHz$