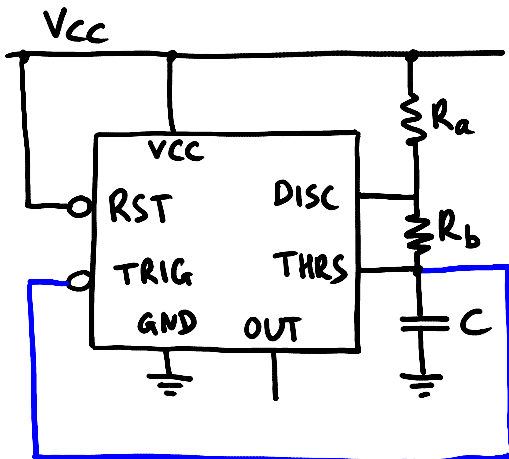



Oscillator configuration of 555



step 1) assume  $v_c = 0$  @  $t = 0$

$$\left. \begin{aligned} v_{\text{trig}} = 0 < \frac{1}{3}V_{\text{cc}} \quad , \Rightarrow S = 1 \\ v_{\text{th}} = 0 < \frac{2}{3}V_{\text{cc}} \quad , \Rightarrow R = 0 \end{aligned} \right\} \begin{aligned} \bar{Q} = \text{LO}, T_1 = \text{OFF} \\ \text{OUT} = \text{HI} \end{aligned}$$

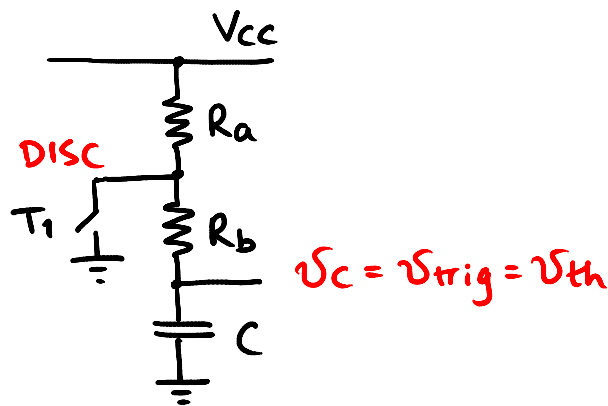
$\Rightarrow C$  charges to  $V_{\text{cc}}$  thru  $R_a + R_b$



step 2) when  $v_c > \frac{1}{3}V_{\text{cc}}$  ,  $S = 0$  ,  $\bar{Q}$  unchanged

step 3) when  $v_c \geq \frac{2}{3} V_{cc}$ ,  $R=1$ ,  $\overline{Q}=HI$ ,  $OUT=LO$   
 $T_1=ON$

C discharges to 0 thru  $R_b$

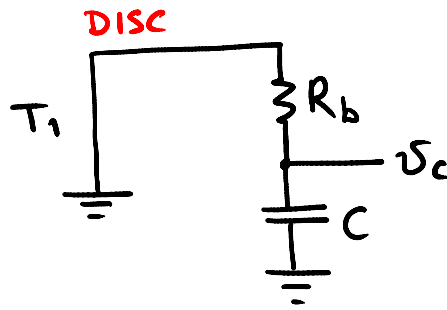


step 4) when  $v_c < \frac{2}{3} V_{cc}$ ,  $R=0$ ,  $\overline{Q}$  unchanged

step 5) when  $v_c < \frac{1}{3} V_{cc}$ ,  $S=1$ ,  $\overline{Q}=LO$ ,  $OUT=HI$   
 $T_1=OFF$

C charges back to  $V_{cc}$  thru  $R_a+R_b$

Repeat step 2)

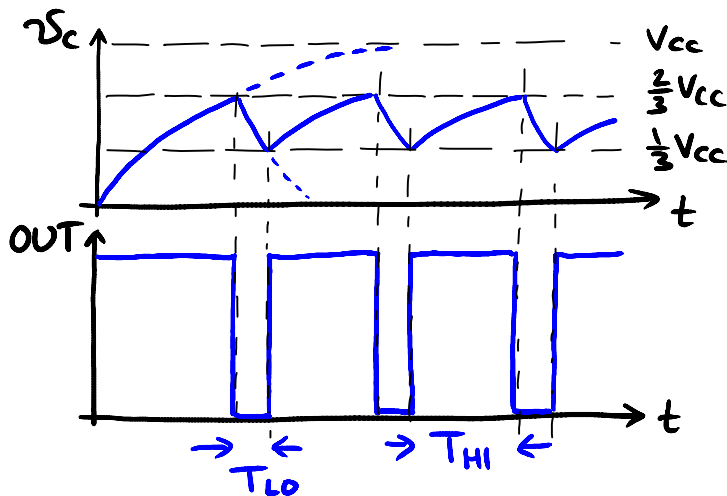

\*  $v_c$  is stuck between  $\frac{1}{3}$  and  $\frac{2}{3} V_{cc}$

\* from cap. charging eqn.

$$T_{H1} = (R_a + R_b) C \ln 2$$

$$T_{L0} = R_b C \ln 2$$

$$f = \frac{1}{T_{H1} + T_{L0}} = \frac{1.44}{(R_a + 2R_b) C}$$

\*  $f$  does not depend on  $V_{cc}$  (good!)

\*  $f$  is stable ( $< 1\%$ ) mainly temp. fluctuations


Q: what if want  $T_{HI} < T_{LO}$ ?

1) invert OUT  $\rightarrow \triangleright$

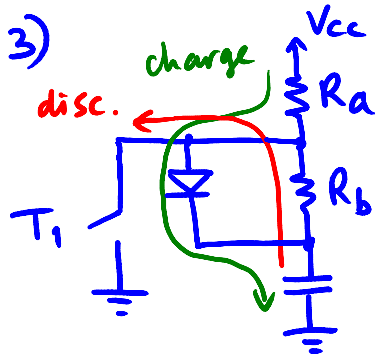2) you can make  $R_a \ll R_b$  to get

a duty factor 50%

(but remember to keep  $R_a \sim 1k\Omega$  to limit current thru  $T_1$ )



$$\tau_{disc} = R_b C$$

( $T_1 = ON, D = OFF$ )

$$\tau_{charg.} = R_a C$$

( $T_1 = OFF, D = ON$ )