

Lecture 40

Noise in op-amps

Recall Johnson noise



$$(\mathcal{V}_n)_{\text{rms}} = \sqrt{4k_B T R B}$$


Noise terms:

—

—

—

Ex.

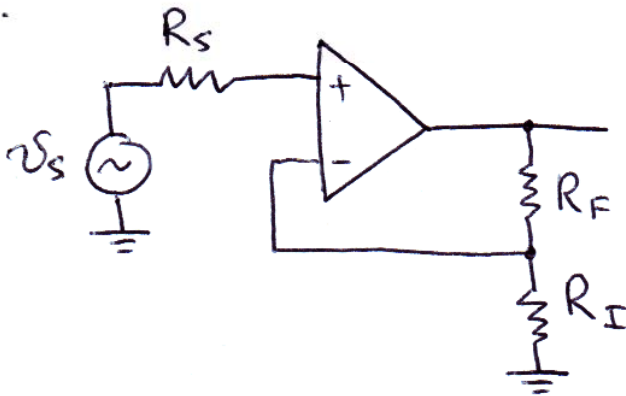

E.g. LF356

$$e_n \sim 12 \text{ nV}/\sqrt{\text{Hz}}$$

$$i_n^\pm \sim 0.01 \text{ pA}/\sqrt{\text{Hz}}$$

$$R_I \approx 1 \text{ k}\Omega$$

$$R_F = 100 \text{ k}\Omega$$

$$R_s \approx 5 \text{ k}\Omega$$

II Interference

- noise due to sources _____ to the circuit

-

Sources

-

-

-

-

-

Coupling mechanisms

① Mechanical

-


-

-

-

② Capacitive coupling

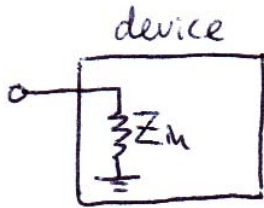- any two conductors connected by _____
have capacitance b/w them



To reduce


-
-
-
-

Lecture 41

③ Magnetic coupling

- time varying B-field induces voltage _____
- low freq. B-field is not easily shielded by metals

To reduce
- avoid

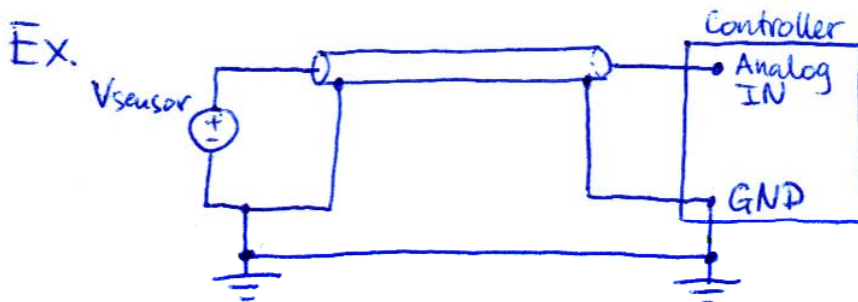

②

- use

- use magnetic shielding :

- use isolation transformers
opto-isolators

④ RF coupling

- wire leads, circuit parts can act as resonant pickups


To reduce

- use shielding

- keep short leads

⑤ Resistive coupling

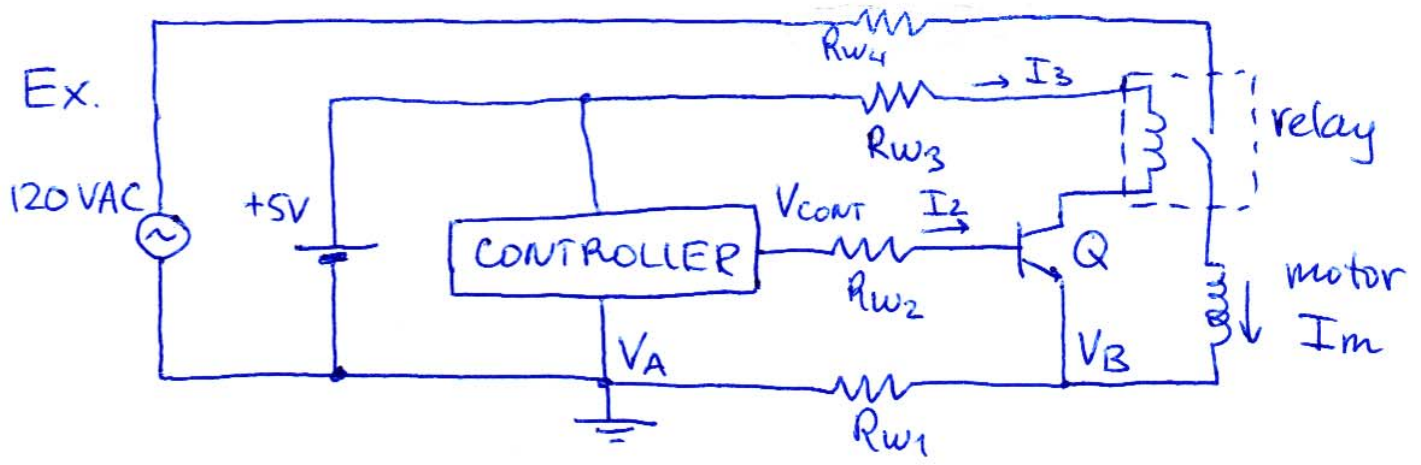- wires \neq equipotentials, have finite resistance
- \Rightarrow currents flowing thru ground lines can generate



To reduce

- use low resistance ground wires (copper busbars in extreme cases)
- separate grounds for _____ level circuit parts

PHYS 3360 / AEP 3630


Lecture 42

Detecting signal buried in noise

For poor S/N signal, recovery is often possible

⇒ SNR can be made very large

signal averaging - example of _____

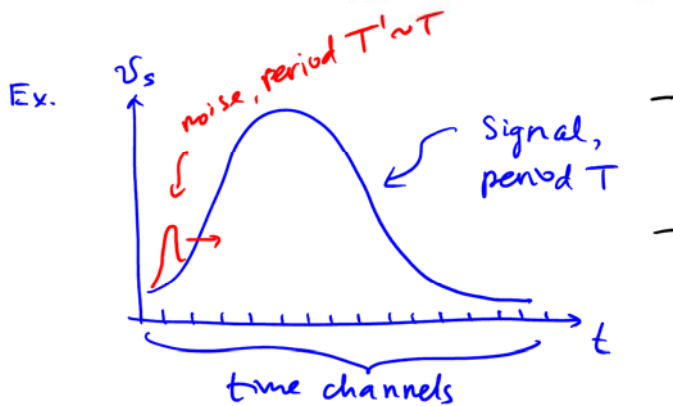


$$SNR_{dB} = 10 \log_{10} \left(\frac{P_s}{P_n} \right)$$

SNR increases 3dB for each _____

Lock-in amplification

- most signals can be made repetitive
- if signal can be addl. made periodic,
can use lock-in amp


Phase sensitive detector:

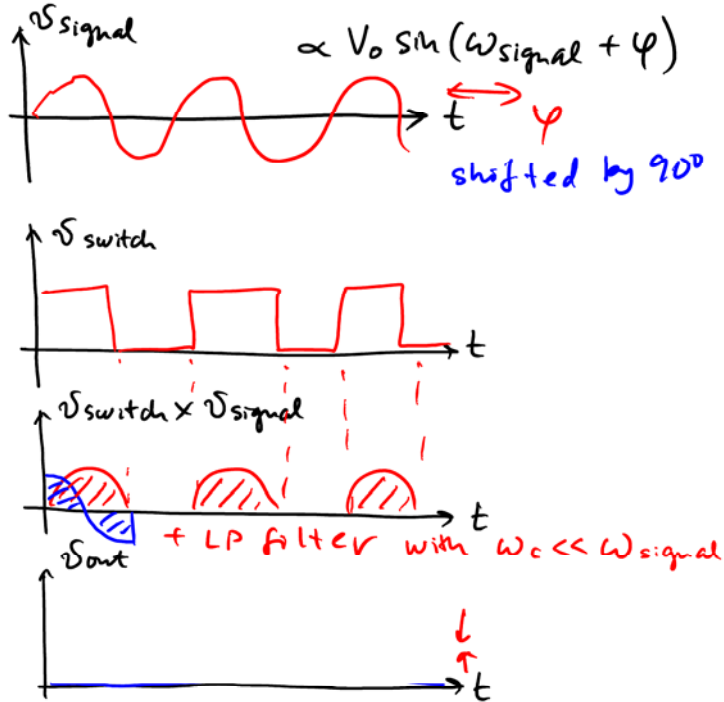

Lock-in amp

- 1) system response signal of interest V_0
- 2) PSD:

3) LP filter after PSD

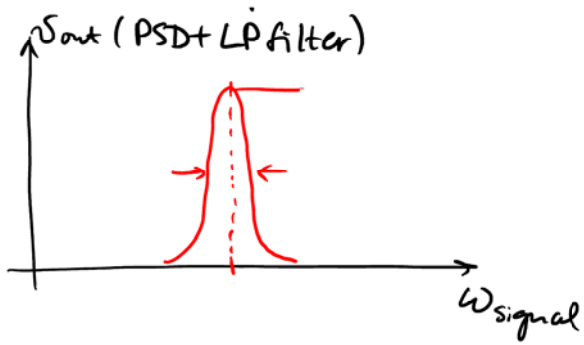

Application Example

you are measuring a very weak signal, e.g.

fluorescence

