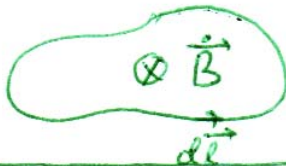


Lecture 41

③ Magnetic coupling

(electric hum in audio equip. noise becomes audible, similar to transformer's hum)

Faraday law



$$\oint \vec{E} \cdot d\vec{l} = - \frac{d}{dt} \int \vec{B} \cdot d\vec{A} = - \frac{d\Phi_B}{dt}$$

Ex. $\dot{B} \sim \text{mV/m}^2$ due to 60Hz

(in most buildings due to power lines, light fixtures)

with $R \sim 0.1 \Omega$ wire, $i_n \sim 10 \text{mA}$ for 1m^2 loop

- time varying B-field induces voltage around any closed loop

- low freq. B-field is not easily shielded by metals

$$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}$$

δ → $\frac{1}{2}$ atten. of B in material
 ← conductivity
 ← magn. permeability



- skin depth

E.g. need 0.43" Al for $\frac{1}{2}$ atten. of 60Hz fields

To reduce

- avoid large enclosed conducting paths (e.g. ground loops)

Ex.

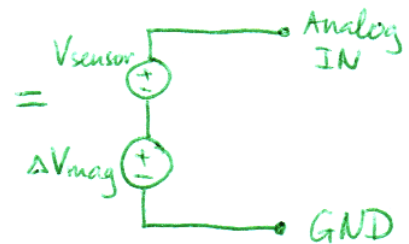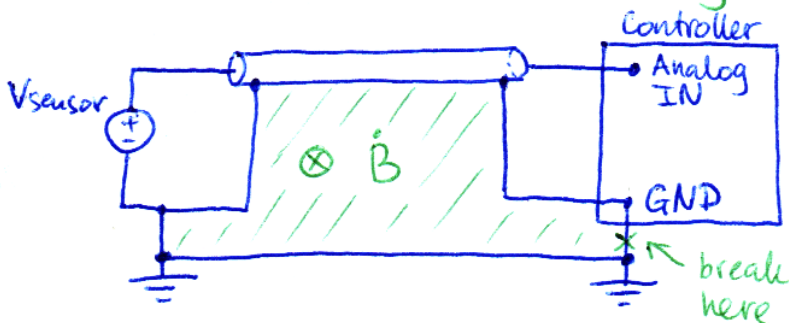

- use coax or twisted pair




- induced fields cancel in successive twists
- small enclosed area

- use magnetic shielding: μ -metal (Ni-Fe alloy $\mu \sim 10^5 \mu_0$)
shorts out magn. flux

1:1 transformers

- use isolation transformers
opto-isolators

} break ground loops
opto-isolator

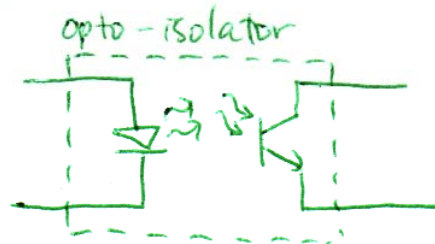

uses short optical transmission path

4) RF coupling

- wire leads, circuit parts can act as resonant pickups (antennas) \Rightarrow high freq. noise (VHF $\lambda \sim 1-10m$ FM, TV

$\frac{\lambda}{2}$ antenna or $\frac{\lambda}{4}$ antenna

(near conducting surface)

UHF 0.1-1m TV, wireless
SHF 0.01-0.1m cell-phones)


\Rightarrow very effective in picking up the RF

To reduce

- use shielding (very effective)
- keep short leads

5 Resistive coupling

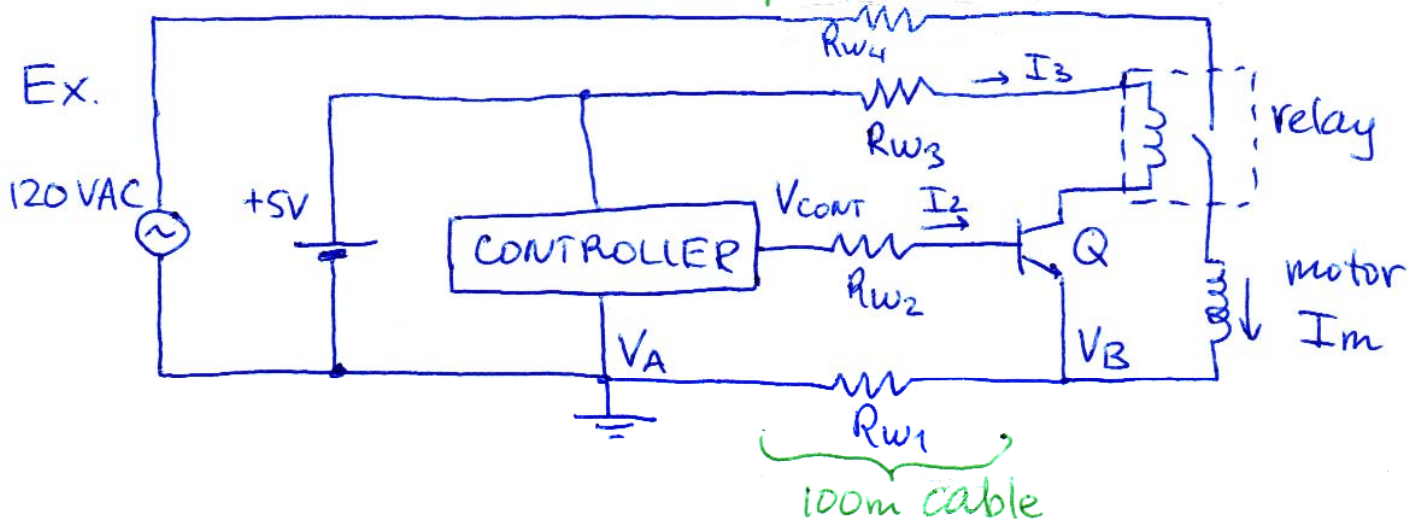- wires \neq equipotentials, have finite resistance
- \Rightarrow currents flowing thru ground lines can generate voltages in another part of the circuit



$R_w \sim 0.3 \Omega$

$Q = ON: I_m \sim 20A$ when starting $\Rightarrow I_2, I_3$
 \leftarrow sees low resistivity wire R_{w1} and chooses to go there

$\Rightarrow V_B - V_A \sim 20A \cdot 0.3 \Omega \sim 6V$

since $V_{CONT} - V_A < 0.6V$, Q goes OFF when motor trying to start

To reduce

- use low resistance ground wires (copper busbars in extreme cases)
- separate grounds for low and high level circuit parts

