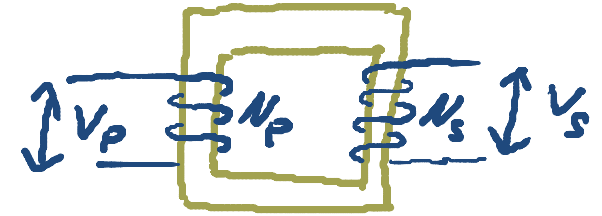


# Recap

## Lecture 24

### • Transformers:

- Transformation of voltage:  $V_s = \frac{N_s}{N_p} V_p$
- Transformation of current:  $i_s = \frac{N_p}{N_s} i_p$



$$\Phi_p = \Phi_s$$

### • Ideal LC-circuit:

Energy oscillates between electric and magnetic fields, but the total sum of energy remains constant:




$$U_{\text{total}} = U_E(t) + U_B(t) = \frac{q(t)^2}{2C} + \frac{L}{2} i(t)^2$$

$$= \frac{1}{2} \frac{Q_{\text{max}}^2}{C} = \text{const}$$

oscillation of charge:  $q(t) = Q_{\text{max}} \cos(\omega t + \phi)$

oscillation of current:  $i(t) = \frac{dq}{dt} = -\omega Q_{\text{max}} \sin(\omega t + \phi)$

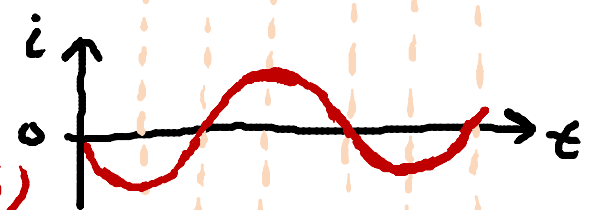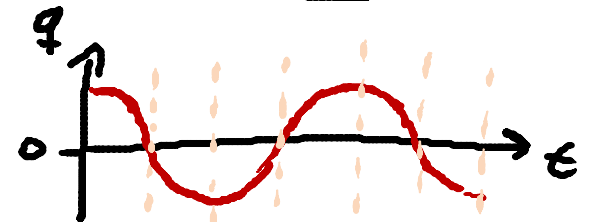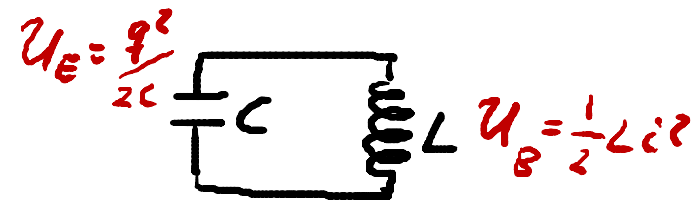angular frequency:  $\omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$



# Today:

- RLC circuit:  
damping and driven
- Another look at  
Faraday's law
- Next time: Maxwell's  
equations

$$\oint \mathbf{E} \cdot d\mathbf{A} = \frac{q_{enc}}{\epsilon_0}$$

$$\oint \mathbf{B} \cdot d\mathbf{A} = 0$$


$$\oint \mathbf{E} \cdot d\mathbf{s} = -\frac{d\Phi_B}{dt}$$

$$\oint \mathbf{B} \cdot d\mathbf{s} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt} + \mu_0 i_{enc}$$



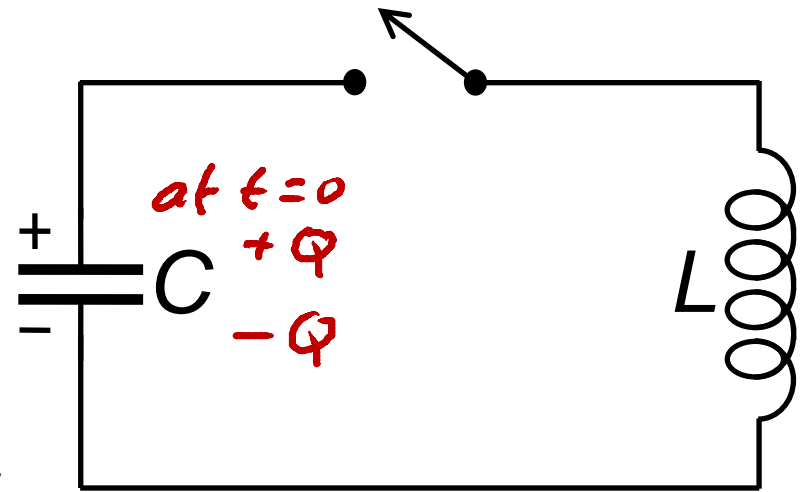
# Ideal LC circuit (no resistance):

The capacitor starts with charge  $q = Q > 0$  with the polarity shown. At time  $t = 0$  the switch is closed and current  $i \equiv dq/dt$  flows in the circuit.



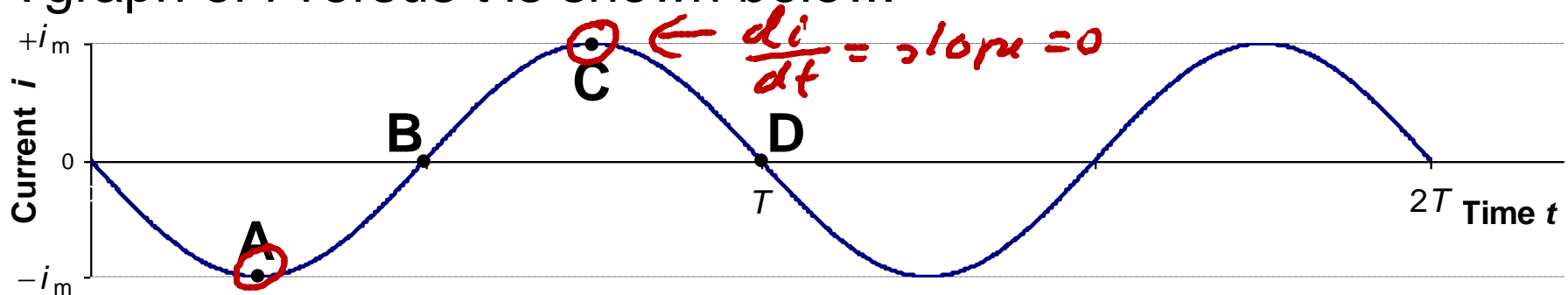A graph of  $i$  versus  $t$  is shown below.




$$\Delta V_L = L \frac{di}{dt} \quad \Rightarrow \quad \Delta V_L = 0 \text{ when } \frac{di}{dt} = \text{slope} = 0$$


Which of the labeled points correspond(s) to **no voltage across the inductor**?

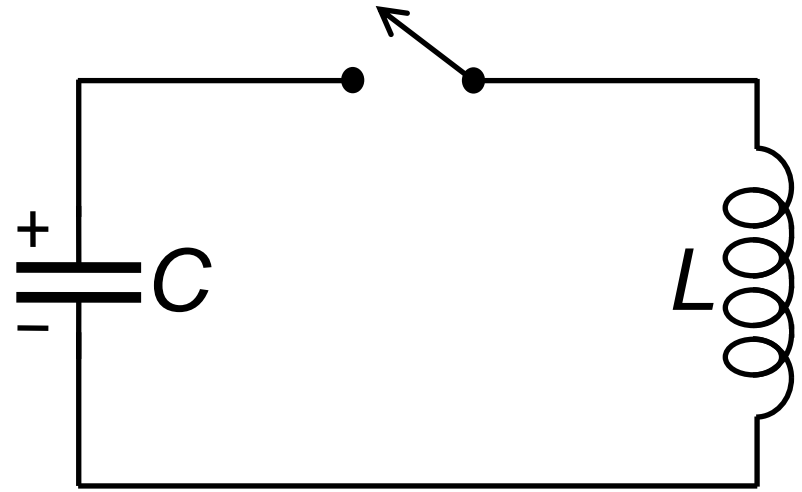- A. A      B. B      C. C      D. D      **E. Both A & C**

The capacitor starts with charge  $q = Q > 0$  with the polarity shown. At time  $t = 0$  the switch is closed and current  $i \equiv dq/dt$  flows in the circuit.



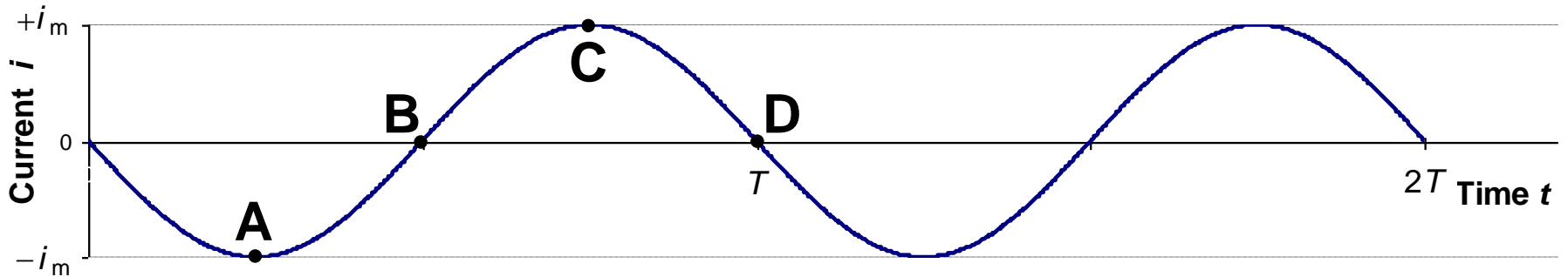A graph of  $i$  versus  $t$  is shown below.




loop rule:  $\Delta V_c + \Delta V_L = 0$   
 $= 0$  at A and C


Which of the labeled points correspond(s) to **no voltage across the capacitor?**

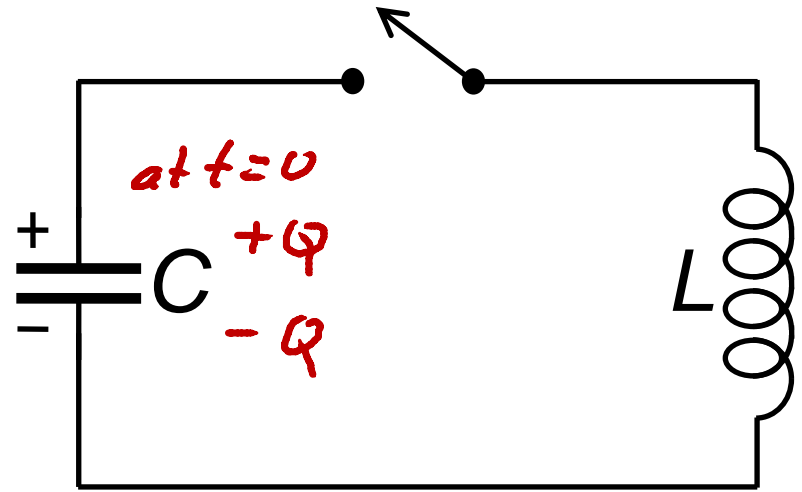- A. A    ~~B. B~~    C. C    ~~D. D~~    **E. Both A & C**

The capacitor starts with charge  $q = Q > 0$  with the polarity shown. At time  $t = 0$  the switch is closed and current  $i \equiv dq/dt$  flows in the circuit.



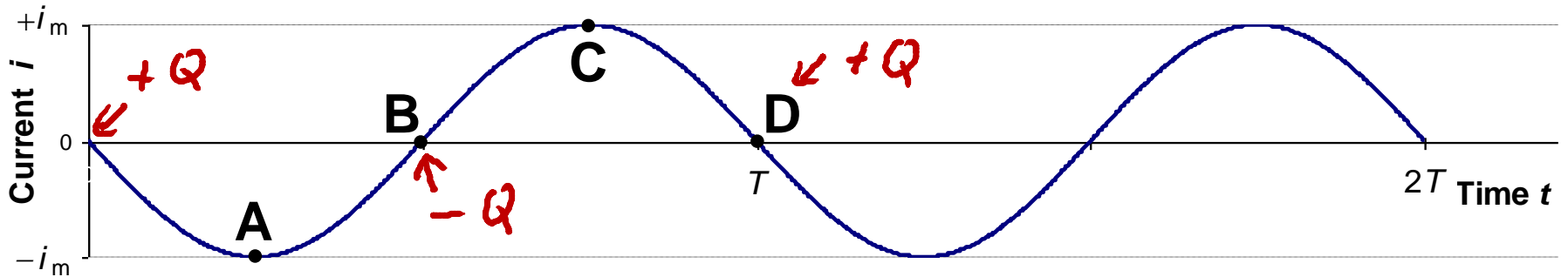
A graph of  $i$  versus  $t$  is shown below.




Which of the labeled points correspond(s) to **charge  $+Q$  on the capacitor?**

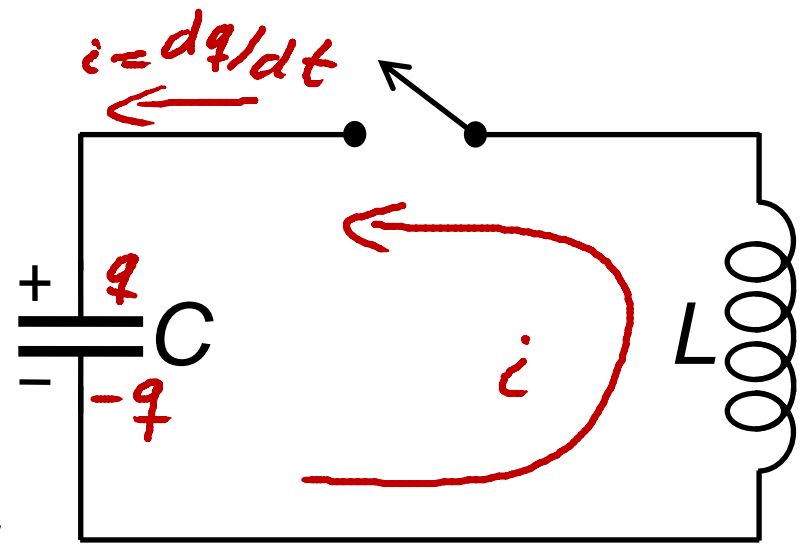- A. A      B. B      C. C      **D. D**      E. Both A & C

The capacitor starts with charge  $q = Q > 0$  with the polarity shown. At time  $t = 0$  the switch is closed and current  $i \equiv dq/dt$  flows in the circuit.



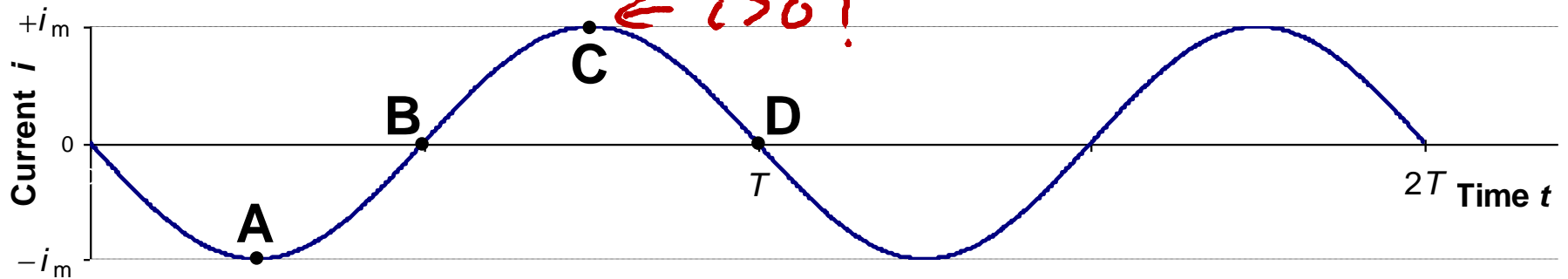
A graph of  $i$  versus  $t$  is shown below.



Which of the labeled points correspond(s) to **counterclockwise current flow in the circuit**?

- ~~A. A~~      ~~B. B~~      **C. C**      ~~D. D~~      ~~E. Both A & C~~

# RLC circuit:

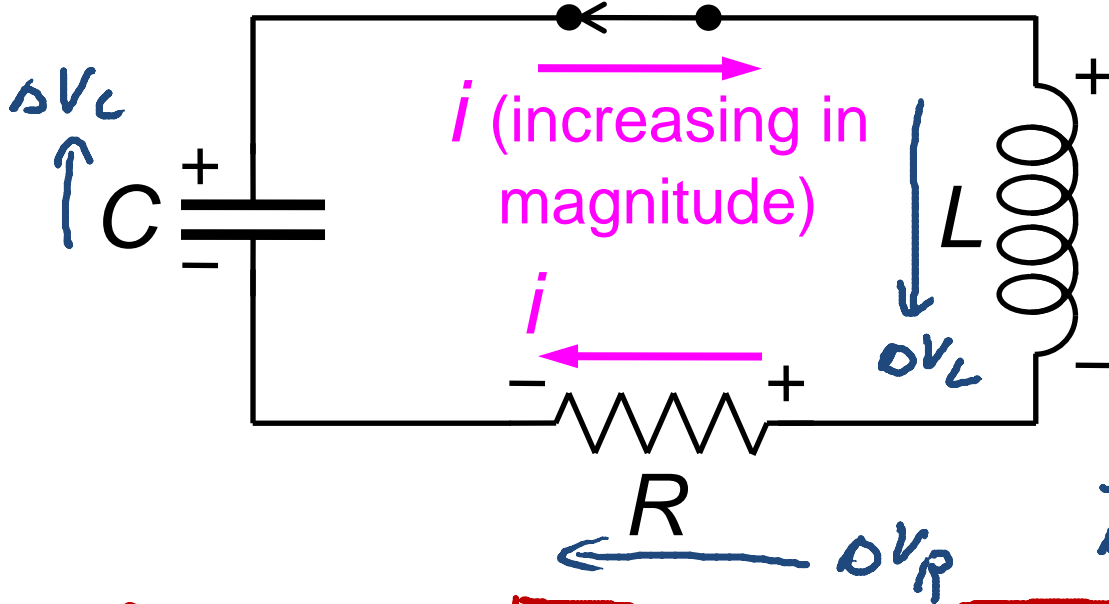

- Resistance  $R$ 
  - $\Rightarrow$  dissipate power
  - $\Rightarrow$  damping of oscillation!
- loop rule now gives:


$$\underbrace{\frac{q}{C}}_{\Delta V_C} + L \underbrace{\frac{d^2 q}{dt^2}}_{\Delta V_L} + \underbrace{\frac{dq}{dt} R}_{\Delta V_R} = 0$$

$\Rightarrow$  solution:  $q(t) = Q_0 e^{-t/2\tau} \cos(\omega' t + \phi)$

with energy decay time constant  $\tau_{RLC} = L/R$

and  $\omega' = \sqrt{\omega_0^2 - (R/2L)^2}$

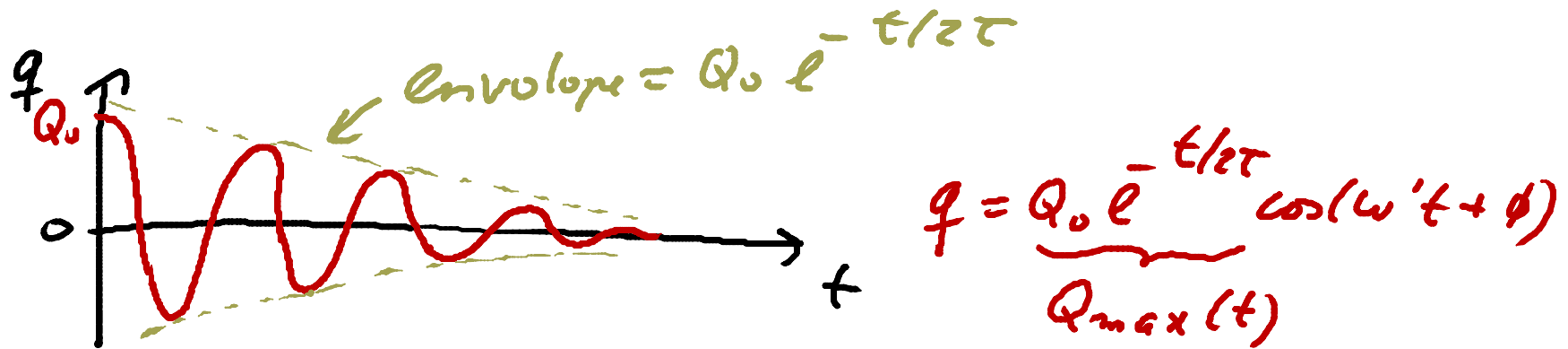$\Rightarrow$  for small  $R$ :  $\omega' \approx \omega_0 = \frac{1}{\sqrt{LC}}$





$\Rightarrow$   $U_{\text{total}}$  (total energy stored in circuit)  
also decreases exponentially:

$$\underline{U_{\text{total}}(t)} = \frac{1}{2C} Q_{\max}(t)^2 = \frac{1}{2C} Q_0^2 e^{-t/\tau}$$

"energy  
decay  
time  
constant"  
 $\tau = L/R$



# Driven RLC circuit:

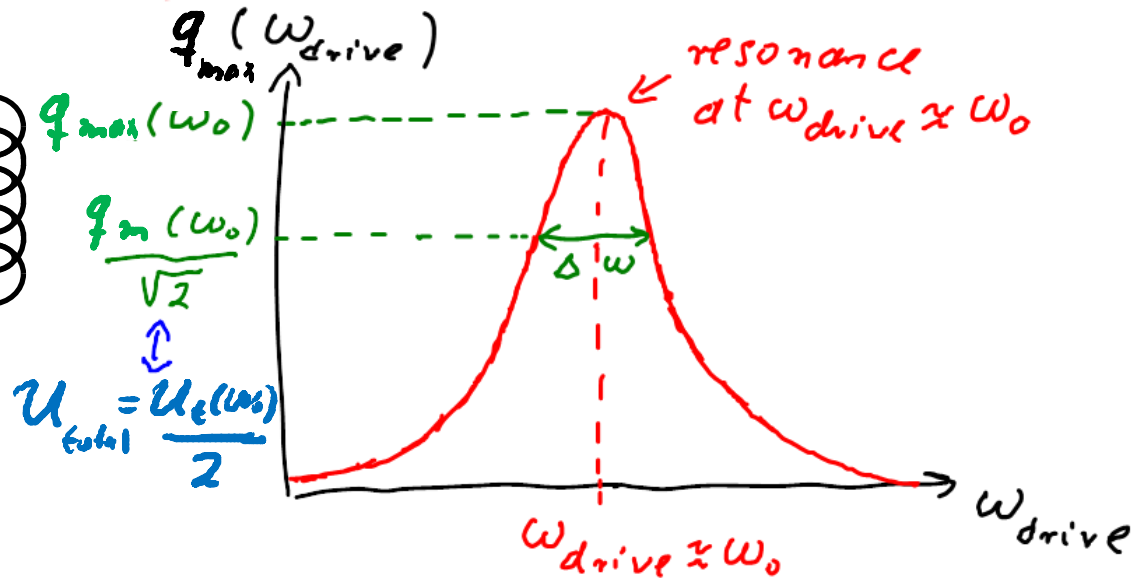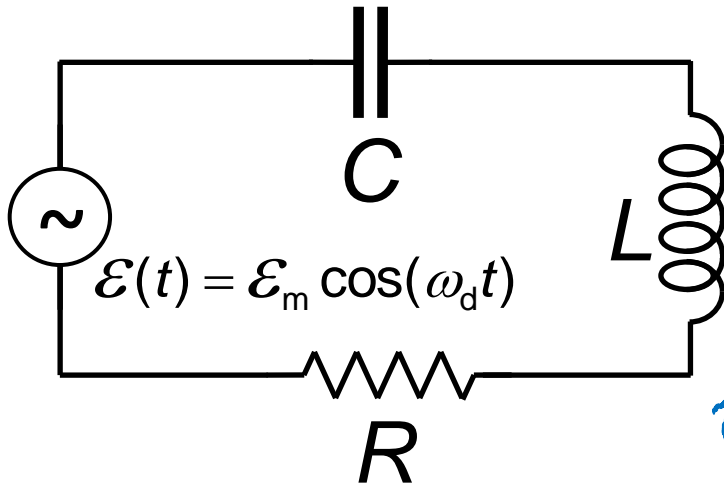

Current will oscillate at the driving frequency:  $f_d = \omega_d / (2\pi)$

- Maximum current amplitude when driving frequency matches natural frequency of circuit:

$$f_d = f_0 \frac{1}{2\pi\sqrt{LC}} \quad (\text{resonance})$$

• resonance width


$$\Delta\omega = \frac{1}{\tau} \quad \text{energy decay time}$$

• define quality factor:

$$Q \equiv \frac{\omega_0}{\Delta\omega} = \omega_0 \tau = \frac{2\pi\tau}{T_0}$$
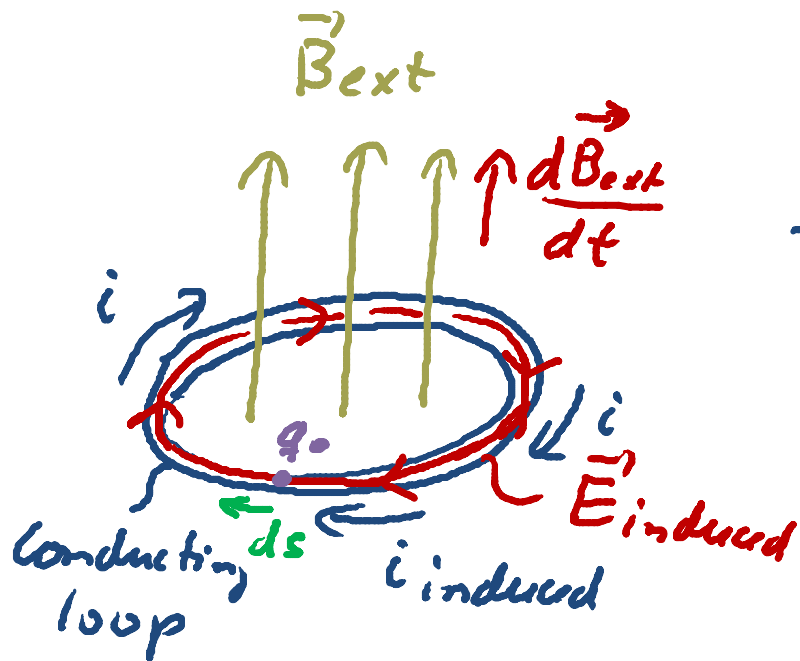
# Another look at Faraday's Law:

A changing magnetic field induces an electric field



- Induced electric field drives the current in the conducting loop ( $i = \mathcal{E}/R$ )
- Work done by the electric field on a charge  $q_0$

$$dW_{on\ q_0\ by\ \vec{E}} = \vec{F} \cdot d\vec{s} = q_0 \vec{E} \cdot d\vec{s}$$


$\Rightarrow$  Total work done on charge  $q_0$  while it moves around the loop:

$$\underline{W_{on\ q_0\ by\ \vec{E}}} = \oint_{\text{around loop}} dW = \oint_{\text{around loop}} q_0 \vec{E} \cdot d\vec{s} = \oint q_0 E_{||} ds$$

But: induced emf =  $\mathcal{E} \equiv \frac{W_{on q_0}}{q_0} = \frac{\text{work done on charge}}{\text{charge}}$   
in loop

so:  $\mathcal{E} = \frac{W_{on q_0}}{q_0} = \oint_{\text{closed path}} \vec{E} \cdot d\vec{s}$

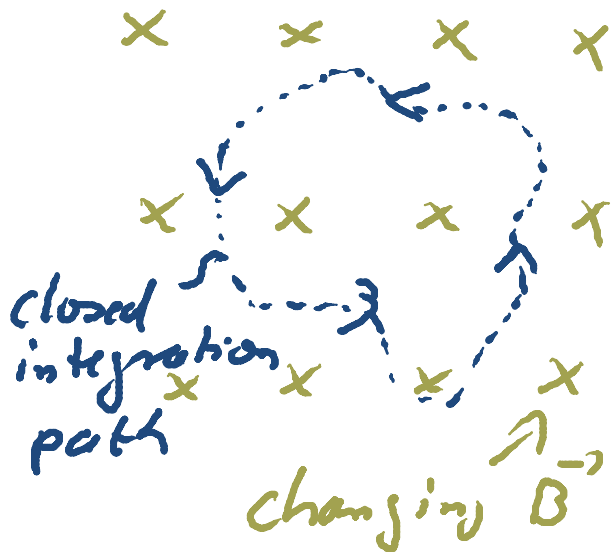$\Rightarrow$  Can write Faraday's Law  $\mathcal{E}_{\text{ind}} = - \frac{d\Phi_B}{dt}$  in the following way:



induced  $\vec{E}$

$$\oint_{\text{closed path}} \vec{E} \cdot d\vec{s} = - \frac{d\Phi_B}{dt}$$

closed path

rate of change of magnetic flux through interior of closed path

This is true whether or not the conducting loop is present!

spatially uniform  $\vec{B}$


The magnetic field is confined to the cylindrical region shown and is spatially uniform but its magnitude is increasing with time.

When Faraday's law,

$$\oint \vec{E} \cdot d\vec{S} = -\frac{d\Phi_B}{dt},$$

is applied to the circular integration path, which best describes  $E_s$ , the component of the electric field along the direction of  $d\vec{S}$  ?
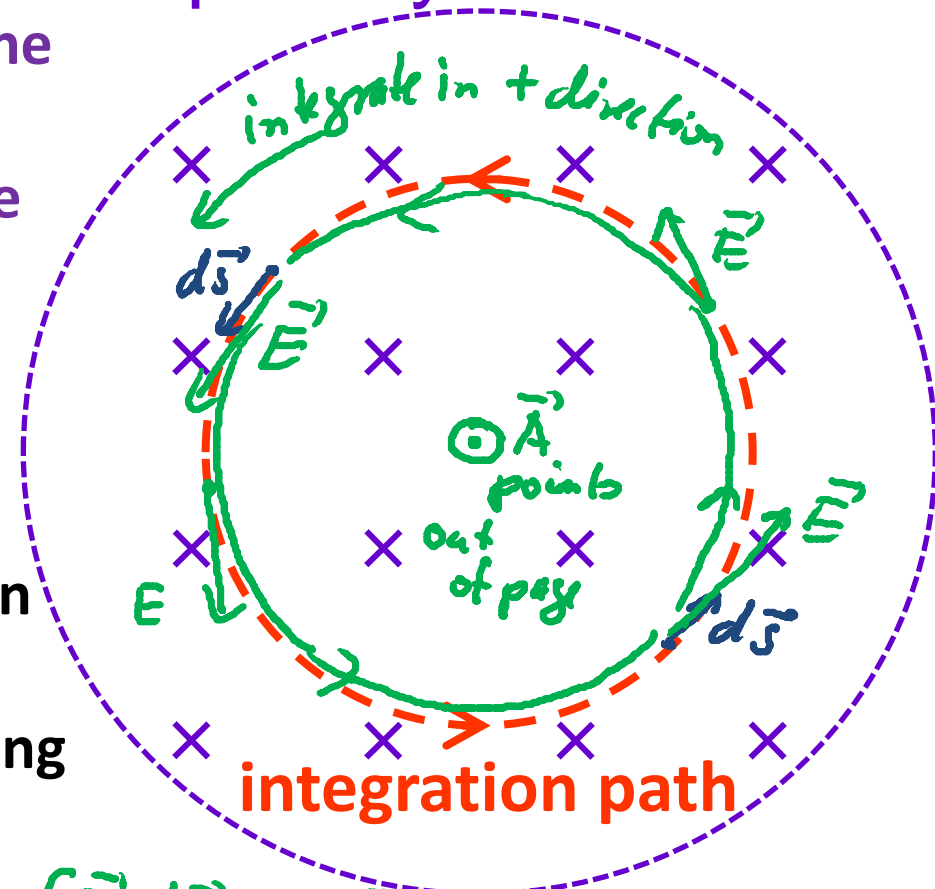
$$\Phi_B = \vec{B} \cdot \vec{A} < 0 \Rightarrow \frac{d\Phi_B}{dt} < 0 \text{ (inc)} \Rightarrow \oint \vec{E} \cdot d\vec{S} = -d\Phi_B/dt > 0$$



A.  $E_s > 0$

B.  $E_s < 0$

C.  $E_s = 0$

D.  $E_s$  depends on where  $d\vec{S}$  is along the integration path.


spatially uniform  $\vec{B}$

The magnetic field is confined to the cylindrical region shown and is spatially uniform but its magnitude is increasing with time.

When Faraday's law,

$$\oint \vec{E} \cdot d\vec{S} = -\frac{d\Phi_B}{dt},$$

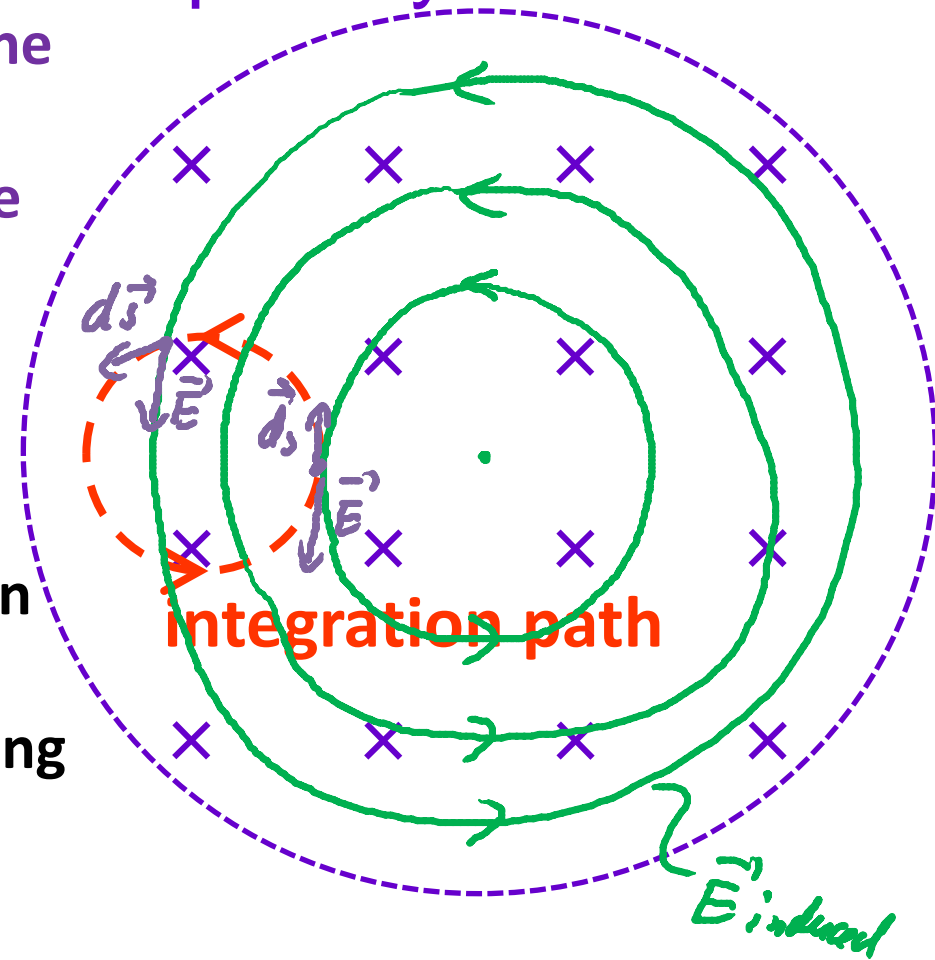is applied to the circular integration path, which best describes  $E_s$ , the component of the electric field along the direction of  $d\vec{S}$  ?



~~A.~~  $E_s > 0$

B.  $E_s < 0$

C.  $E_s = 0$

D.  $E_s$  depends on where  $d\vec{S}$  is along the integration path.

# Ampère - Maxwell Law:

Symmetry is powerful in physics!

changing magnetic field produces an electric field

⇓ Symmetry

changing electric field produces a magnetic field

Faraday's Law for  
magnetic induction

$$\oint_{\text{closed path}} \vec{E} \cdot d\vec{s} = - \frac{d\Phi_B}{dt}$$

Maxwell's Law for  
electric induction

$$\Leftrightarrow \oint_{\text{closed path}} \vec{B} \cdot d\vec{s} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$


rate of change of  
electric flux through  
interior of closed path

also have Ampère's Law:  $\oint \vec{B} \cdot d\vec{s}' = \mu_0 i_{\text{enclosed}}$   
 for B produced by a current closed path

=> combine: Ampère - Maxwell Law:

$$\oint_{\text{closed path}} \vec{B} \cdot d\vec{s}' = \mu_0 i_{\text{enclosed}} + \underbrace{\mu_0 \epsilon_0 \frac{d\Phi_E}{dt}}_{\text{"displacement current"}}$$

Example:

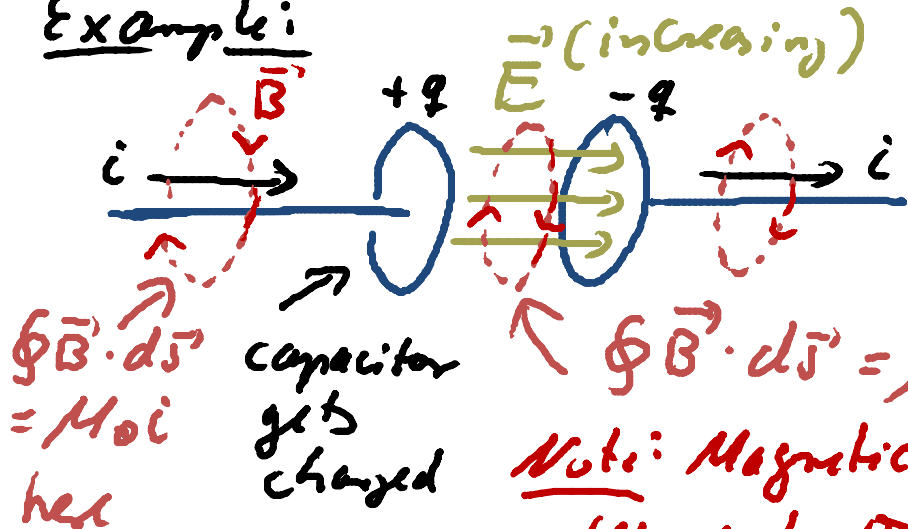

"displacement current"

$$\oint \vec{B} \cdot d\vec{s}' = \mu_0 \left( \epsilon_0 \cdot \frac{d\Phi_E}{dt} \right) \text{ here}$$

Note: Magnetic field lines must surround either currents or changing electric fields (or both).